

# ELEC353 Lecture Notes Set 10

The homework assignments are posted on the course web site.

[http://users.encs.concordia.ca/~trueman/web\\_page\\_353.htm](http://users.encs.concordia.ca/~trueman/web_page_353.htm)


Homework #6: Do homework #6 by February 22, 2019.

Homework #7: Do homework #7 by March 8, 2019.

Homework #8: Do homework #8 by March 15, 2019.

Tentative final exam date: Tuesday April 23, 2019, 9:00 to 12:00.

# Mid Term Grades 2019

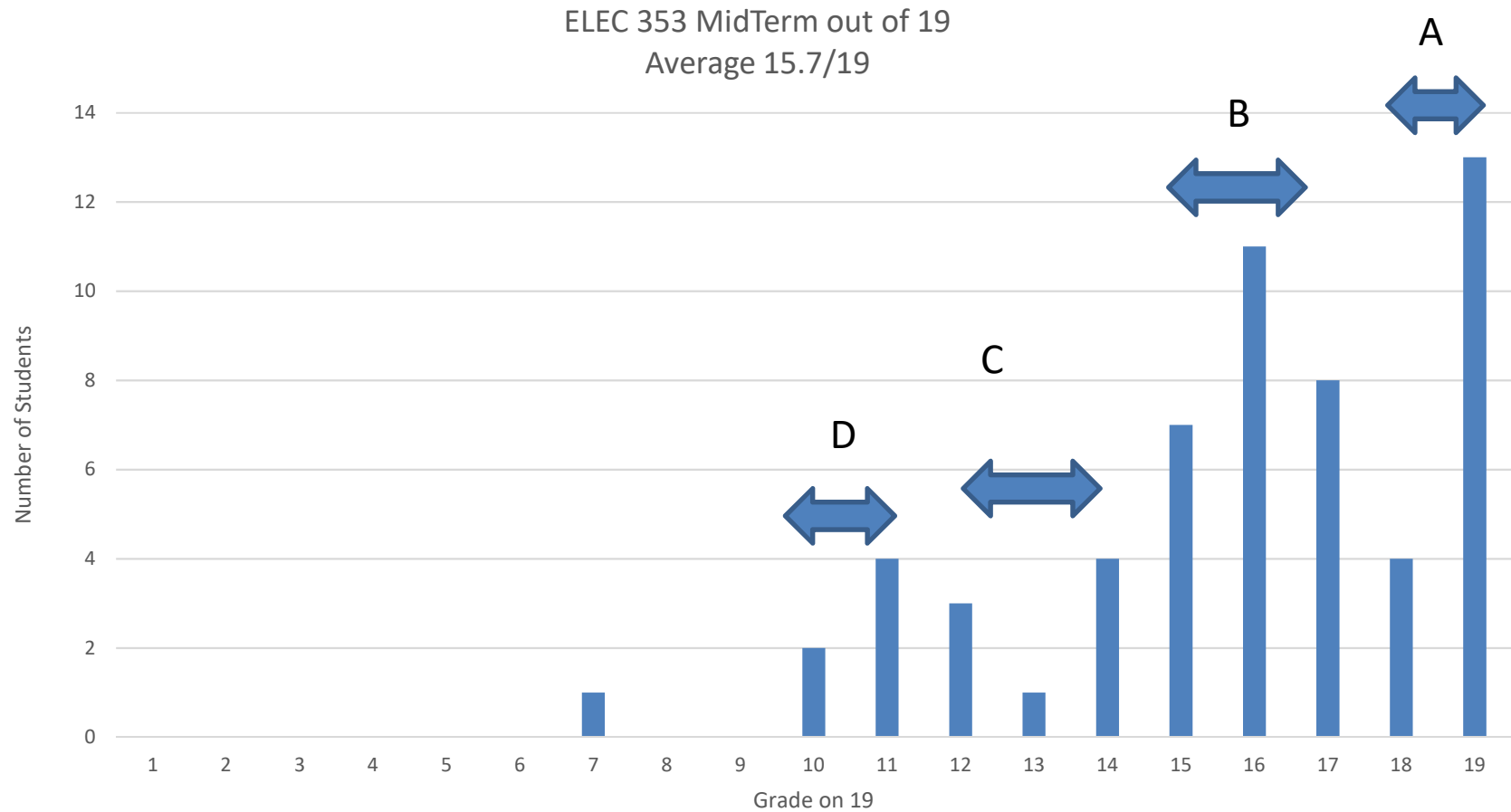

# Topics to be Covered

## Transmission Lines (TLs)

- Wave Equation and Solution
- Solving a TL Circuit
- Standing Wave Patterns
- Impedance Matching
- Bandwidth of Digital Signal

## Plane Waves


- Maxwell's Equations and the Wave Equation
- Plane waves
- Material Boundaries
- Transmission Through a Wall

## Antennas

# Transmission Line Circuits in the Sinusoidal Steady State

Properties  $r, \ell, g, c$

Inan, Inan and Said Section 2.2


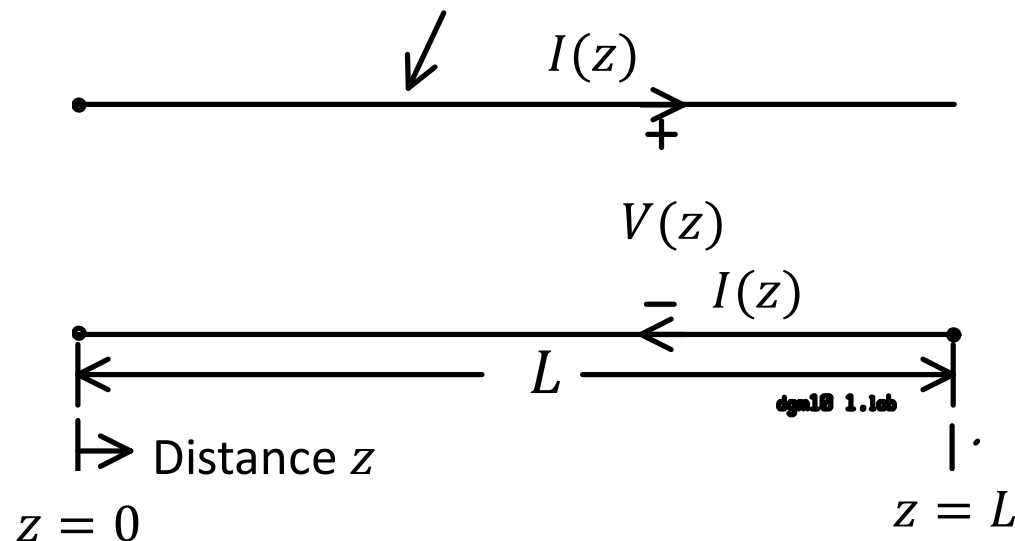



The transmission line parameters are:

- $\ell$  H/m = inductance per unit length
- $c$  F/m = capacitance per unit length
- $r$  ohms/meter = series resistance per unit length
  - series resistance arises because of the currents flowing in the metal of the conductors
- $g$  Siemens/meter = shunt conductance per unit length


# Lossy Transmission Line Equations

Properties  $r, \ell, g, c$

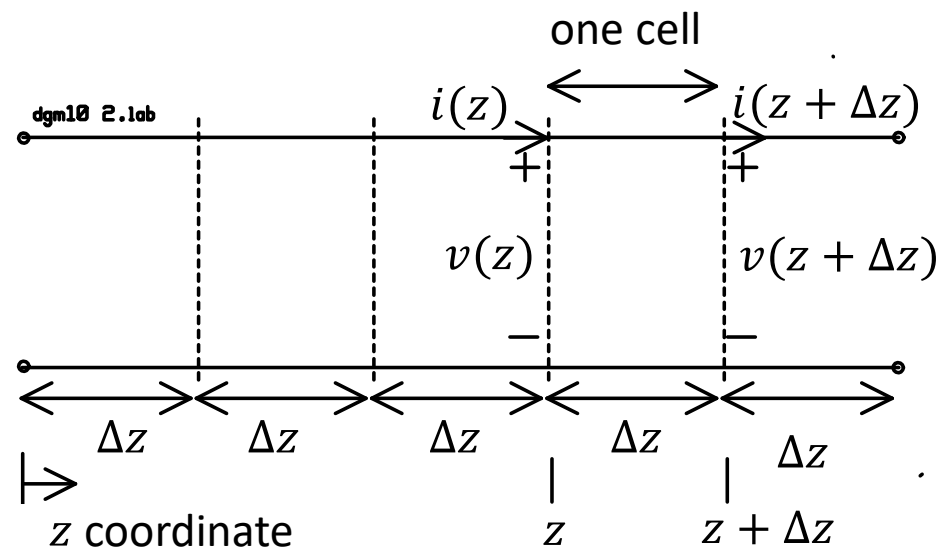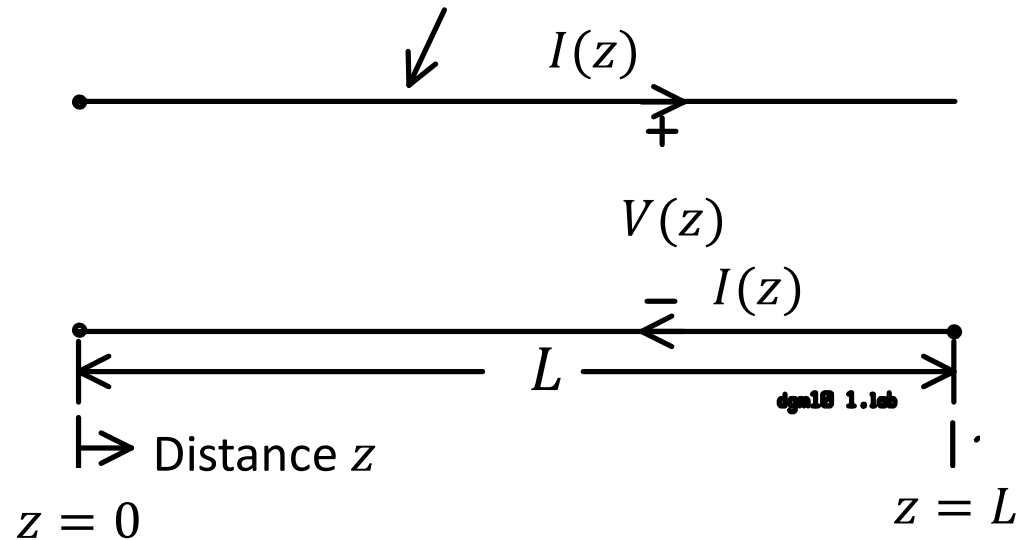


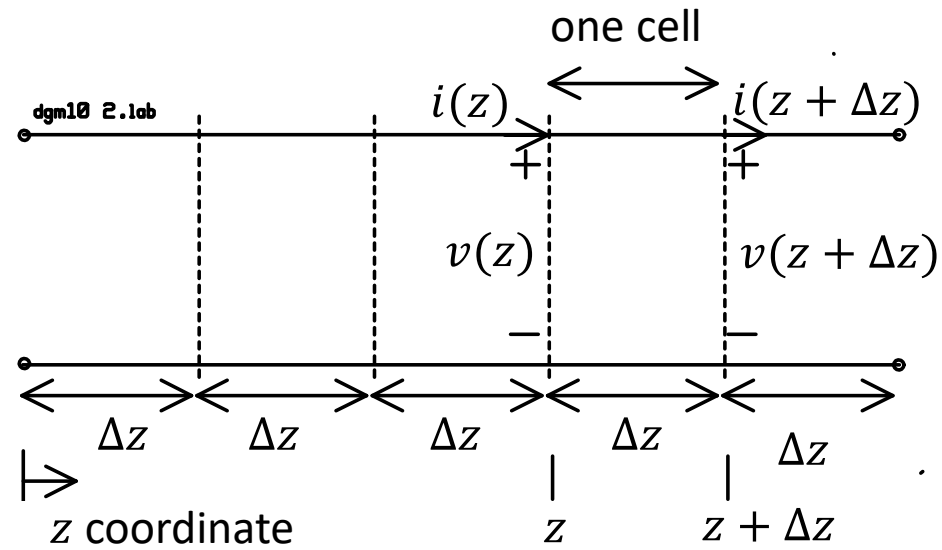

Examine one individual cell.

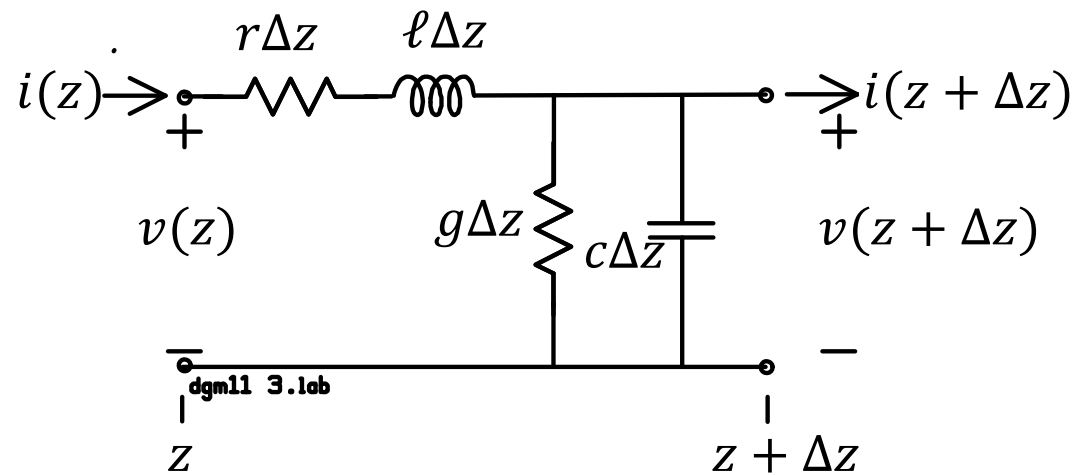

# KVL Equation

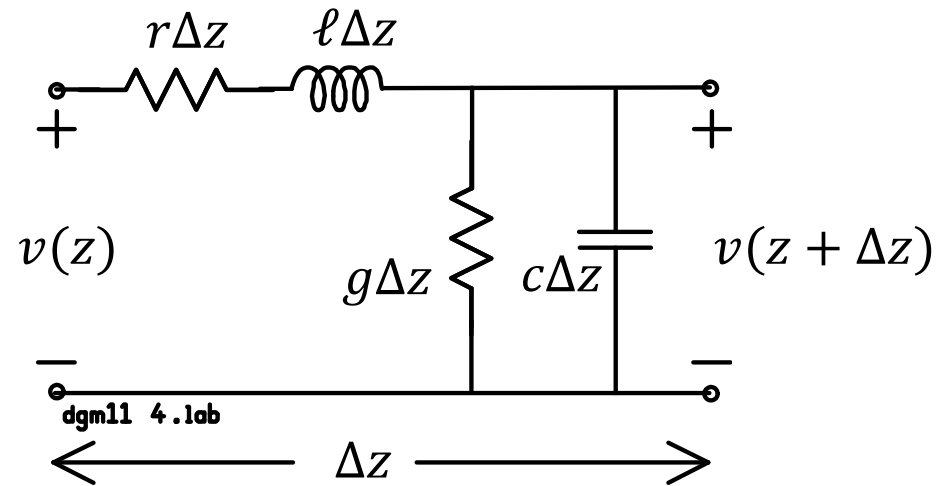

KVL for the cell states:

$$v(z) - r\Delta z i - \ell\Delta z \frac{\partial i}{\partial t} - v(z + \Delta z) = 0$$


Rearrange the KVL equation:

$$v(z + \Delta z) - v(z) = -r\Delta z i - \ell\Delta z \frac{\partial i}{\partial t}$$

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z) - v(z)}{\Delta z} = -ri - \ell \frac{\partial i}{\partial t}$$

$$\frac{\partial v}{\partial z} = -ri - \ell \frac{\partial i}{\partial t}$$

# KCL Equation

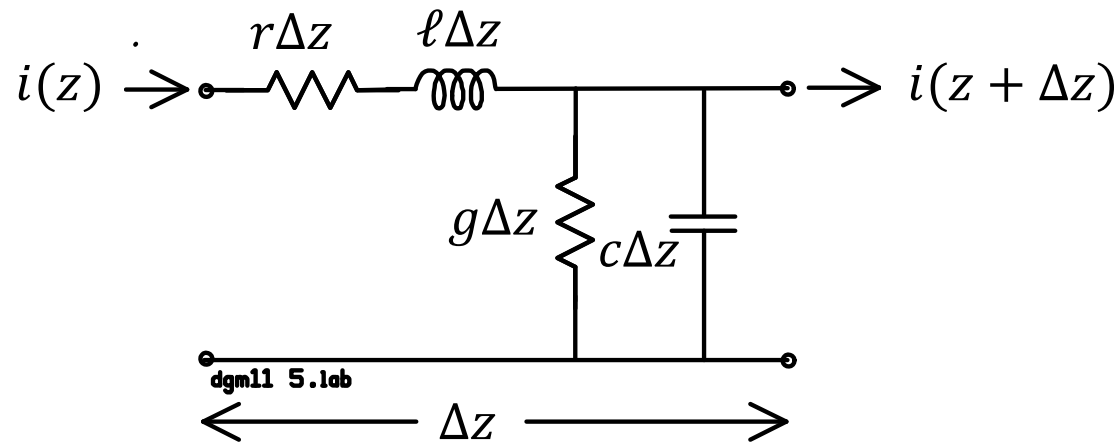

KCL for the cell states:

$$i(z) - g\Delta z v - c\Delta z \frac{\partial v}{\partial t} - i(z + \Delta z) = 0$$


Rearrange the KCL equation:

$$i(z + \Delta z) - i(z) = -g\Delta z v - c\Delta z \frac{\partial v}{\partial t}$$

$$\lim_{\Delta z \rightarrow 0} \frac{i(z + \Delta z) - i(z)}{\Delta z} = -gv - c \frac{\partial v}{\partial t}$$
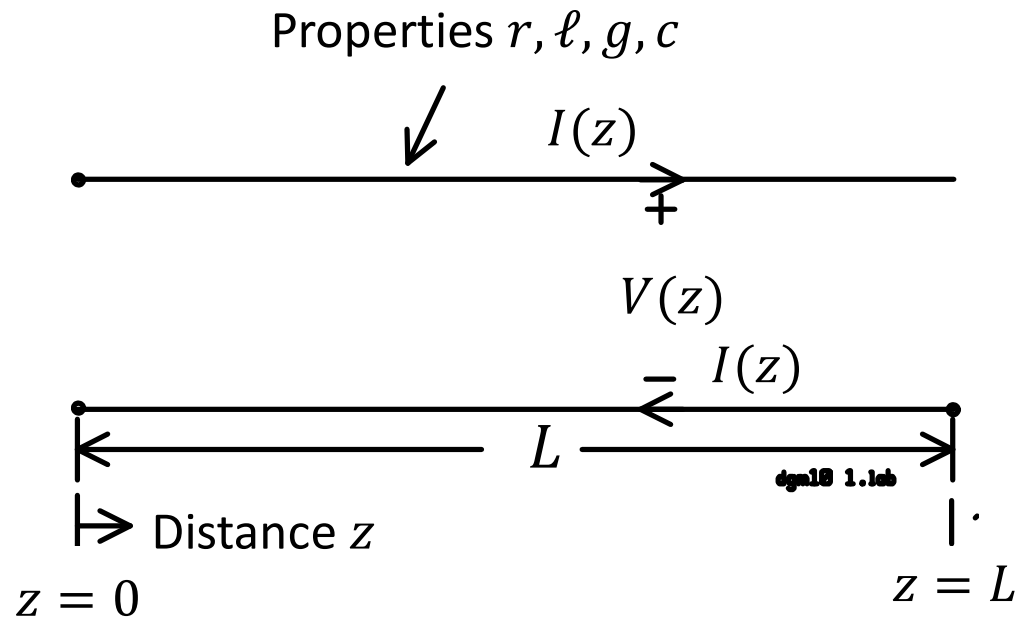
$$\frac{\partial i}{\partial z} = -gv - c \frac{\partial v}{\partial t}$$





We have shown that:

$$\frac{\partial v}{\partial z} = -ri - \ell \frac{\partial i}{\partial t}$$

$$\frac{\partial i}{\partial z} = -gv - c \frac{\partial v}{\partial t}$$

These equations are called “lossy” transmission line equations or “lossy” Telegrapher’s Equations.

# Transmission-Line Equations for the Phasor Voltage and Current

$$v(z, t) = A(z) \cos(\omega t + \theta(z)) \longleftrightarrow V(z) = A(z) e^{j\theta(z)}$$

$$i(z, t) = B(z) \cos(\omega t + \phi(z)) \longleftrightarrow I(z) = B(z) e^{j\phi(z)}$$

The **magnitude** of the phasor is the **amplitude** of the cosine.  
The **angle** of the phasor is the **phase angle** of the cosine.

time differentiation  $\frac{\partial}{\partial t}$  is equivalent to multiplication by  $j\omega$

Homework:  
Prove this!

$$\frac{\partial v}{\partial z} = -ri - \ell \frac{\partial i}{\partial t} \quad \Leftrightarrow \quad \frac{dV}{dz} = -(r + j\omega\ell)I$$

$$\frac{\partial i}{\partial z} = -gv - c \frac{\partial v}{\partial t} \quad \Leftrightarrow \quad \frac{dI}{dz} = -(g + j\omega c)V$$

These are the transmission line equations in the frequency domain.

# Wave Equation for Phasors

Inan, Inan and Said, Section 3.1

$$\frac{dV}{dz} = -(r + j\omega\ell)I \qquad \frac{dI}{dz} = -(g + j\omega c)V$$

$$\frac{d^2V}{dz^2} = -(r + j\omega\ell) \frac{dI}{dz}$$

$$\frac{d^2V}{dz^2} = -(r + j\omega\ell)[-(g + j\omega c)V]$$

$$\frac{d^2V}{dz^2} = (r + j\omega\ell)(g + j\omega c)V$$

Define the “propagation constant” as  $\gamma = \sqrt{(r + j\omega\ell)(g + j\omega c)}$

$$\frac{d^2V}{dz^2} = \gamma^2 V$$

# Solution to the Wave Equation

$$\frac{d^2 V}{dz^2} = \gamma^2 V$$

$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

Prove that  $V(z) = V^+ e^{-\gamma z}$  satisfies the wave equation:

$$\frac{dV}{dz} = \frac{d}{dz} (V^+ e^{-\gamma z}) = -\gamma V^+ e^{-\gamma z}$$

$$\frac{d^2 V}{dz^2} = \frac{d}{dz} (-\gamma V^+ e^{-\gamma z}) = (-\gamma)(-\gamma) V^+ e^{-\gamma z} = \gamma^2 V^+ e^{-\gamma z} = \gamma^2 V$$

Hence  $\frac{d^2 V}{dz^2} = \gamma^2 V$  and  $V = V^+ e^{-\gamma z}$  does indeed satisfy the wave equation.

Homework: prove that  $V = V^- e^{\gamma z}$  satisfies the wave equation.

# Propagation Constant

$$\gamma = \sqrt{(r + j\omega\ell)(g + j\omega c)}$$

$$\gamma = \alpha + j\beta$$

- $\alpha$  is the “attenuation constant” in “Nepers/meter”
  - “Neper” is a “unitless” unit like “radian”.
- $\beta$  is the “phase constant” in radians/meter.

# Current on the Transmission Line

$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$\frac{dV}{dz} = -(r + j\omega\ell)I$$

$$I(z) = \frac{-1}{(r + j\omega\ell)} \frac{dV}{dz}$$

$$I(z) = \frac{-1}{(r + j\omega\ell)} \frac{d}{dz} (V^+ e^{-\gamma z} + V^- e^{\gamma z})$$

$$I(z) = \frac{-1}{(r + j\omega\ell)} (-\gamma V^+ e^{-\gamma z} + \gamma V^- e^{\gamma z})$$

$$I(z) = \frac{\gamma}{(r + j\omega\ell)} (V^+ e^{-\gamma z} - V^- e^{\gamma z})$$

# Characteristic Impedance

$$V = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$I(z) = \frac{\gamma}{(r + j\omega\ell)} (V^+ e^{-\gamma z} - V^- e^{\gamma z})$$

- The “characteristic resistance”  $R_c$  was defined earlier in the course as

$$R_c = \sqrt{\frac{\ell}{c}} \text{ ohms}$$

- For a “lossy” transmission line, define the “characteristic impedance”  $Z_c$  as

$$Z_c = \frac{r + j\omega\ell}{\gamma} = \frac{r + j\omega\ell}{\sqrt{(r + j\omega\ell)(g + j\omega c)}} = \sqrt{\frac{(r + j\omega\ell)^2}{(r + j\omega\ell)(g + j\omega c)}}$$


$$Z_c = \sqrt{\frac{r + j\omega\ell}{g + j\omega c}} \text{ ohms}$$

- Then the current on the transmission line is

$$I(z) = \left( \frac{V^+}{Z_c} e^{-\gamma z} - \frac{V^-}{Z_c} e^{\gamma z} \right)$$

# Summary-Sinusoidal Steady State

Properties  $r, \ell, g, c$

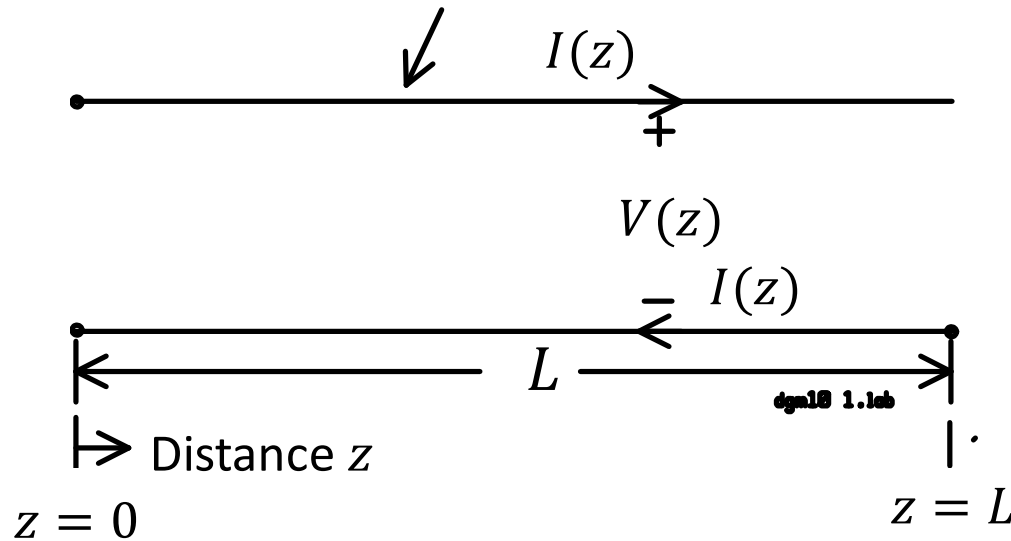

$$\frac{dV}{dz} = -(r + j\omega\ell)I$$

$$\frac{dI}{dz} = -(g + j\omega c)V$$

$$\frac{d^2V}{dz^2} = \gamma^2 V$$

$$\gamma = \sqrt{(r + j\omega\ell)(g + j\omega c)}$$


$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$I(z) = \frac{V^+}{Z_c} e^{-\gamma z} - \frac{V^-}{Z_c} e^{\gamma z}$$

$$Z_c = \sqrt{\frac{r + j\omega\ell}{g + j\omega c}}$$



# Attenuation with Distance Travelled

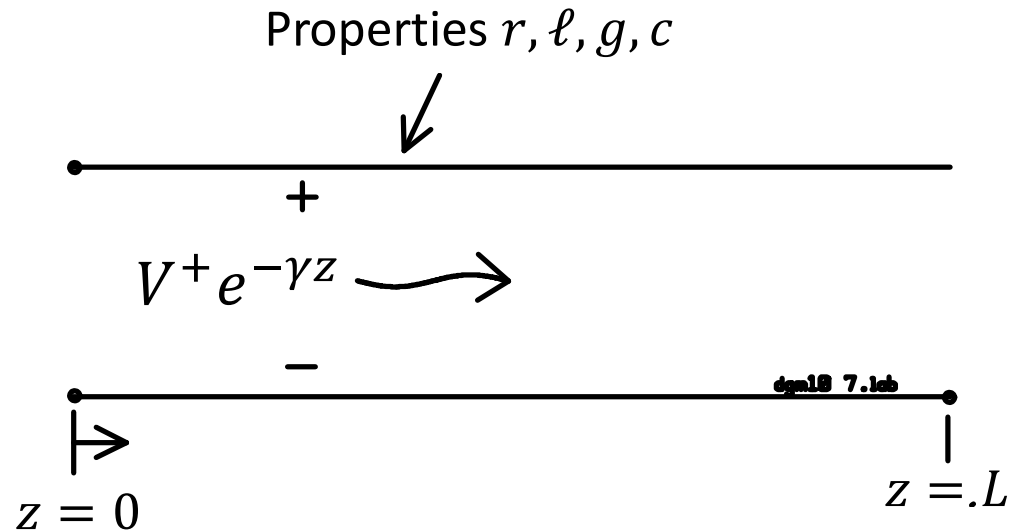

$$V^+ = Ae^{j\theta}$$

$$\gamma = \alpha + j\beta$$

$$V(z) = V^+ e^{-\gamma z}$$

$$V(z) = Ae^{j\theta} e^{-\gamma z}$$

$$V(z) = Ae^{j\theta} e^{-(\alpha + j\beta)z}$$

$$V(z) = Ae^{-\alpha z} e^{j(-\beta z + \theta)}$$

In the time domain:


$$v(z, t) = Ae^{-\alpha z} \cos(\omega t - \beta z + \theta)$$

The amplitude is  $Ae^{-\alpha z}$
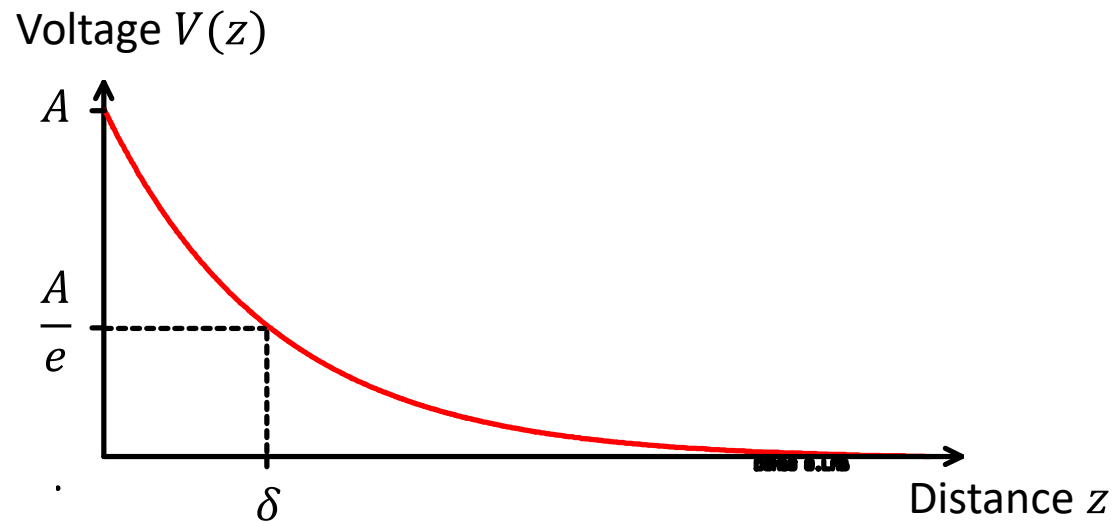
# Exponential Attenuation

$$v(z, t) = Ae^{-\alpha z} \cos(\omega t - \beta z + \theta)$$


The amplitude of  $v(z, t)$  is  $Ae^{-\alpha z}$



- The distance  $\delta$  required for the amplitude to decrease by a factor of  $\frac{1}{e}$  is called the “penetration depth”, or for metals the “skin depth”.

$$Ae^{-\alpha\delta} = \frac{A}{e} \quad \text{so} \quad e^{-\alpha\delta} = \frac{1}{e} \quad \text{so} \quad \delta = \frac{1}{\alpha}$$

# Lossless Transmission Lines

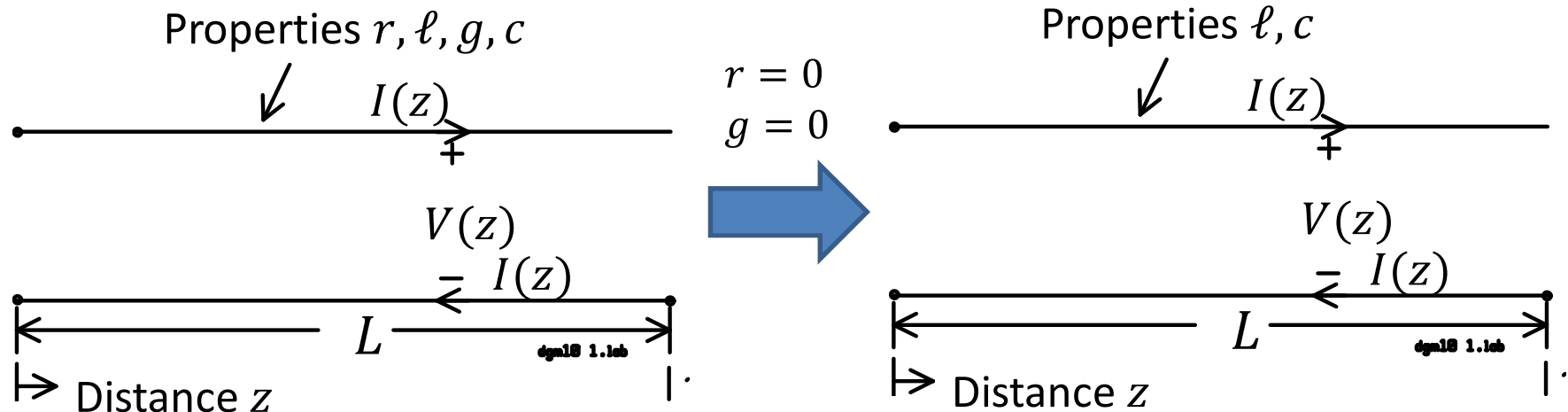

On a “lossless” transmission line, the series-resistance-per-unit-length is zero ( $r = 0$ ) and the shunt-conductance-per-unit-length is zero ( $g = 0$ ).

$$\begin{aligned} \frac{dV}{dz} &= -(r + j\omega\ell)I & \Rightarrow & \frac{dV}{dz} = -j\omega\ell I \\ \frac{dI}{dz} &= -(g + j\omega c)V & \Rightarrow & \frac{dI}{dz} = -j\omega c V \end{aligned}$$

# Lossless Wave Equation

$$\frac{dV}{dz} = -j\omega\ell I$$

$$\frac{dI}{dz} = -j\omega c V$$

$$\frac{d^2V}{dz^2} = -j\omega\ell \frac{dI}{dz} = -j\omega\ell(-j\omega c V) = -\omega^2\ell c V$$

$$\frac{d^2V}{dz^2} = -\omega^2\ell c V$$

$$\gamma = \sqrt{(r + j\omega\ell)(g + j\omega c)} = \sqrt{(j\omega\ell)(j\omega c)} = j\omega\sqrt{\ell c}$$

$$\gamma = \alpha + j\beta$$

So for “lossless” lines:

- $\alpha = 0$  so  $\gamma = j\beta$
- $\beta = \omega\sqrt{\ell c}$

$$\beta^2 = (\omega\sqrt{\ell c})^2 = \omega^2\ell c$$

$$\frac{d^2V}{dz^2} = -\beta^2 V$$

# Solution to the Lossless Wave Equation

$$\frac{d^2 V}{dz^2} = -\beta^2 V$$

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

(Homework: prove this is a solution to  $\frac{d^2 V}{dz^2} = -\beta^2 V$  by direct substitution.)

$$V^+ = |V^+| e^{j\theta^+} = C^+ e^{j\theta^+}$$

$$V^- = |V^-| e^{j\theta^-} = C^- e^{j\theta^-}$$

$$V(z) = C^+ e^{j\theta^+} e^{-j\beta z} + C^- e^{j\theta^-} e^{j\beta z}$$

$$V(z) = C^+ e^{j(-\beta z + \theta^+)} + C^- e^{j(\beta z + \theta^-)}$$

In the time domain:

$$v(z, t) = C^+ \cos(\omega t - \beta z + \theta^+) + C^- \cos(\omega t + \beta z + \theta^-)$$

# Find the Current on the Lossless Transmission Line

$$\frac{dV}{dz} = -j\omega\ell I$$

$$\beta = \omega\sqrt{\ell c}$$

$$\frac{dI}{dz} = -j\omega c V$$

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I = \frac{-1}{j\omega\ell} \frac{dV}{dz} = \frac{-1}{j\omega\ell} \frac{d}{dz} (V^+ e^{-j\beta z} + V^- e^{j\beta z})$$


$$I = \frac{-1}{j\omega\ell} \frac{dV}{dz} = \left( \frac{-1}{j\omega\ell} \right) (-j\beta V^+ e^{-j\beta z} + j\beta V^- e^{j\beta z})$$

$$I = \frac{\beta}{\omega\ell} V^+ e^{-j\beta z} - \frac{\beta}{\omega\ell} V^- e^{j\beta z}$$

$$R_c = \frac{\omega\ell}{\beta} = \frac{\omega\ell}{\omega\sqrt{\ell c}} = \sqrt{\frac{\ell}{c}} \text{ ohms}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$

# Summary – Lossless Transmission Lines

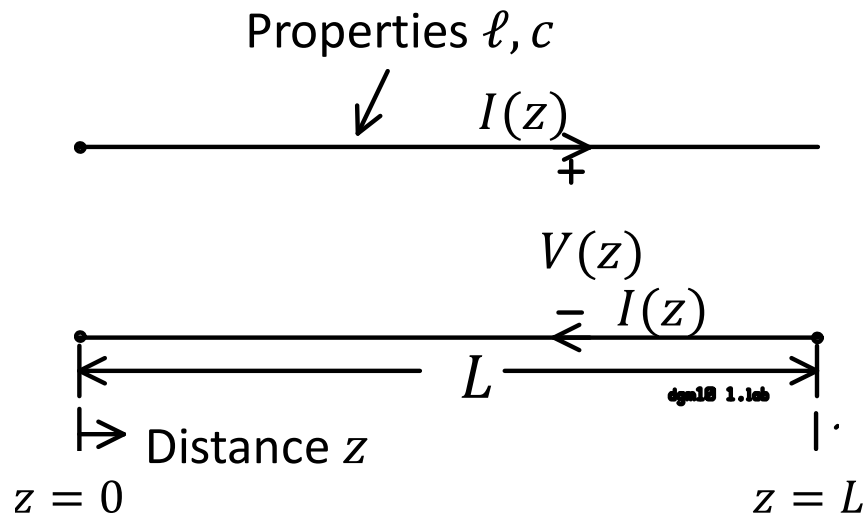

Lossless transmission-line equations:

$$\frac{dV}{dz} = -j\omega\ell I$$

$$\frac{dI}{dz} = -j\omega c V$$

Lossless wave equation:

$$\frac{d^2V}{dz^2} = -\beta^2 V$$

where  $\beta = \omega\sqrt{\ell c}$  is the phase constant.

Characteristic Resistance

$$R_c = \sqrt{\frac{\ell}{c}} \text{ ohms}$$

Voltage and Current

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$


# Find the Wavelength

$$V = Ae^{-j\beta z} \quad \longrightarrow \quad v(z, t) = \text{Re}[Ve^{j\omega t}] = \text{Re}[Ae^{-j\beta z} e^{j\omega t}] = \text{Re}[Ae^{j(\omega t - \beta z)}]$$

$$v(z, t) = \text{Re}[A \cos(\omega t - \beta z) + jA \sin(\omega t - \beta z)]$$

$$v(z, t) = A \cos(\omega t - \beta z)$$

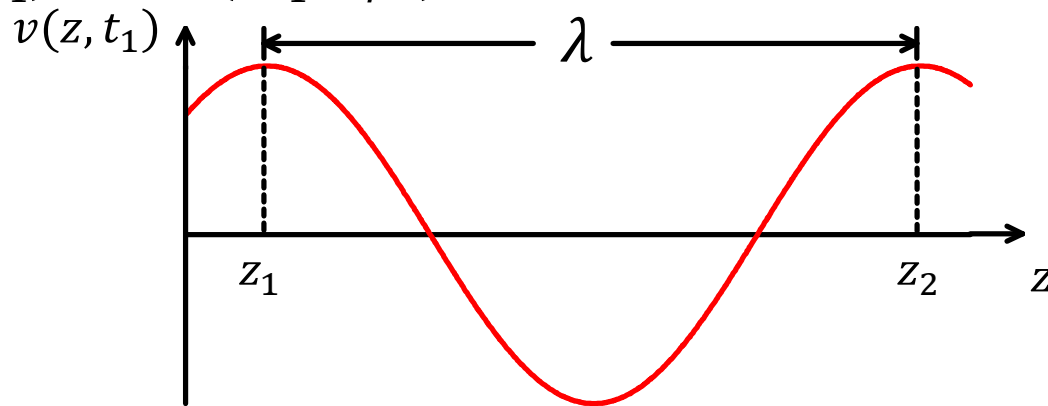At  $t = t_1$ , graph  $v(z, t_1) = A \cos(\omega t_1 - \beta z)$ :



$\cos(\omega t - \beta z)$  is a maximum when  $(\omega t - \beta z) = \dots, -2\pi, 0, 2\pi, \dots$

$$z_1 = ? \quad \omega t_1 - \beta z_1 = 0 \quad \text{so} \quad z_1 = \frac{\omega t_1}{\beta}$$

$$z_2 = ? \quad z_2 > z_1 \text{ and as } z \text{ increases, } (\omega t - \beta z) \text{ becomes more negative, so}$$


$$\omega t_1 - \beta z_2 = -2\pi \quad \text{so} \quad z_2 = \frac{\omega t_1 + 2\pi}{\beta}$$

$$\lambda = ? \quad \lambda = z_2 - z_1 = \frac{\omega t_1 + 2\pi}{\beta} - \frac{\omega t_1}{\beta} = \frac{2\pi}{\beta}$$



# Find the Speed of Travel

$$v(z, t) = A \cos(\omega t - \beta z)$$

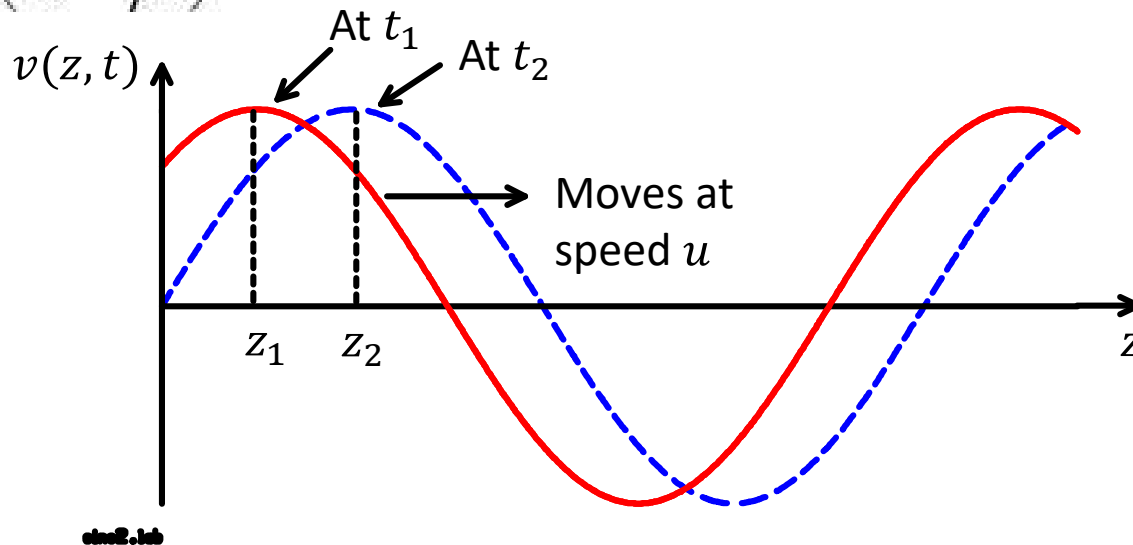

How far does the wave travel between  $t = t_1$  and  $t = t_2$  ?

At  $t = t_1$  find  $z_1 = ?$       $\omega t_1 - \beta z_1 = 0$  so  $z_1 = \frac{\omega t_1}{\beta}$

At  $t = t_2$  find  $z_2 = ?$       $\omega t_2 - \beta z_2 = 0$  so  $z_2 = \frac{\omega t_2}{\beta}$

The speed of travel or “phase velocity is  $u = \text{distance} / \text{time} =$  ?

$$u = \frac{z_2 - z_1}{t_2 - t_1} = \frac{\frac{\omega t_2}{\beta} - \frac{\omega t_1}{\beta}}{t_2 - t_1} = \frac{\frac{\omega}{\beta} (t_2 - t_1)}{t_2 - t_1} = \frac{\omega}{\beta}$$

# Wavelength and Speed of Travel

In general the wavelength is  $\lambda = \frac{2\pi}{\beta}$

In general the speed of travel is  $u = \frac{\omega}{\beta}$

For a lossless transmission line  $\beta = \omega\sqrt{\ell c}$

$$u = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{\ell c}} = \frac{1}{\sqrt{\ell c}}$$


$$u = \frac{1}{\sqrt{\ell c}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega/u} = \frac{2\pi u}{\omega} = \frac{u}{f}$$

$$\lambda = \frac{u}{f}$$

$$\beta = \omega\sqrt{\ell c} = \frac{\omega}{1/\sqrt{\ell c}} = \frac{\omega}{u}$$

# Summary – Lossless Transmission Lines

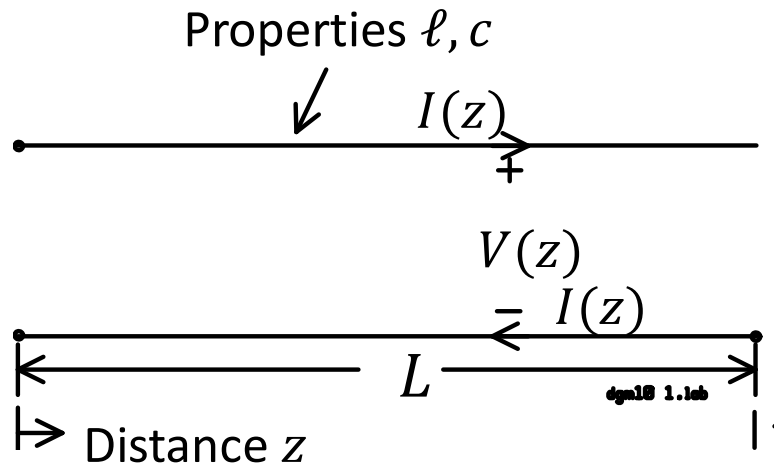

Lossless transmission line equations:

$$\frac{dV}{dz} = -j\omega\ell I$$

$$\frac{dI}{dz} = -j\omega c V$$

Lossless wave equation:

$$\frac{d^2V}{dz^2} = -\beta^2 V$$

where  $\beta = \omega\sqrt{\ell c}$  is the phase constant.

Voltage and current:

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$

Characteristic resistance:

$$R_c = \sqrt{\frac{\ell}{c}}$$

In general:

$$u = \frac{\omega}{\beta}$$

$$\lambda = \frac{2\pi}{\beta}$$

Lossless case:


$$u = \frac{1}{\sqrt{\ell c}}$$

$$\lambda = \frac{u}{f}$$

$$\beta = \omega\sqrt{\ell c} = \frac{\omega}{u}$$

# Transmission Line Terminated with a Load

Inan and Inan Sections 3.2 and 3.3

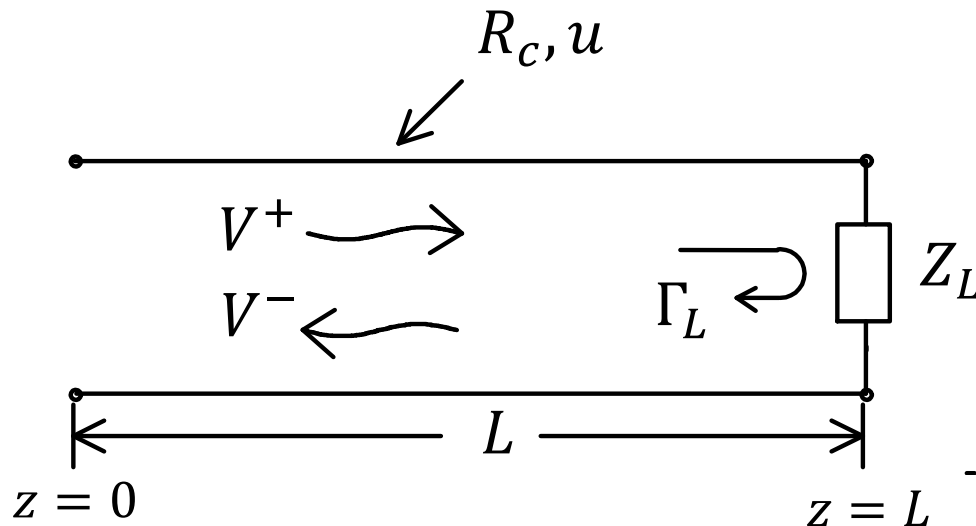

Voltage and current:

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$

If we know  $V^+$ , can we find  $V^-$ ?

At the load we must satisfy  $V(L) = Z_L I(L)$

$$V(L) = V^+ e^{-j\beta L} + V^- e^{j\beta L}$$

$$I(L) = \frac{V^+}{R_c} e^{-j\beta L} - \frac{V^-}{R_c} e^{j\beta L}$$

$$V(L) = Z_L I(L)$$

$$V^+ e^{-j\beta L} + V^- e^{j\beta L} = Z_L \left( \frac{V^+}{R_c} e^{-j\beta L} - \frac{V^-}{R_c} e^{j\beta L} \right)$$

$$V^- = \frac{Z_L - R_c}{Z_L + R_c} e^{-j2\beta L} V^+$$

# Reflection Coefficient at the Load

Definition:

$$\Gamma_L = \frac{V^- e^{j\beta L}}{V^+ e^{-j\beta L}}$$


From the previous page:

$$V^- = V^+ e^{-2j\beta L} \frac{Z_L - R_c}{Z_L + R_c}$$


$$\Gamma_L = \frac{V^+ e^{-2j\beta L} \frac{Z_L - R_c}{Z_L + R_c} e^{j\beta L}}{V^+ e^{-j\beta L}}$$

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c}$$

$$V^- = \Gamma_L e^{-j2\beta L} V^+$$

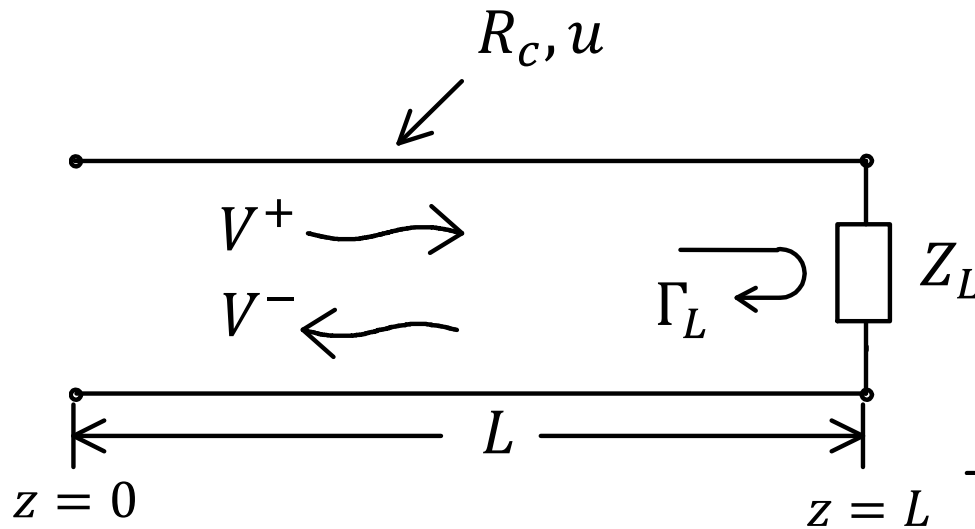

# Matched Load

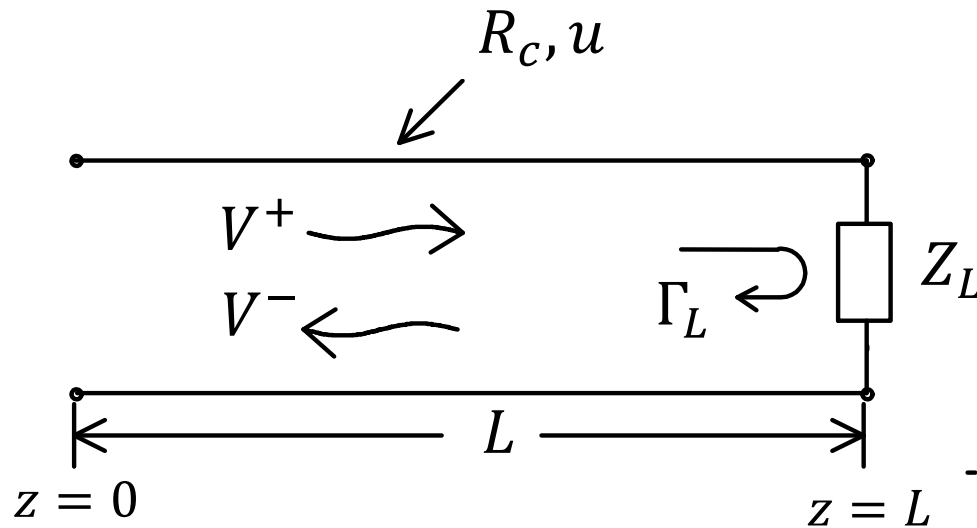

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c}$$


Matched load  $Z_L = R_c$ :

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c} = \frac{R_c - R_c}{R_c + R_c} = 0$$

The reflected voltage is

$$V^- = \Gamma_L e^{-j2\beta L} V^+ = 0$$

# Voltage and Current using $\Gamma_L$

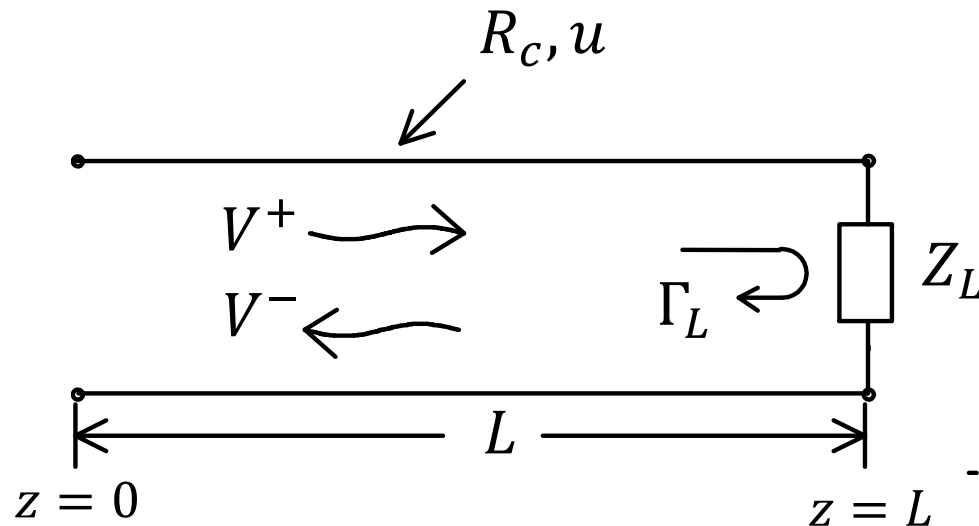

Voltage and Current

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$


$$V^- = \Gamma_L e^{-j2\beta L} V^+$$

$$\begin{aligned} V(z) &= V^+ e^{-j\beta z} + V^- e^{j\beta z} \\ &= V^+ e^{-j\beta z} + \Gamma_L e^{-j2\beta L} V^+ e^{j\beta z} \\ &= V^+ \left( e^{-j\beta z} + \Gamma_L e^{-j2\beta L} e^{j\beta z} \right) \end{aligned}$$

$$V(z) = V^+ e^{-j\beta z} \left( e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)} \right)$$

$$I(z) = V^+ e^{-j\beta z} \left( \frac{1}{R_c} e^{-j\beta(z-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(z-L)} \right)$$

# Impedance as a function of position

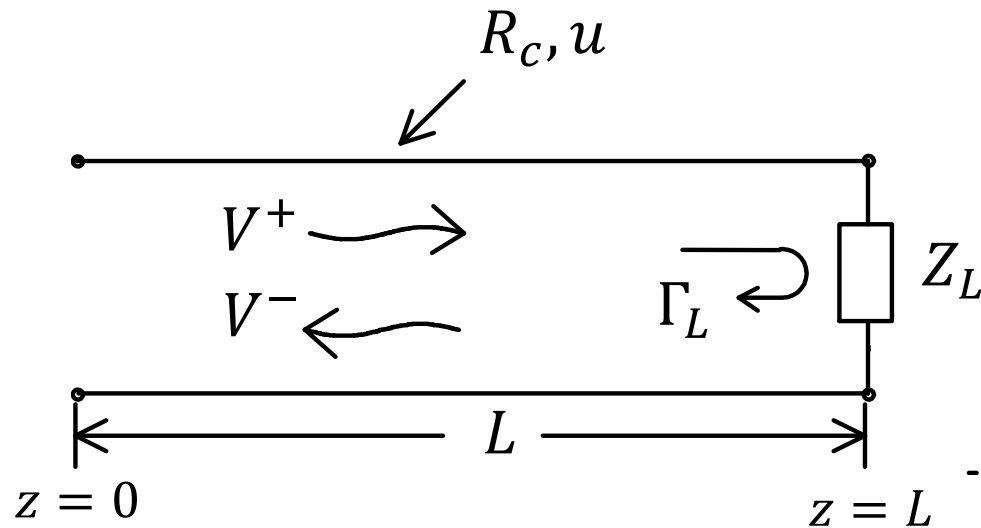

$$V(z) = V^+ e^{-j\beta z} \left( e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)} \right)$$

$$I(z) = V^+ e^{-j\beta z} \left( \frac{1}{R_c} e^{-j\beta(z-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(z-L)} \right)$$

At any location  $z$  on the transmission line, define the impedance  $Z(z)$  as

$$Z(z) = \frac{V(z)}{I(z)} = \frac{V^+ e^{-j\beta L} (e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)})}{V^+ e^{-j\beta L} \left( \frac{1}{R_c} e^{-j\beta(z-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(z-L)} \right)}$$



# Impedance $Z(z)$

At any location  $z$  on the transmission line, define the impedance  $Z(z)$  as

$$Z(z) = \frac{V(z)}{I(z)} = \frac{V^+ e^{-j\beta L} (e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)})}{V^+ e^{-j\beta L} \left( \frac{1}{R_c} e^{-j\beta(z-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(z-L)} \right)}$$


$$Z(z) = R_c \frac{(e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)})}{(e^{-j\beta(L-z)} - \Gamma_L e^{j\beta(L-z)})}$$

$$Z(z) = R_c \frac{e^{-j\beta(z-L)} (1 + \Gamma_L e^{j2\beta(z-L)})}{e^{-j\beta(z-L)} (1 - \Gamma_L e^{j2\beta(z-L)})}$$

$$Z(z) = R_c \frac{(1 + \Gamma_L e^{j2\beta(z-L)})}{(1 - \Gamma_L e^{j2\beta(z-L)})}$$

We will use this formula later!

# The Input Impedance

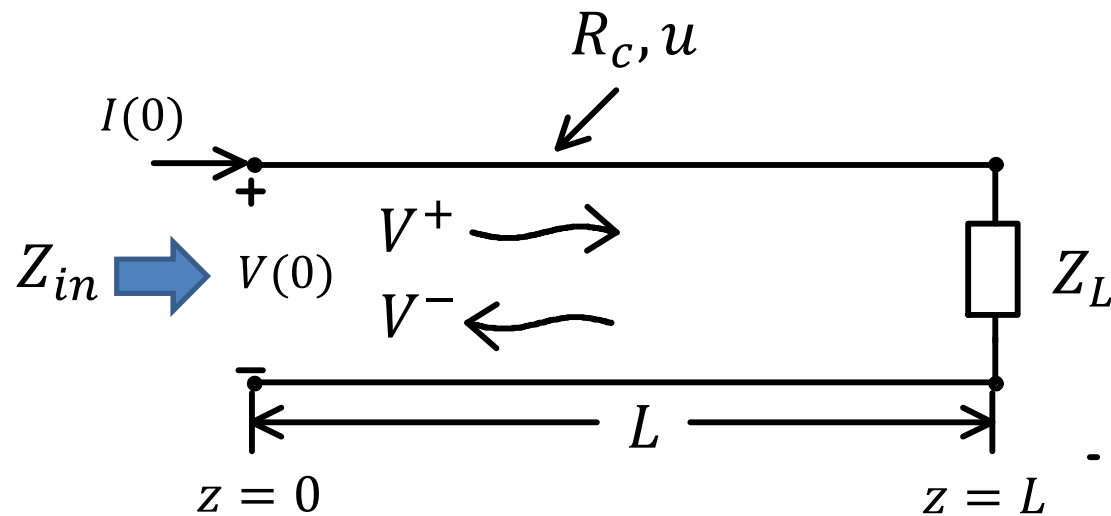

$$V(z) = V^+ e^{-j\beta z} (e^{-j\beta(z-L)} + \Gamma_L e^{j\beta(z-L)})$$

$$I(z) = V^+ e^{-j\beta z} \left( \frac{1}{R_c} e^{-j\beta(z-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(z-L)} \right)$$

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c}$$

$$Z_{in} = \frac{V(0)}{I(0)}$$

$$V(0) = V^+ e^{-j\beta \cdot 0} (e^{-j\beta(0-L)} + \Gamma_L e^{j\beta(0-L)})$$

$$V(0) = V^+ e^{-j\beta \cdot 0} (e^{j\beta L} + \Gamma_L e^{-j\beta L})$$

$$I(0) = V^+ e^{-j\beta \cdot 0} \left( \frac{1}{R_c} e^{-j\beta(0-L)} - \frac{1}{R_c} \Gamma_L e^{j\beta(0-L)} \right)$$

$$I(0) = V^+ e^{-j\beta \cdot 0} \left( \frac{1}{R_c} e^{j\beta L} - \frac{1}{R_c} \Gamma_L e^{-j\beta L} \right)$$

$$Z_{in} = \frac{V(z=0)}{I(z=0)} = \frac{V^+ e^{-j\beta \cdot 0} (e^{j\beta L} + \Gamma_L e^{-j\beta L})}{V^+ e^{-j\beta \cdot 0} \left( \frac{1}{R_c} e^{j\beta L} - \frac{1}{R_c} \Gamma_L e^{-j\beta L} \right)}$$


$$Z_{in} = R_c \frac{Z_L + jR_c \tan \beta L}{R_c + jZ_L \tan \beta L}$$

Homework: do the missing algebra to derive this formula.

# Important Special Cases
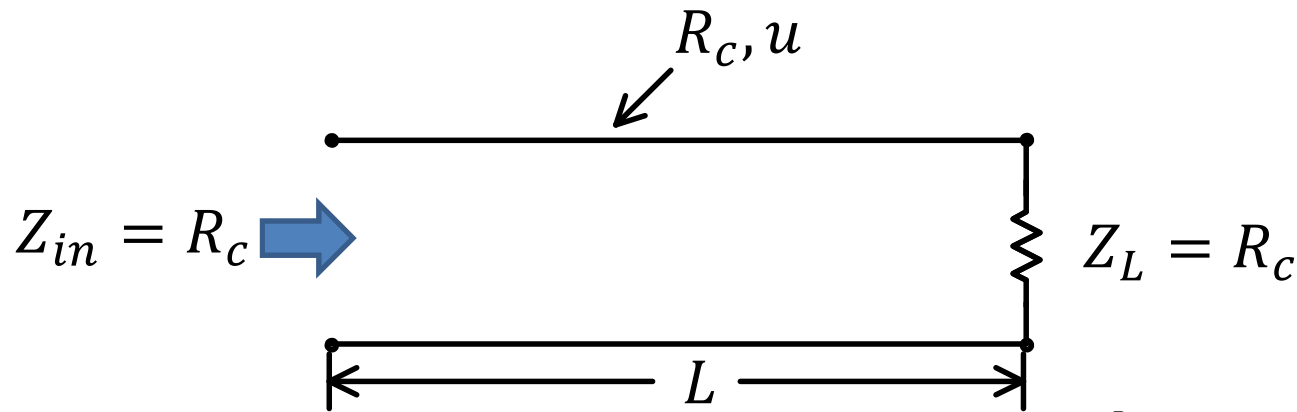
## Matched Load

- What is the input impedance of a transmission line terminated with a matched load?




- If  $Z_L = R_c$ , then the input impedance is

$$Z_{in} = R_c \frac{Z_L + jR_c \tan \beta L}{R_c + jZ_L \tan \beta L} = R_c \frac{R_c + jR_c \tan \beta L}{R_c + jR_c \tan \beta L} = R_c$$

- So the input impedance of a transmission line terminated with a matched load is  $Z_{in} = R_c$ .
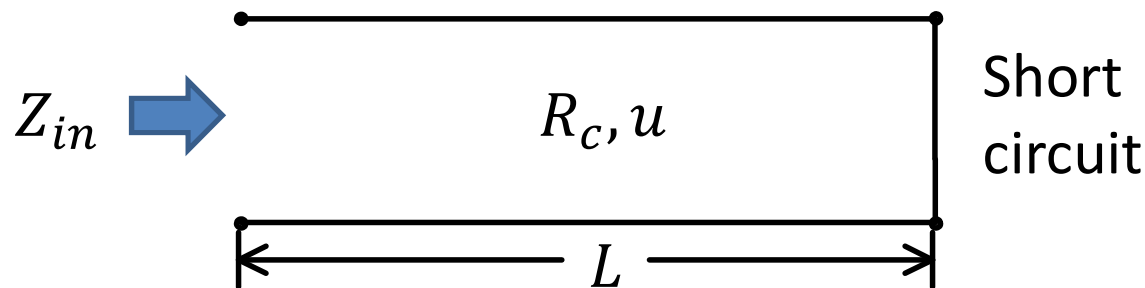
### Short-Circuited Transmission Line


- What is the input impedance of a transmission line terminated with a short circuit?




- A short length of transmission line terminated with a short circuit is called a “stub” and can be used for impedance matching. (We will do this later in the course.)
- What is the input impedance of a transmission line terminated with a short circuit,  $Z_L = 0$ ?

$$Z_{in} = R_c \frac{Z_L + jR_c \tan \beta L}{R_c + jZ_L \tan \beta L} = R_c \frac{0 + jR_c \tan \beta L}{R_c + j0 \tan \beta L} = jR_c \tan \beta L$$
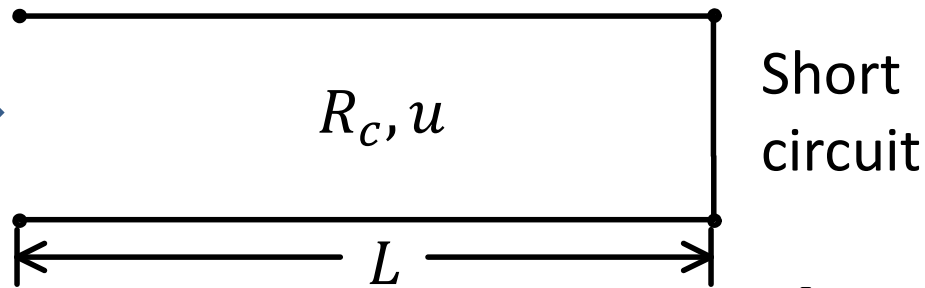
$$Z_{in} = jR_c \tan \beta L \rightarrow$$



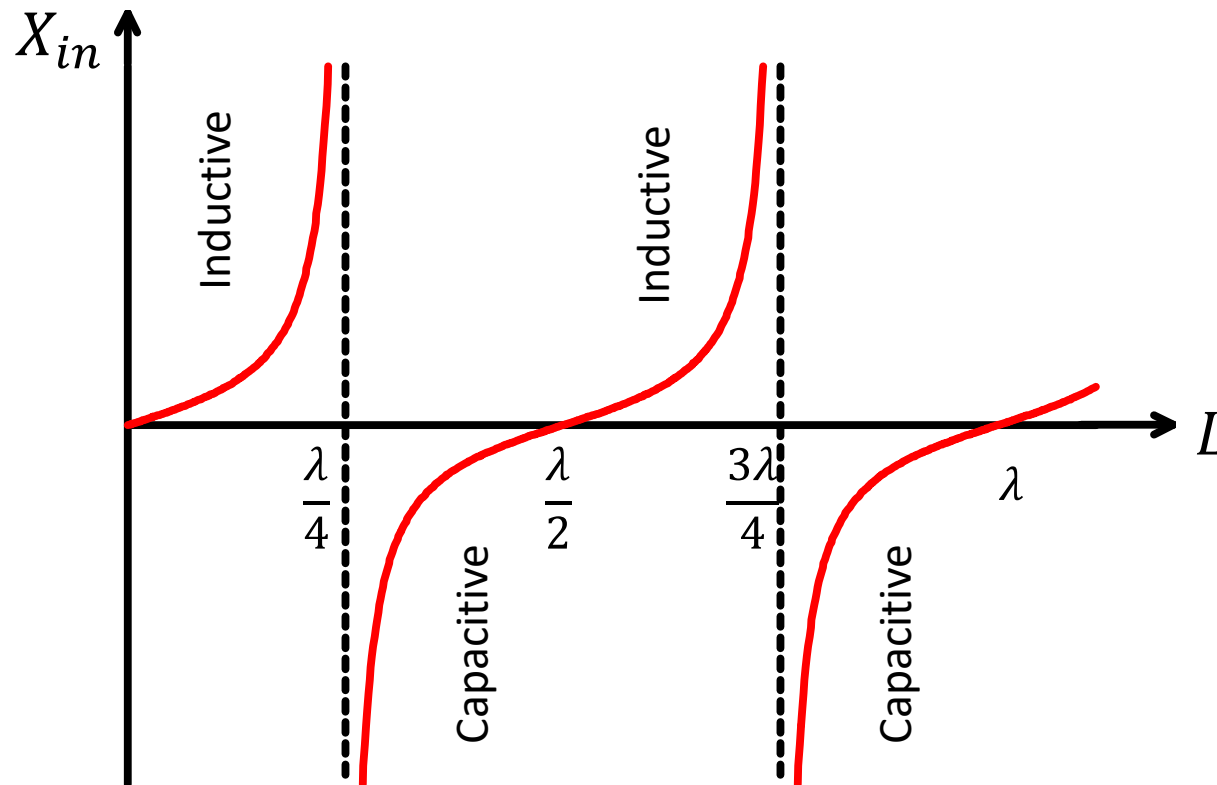- $Z_{in} = jR_c \tan \beta L$  is “reactive”, meaning that it is pure imaginary.
- We can write  $Z_{in} = jX_{in}$  where the reactance is  $X_{in} = R_c \tan \beta L$



When  $\beta L \rightarrow \frac{\pi}{2}$ ,  $\tan \beta L \rightarrow +\infty$ .

$$L = \frac{\pi}{2\beta} = \frac{\pi}{2 \frac{2\pi}{\lambda}} = \frac{\lambda}{4}$$

## Open-Circuited Transmission Line

- What is the input impedance of a transmission line terminated with an open circuit,  $Z_L \rightarrow \infty$ ?

$$Z_{in} = \lim_{Z_L \rightarrow \infty} R_c \frac{Z_L + jR_c \tan \beta L}{R_c + jZ_L \tan \beta L}$$

$$Z_{in} = R_c \frac{Z_L}{jZ_L \tan \beta L} = -jR_c \cot \beta L$$

- $Z_{in} = -jR_c \cot \beta L$  is “reactive” meaning pure imaginary.
- We can write  $Z_{in} = jX_{in}$  where the reactance is  $X_{in} = -R_c \cot \beta L$

