

ELEC353 Lecture Notes Set 12

The homework assignments are posted on the course web site.

http://users.encs.concordia.ca/~trueman/web_page_353.htm

Homework #7: Do homework #7 by March 8, 2019.

Homework #8: Do homework #8 by March 15, 2019.

Homework #9: Do homework #9 by March 22, 2019.

Tutorial Workshop #8: Friday March 8, 2019.

Tutorial Workshop #9: Friday March 15, 2019.

Tutorial Workshop #10: Friday March 22, 2019.

Final exam date: Tuesday April 23, 2019, 9:00 to 12:00, in H531.

Topics to be Covered

Transmission Lines (TLs)

- Wave Equation and Solution - done
- Solving a TL Circuit - done
- Standing Wave Patterns
- Impedance Matching
- Bandwidth of Digital Signal


Plane Waves

- Maxwell's Equations and the Wave Equation
- Plane waves
- Material Boundaries
- Transmission Through a Wall

Antennas

Review:

Summary – Lossless Transmission Lines

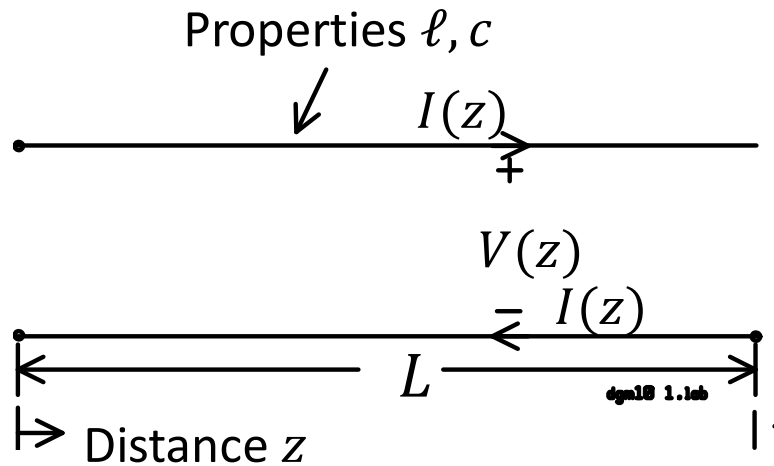

Lossless transmission line equations:

$$\frac{dV}{dz} = -j\omega\ell I$$
$$\frac{dI}{dz} = -j\omega c V$$

Lossless wave equation:

$$\frac{d^2V}{dz^2} = -\beta^2 V$$

where $\beta = \omega\sqrt{\ell c}$ is the phase constant.

Voltage and current:

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+}{R_c} e^{-j\beta z} - \frac{V^-}{R_c} e^{j\beta z}$$

Characteristic resistance:

$$R_c = \sqrt{\frac{\ell}{c}}$$

In general:

$$u = \frac{\omega}{\beta}$$

$$\lambda = \frac{2\pi}{\beta}$$


Lossless case:

$$u = \frac{1}{\sqrt{\ell c}}$$

$$\lambda = \frac{u}{f}$$

$$\beta = \omega\sqrt{\ell c} = \frac{\omega}{u}$$

Last class we solved this example:

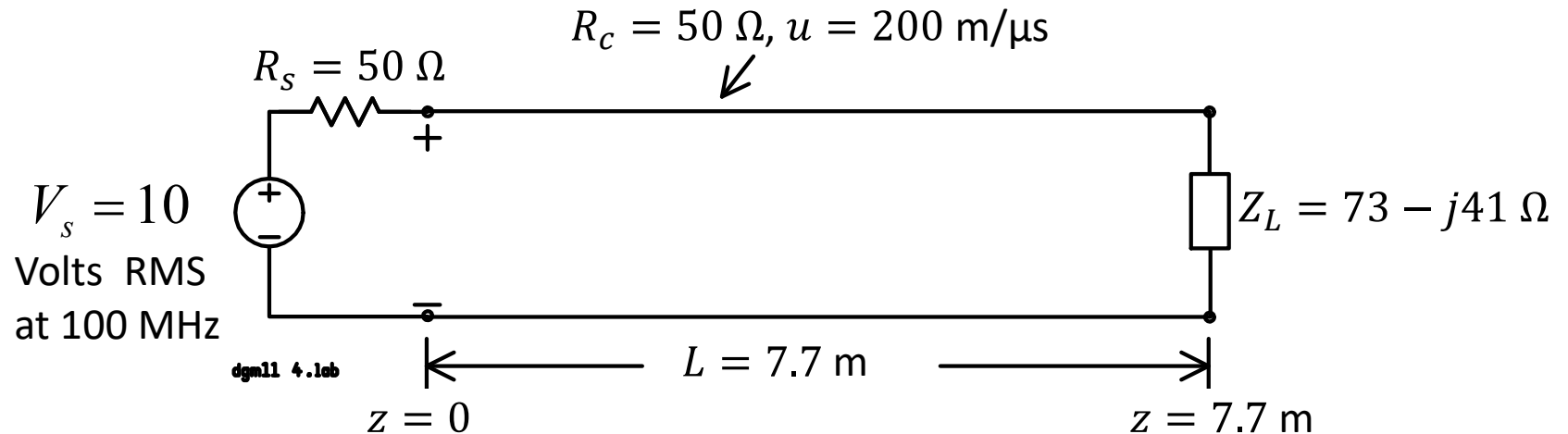


In general, $V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$

We solved the circuit to find: $V^+ = 5\angle 0^\circ$
 $V^- = 1.813\angle 65.73^\circ$

Then the voltage on the transmission line is:

$$V(z) = 5e^{-j\beta z} + 1.813e^{j65.73^\circ} e^{j\beta z}$$

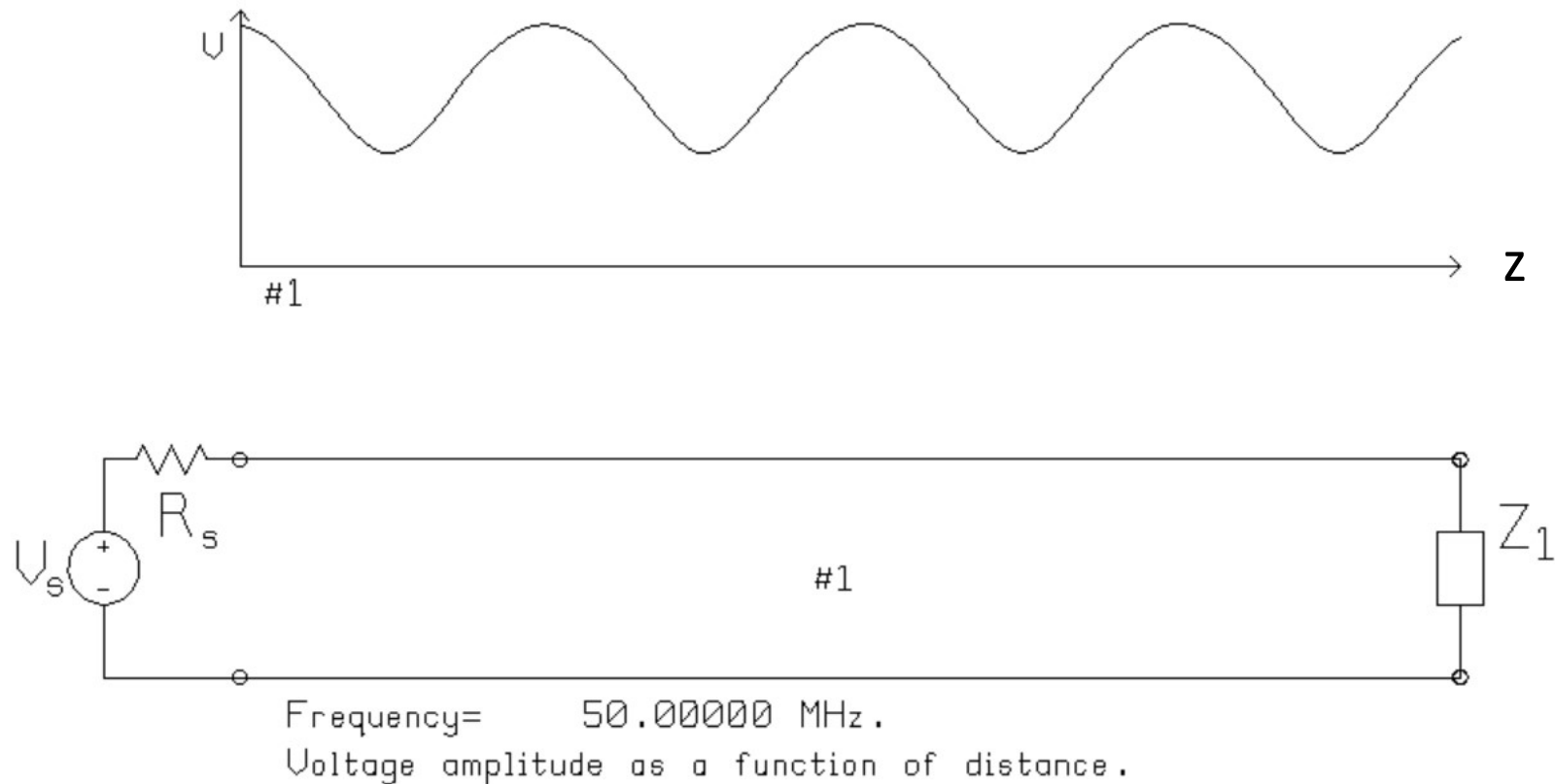
What is the Voltage on the Transmission Line?



$$V(z) = 5e^{-j\beta z} + 1.813e^{j65.73^\circ}e^{j\beta z}$$

This is called an “interference pattern” or “standing-wave pattern” and is formed as $5e^{-j\beta z}$ and $1.813e^{j65.73^\circ}e^{j\beta z}$ go in and out of phase.

Standing Waves and Interference Patterns

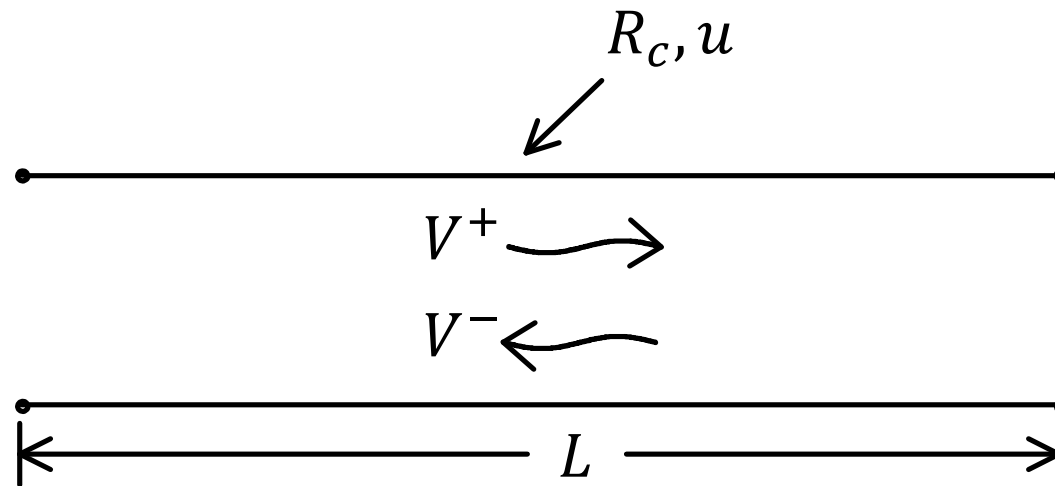

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$V^+ = A^+ e^{j\theta^+}$$

$$V^- = A^- e^{j\theta^-}$$

$$V(z) = A^+ e^{j\theta^+} e^{-j\beta z} + A^- e^{j\theta^-} e^{j\beta z}$$

$$V(z) = A^+ e^{j(\theta^+ - \beta z)} + A^- e^{j(\theta^- + \beta z)}$$

Interference Pattern

$$V(z) = A^+ e^{j(\theta^+ - \beta z)} + A^- e^{j(\theta^- + \beta z)}$$

Graph the amplitude of the A.C. voltage as a function of position.

The amplitude of the voltage $A(z)$ is the magnitude of the phasor, so

$$A(z) = |V(z)| = \left| A^+ e^{j(\theta^+ - \beta z)} + A^- e^{j(\theta^- + \beta z)} \right|$$

Maxima

As z increases, there will be locations where $e^{j(\theta^+ - \beta z)}$ and $A^- e^{j(\theta^- + \beta z)}$ are in phase: $(\theta^+ - \beta z) = (\theta^- + \beta z) \pm 2n\pi$

Then $e^{j(\theta^+ - \beta z)} = e^{j(\theta^- + \beta z)}$ and so the largest amplitude is

$$A_{max} = A^+ + A^- = |V^+| + |V^-|$$

Minima

There will be locations where $e^{j(\theta^+ - \beta z)}$ and $A^- e^{j(\theta^- + \beta z)}$ are out of phase: $(\theta^+ - \beta z) = (\theta^- + \beta z) + \pi \pm 2n\pi$

Then $e^{j(\theta^+ - \beta z)} = -e^{j(\theta^- + \beta z)}$ and so

$$A_{min} = A^+ - A^- = |V^+| - |V^-|$$

Standing-Wave Ratio

The standing-wave ratio is defined as

$$SWR = \frac{A_{max}}{A_{min}}$$
$$SWR = \frac{A^+ + A^-}{A^+ - A^-} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|}$$

Standing-Wave Ratio

The standing-wave ratio is defined as

$$SWR = \frac{\max}{\min} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|}$$

For the example previously given,


$$V(z) = 5e^{-j\beta z} + 1.813e^{j65.73^\circ}e^{j\beta z}$$

Hence the maximum value is

$$A_{max} = |V^+| + |V^-| = 5 + 1.813 = 6.813$$

And the minimum value is

$$A_{min} = |V^+| - |V^-| = 5 - 1.813 = 3.187$$

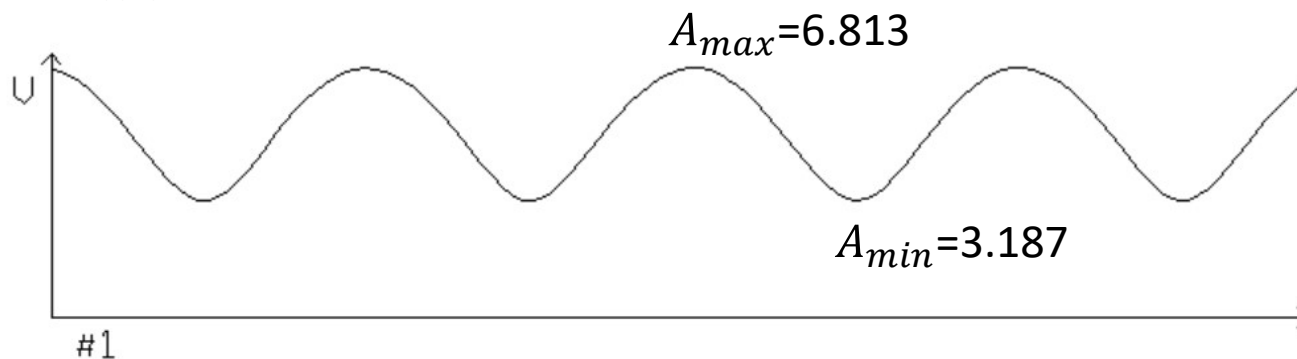

$$SWR = \frac{6.813}{3.187} = 2.14$$

z

Where are the maxima and minima?

$$V(z) = A^+ e^{j(\theta^+ - \beta z)} + A^- e^{j(\theta^- + \beta z)}$$

$$v(z, t) = A^+ \cos(\omega t + \theta^+ - \beta z) + A^- \cos(\omega t + \theta^- + \beta z)$$

There will be a maximum at locations where $A^+ \cos(\omega t + \theta^+ - \beta z)$ and

$A^- \cos(\omega t + \theta^- + \beta z)$ are in phase. This is true when:

$$(\theta^+ - \beta z) = (\theta^- + \beta z) \pm 2n\pi$$

$$2\beta z = (\theta^+ - \theta^-) \mp 2n\pi$$

$$z = \frac{(\theta^+ - \theta^-) \mp 2n\pi}{2\beta}$$

There will be a minimum at locations where $A^+ \cos(\omega t + \theta^+ - \beta z)$ and

$A^- \cos(\omega t + \theta^- + \beta z)$ are out of phase:

$$(\theta^+ - \beta z) = (\theta^- + \beta z) + \pi \pm 2n\pi$$

$$z = \frac{(\theta^+ - \theta^-) - \pi \mp 2n\pi}{2\beta}$$

$$z = \frac{(\theta^+ - \theta^-) - \pi \mp 2n\pi}{2\beta}$$

In terms of the wavelength: $\beta = \frac{2\pi}{\lambda}$

$$z = \frac{(\theta^+ - \theta^-) - \pi \mp 2n\pi}{2 \frac{2\pi}{\lambda}}$$

$$z = \frac{(\theta^+ - \theta^-)\lambda - \pi\lambda \mp 2n\pi\lambda}{4\pi}$$

$$z = \frac{(\theta^+ - \theta^-)\lambda}{4\pi} - \frac{\lambda}{4} \mp n \frac{\lambda}{2}$$

Define the principal minimum as


$$z_o = \frac{(\theta^+ - \theta^-)\lambda}{4\pi} - \frac{\lambda}{4}$$

Then the minima are at

$$z = z_o \pm n \frac{\lambda}{2}$$

Review:

Standing Wave Pattern

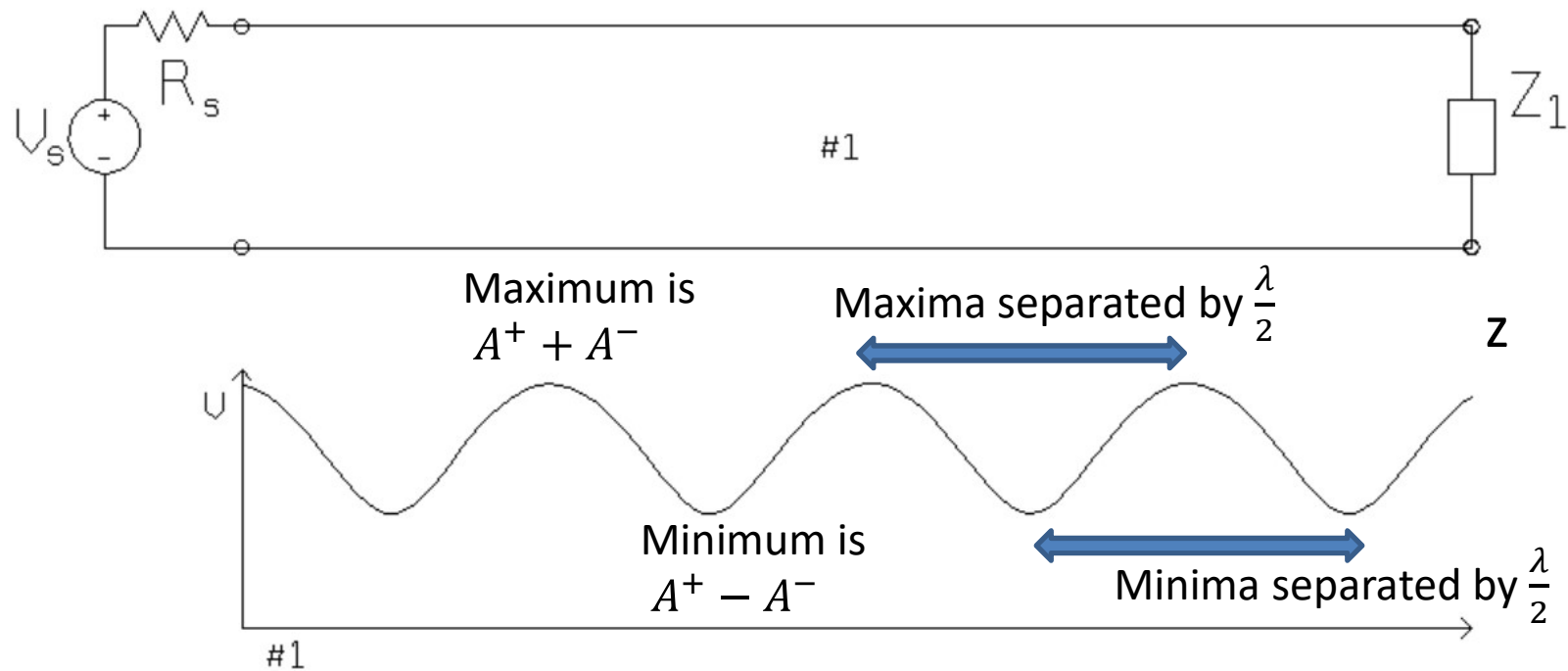


$$V(z) = (A^+ e^{j\theta^+})e^{-j\beta z} + (A^- e^{j\theta^-})e^{j\beta z}$$

$$SWR = \frac{\text{Maximum}}{\text{Minimum}} = \frac{A^+ + A^-}{A^+ - A^-}$$

$$\text{The minima are located at } z = \frac{(\theta^+ - \theta^-)\lambda}{4\pi} - \frac{\lambda}{4} \mp 2n\frac{\lambda}{4}$$

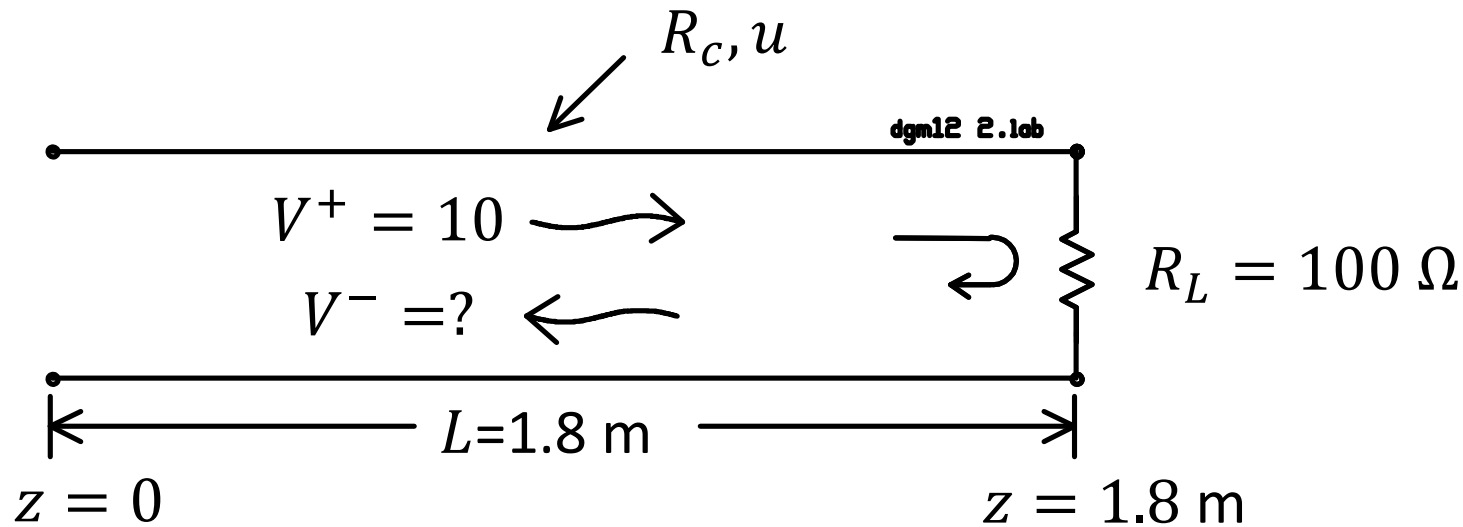
Example: Find the maxima and minima and the SWR.



A transmission line is 1.8 m long and the complex amplitude of the positive-going traveling wave is $V^+ = 10$ volts with zero phase angle. The characteristic impedance is $Z_0 = 50$ ohms and the speed of propagation is $u = 300$ meters per microsecond ($=30 \text{ cm/ns}$). The frequency is 300 MHz. Find:

- (1) The complex amplitude of the reflected wave
- (2) The position of the maxima in the standing-wave pattern
- (3) The position of the minima in the standing-wave pattern
- (4) The largest voltage and the smallest voltage on the transmission line
- (5) The “standing wave ratio” $\text{SWR} = \text{largest voltage} / \text{smallest voltage}$
- (6) Run TRLINE to verify the SWR, and the position of the minima and maxima.

Solution

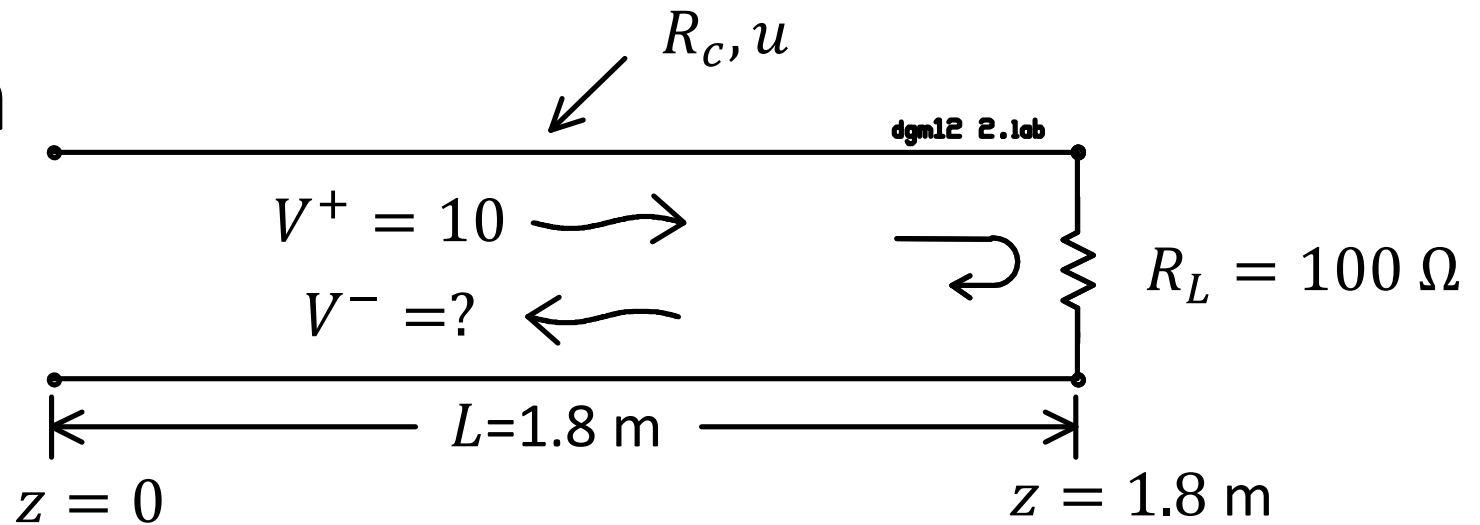

$$V^- = V^+ \Gamma_L e^{-2j\beta L} \quad \text{where } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = 0.3333$$

$$\lambda = \frac{u}{f} = \frac{300}{300} = 1 \text{ meter}$$

$$\beta = \frac{2\pi}{\lambda} = 2\pi \text{ radians/meter or in degrees, } \beta = 360 \text{ degrees/meter}$$

$$V^- = V^+ \Gamma_L e^{-2j\beta L} \quad \text{where } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$-2\beta L = -2 \cdot 360 \cdot 1.8 = -1296 \text{ degrees}$$

○ remove the full 360 degree cycles:

$$-2\beta L = -1296 + 4 \times 360 = 144 \text{ degrees}$$

$$V^- = V^+ \Gamma_L e^{-2j\beta L} = 10 \cdot 0.3333 \cdot e^{j144^\circ} = 3.333e^{j144^\circ}$$

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} \text{ amounts to}$$

$$V(z) = 10e^{-j\beta z} + 3.333e^{j144^\circ} e^{j\beta z}$$

Find the Maxima

$$V(z) = 10e^{-j\beta z} + 3.333e^{j144^\circ}e^{j\beta z}$$

Where is $10e^{-j\beta z}$ in phase with $3.333e^{j(\beta z + 144^\circ)}$?

$$-\beta z = (\beta z + 144^\circ) \pm 360n$$

$$2\beta z = -144^\circ \mp 360n$$

$$z = \frac{-144^\circ}{2\beta} \mp \frac{360n}{2\beta}$$

$\beta = 360$ degree/meter so $2\beta = 720$

$$z = \frac{-144}{720} \mp \frac{360n}{720}$$

$$z = -0.2 \mp 0.5n$$

$$z = +0.3, +0.8, +1.3, 1.8$$

Maxima:

$$|V^+| + |V^-| = 10 + 3.333 = 13.333$$

Find the Minima

$$V(z) = 10e^{-j\beta z} + 3.333e^{j144^\circ}e^{j\beta z}$$

Where is $10e^{-j\beta z}$ 180 degrees out of phase with $3.333e^{j144^\circ}e^{j\beta z}$?

$$-\beta z = (\beta z + 144^\circ) \pm 360n + 180^\circ$$

$$2\beta z = -144^\circ \mp 360n - 180^\circ$$

$$z = \frac{-144^\circ}{2\beta} \mp \frac{360n}{2\beta} - \frac{180}{2\beta}$$

$$\beta = 360 \text{ degrees/meter}$$

$$z = \frac{-144}{720} \mp \frac{360n}{720} - \frac{180}{720}$$

$$z = -0.45 \mp 0.5n$$

$$z = +0.05, +0.55, +1.05, +1.55$$

Minima:

$$|V^+| - |V^-| = 10 - 3.333 = 6.667$$

Standing-Wave Ratio

The standing-wave ratio is defined as


$$SWR = \frac{\max}{\min} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|}$$

$$\text{Maxima: } |V^+| + |V^-| = 10 + 3.333 = 13.333$$

$$\text{Minima: } |V^+| - |V^-| = 10 - 3.333 = 6.667$$

$$SWR = \frac{\max}{\min} = \frac{13.333}{6.667} = 2$$

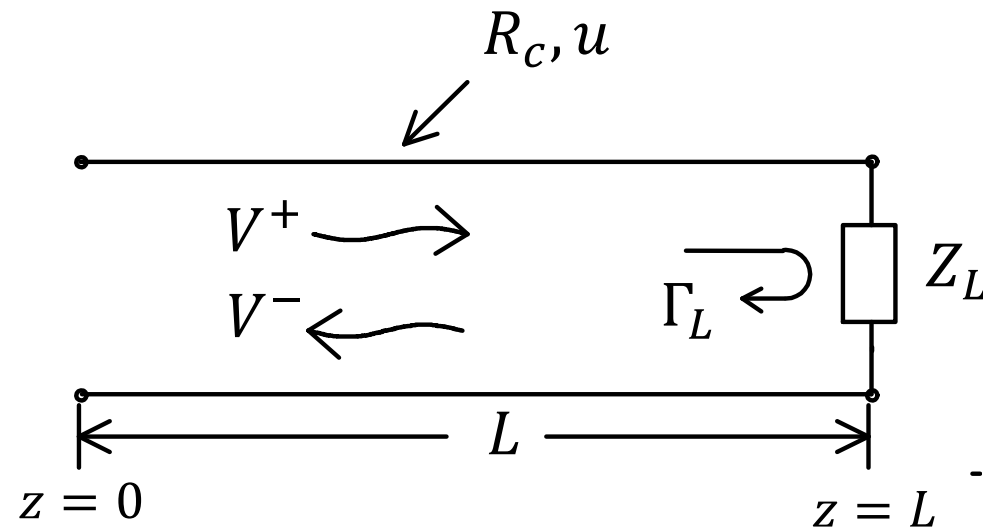Find a Load Impedance from a Standing-Wave Pattern



$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$V^- = V^+ \Gamma_L e^{-2j\beta L}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = |\Gamma_L| e^{j\phi} \quad \text{magnitude } |\Gamma_L| \text{ and angle } \phi$$

Can we find Z_L from a standing-wave pattern?

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$V^+ = A^+ e^{j\theta^+}$$

$$V^- = A^- e^{j\theta^-} \quad V(z) = A^+ e^{j\theta^+} e^{-j\beta z} + A^- e^{j\theta^-} e^{j\beta z}$$

Previously we have shown that the standing-wave ratio is

$$SWR = \frac{\max}{\min} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|}$$

And that the minima in the standing wave pattern are at

$$z_n = \frac{(\theta^+ - \theta^-)\lambda}{4\pi} - \frac{\lambda}{4} \mp n \frac{\lambda}{2}$$

Can we find the load impedance Z_L from the SWR and the location of one of the minima?

What does the SWR tell us?

$$SWR = \frac{|V^+| + |V^-|}{|V^+| - |V^-|}$$

Since $V^- = V^+ \Gamma_L e^{-2j\beta L}$ we can write

$$\begin{aligned}|V^-| &= |V^+| |\Gamma_L| e^{-2j\beta L} \\ |V^-| &= |V^+| |\Gamma_L|\end{aligned}$$

So

$$SWR = \frac{|V^+| + |V^+| |\Gamma_L|}{|V^+| - |V^+| |\Gamma_L|}$$

$$SWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Hence if we know the SWR we can find $|\Gamma_L|$ as

$$|\Gamma_L| = \frac{SWR - 1}{SWR + 1}$$

What does the location of a minimum tell us?

We can find the angle of the reflection coefficient ϕ from the location of a minimum on the transmission line. How?

$$V^- = V^+ \Gamma_L e^{-2j\beta L}$$

We can expand Γ_L in terms of magnitude and angle as $\Gamma_L = |\Gamma_L| e^{j\phi}$ so

$$V^- = V^+ |\Gamma_L| e^{j\phi} e^{-2j\beta L}$$

$$V^+ = A^+ e^{j\theta^+} \text{ and } V^- = A^- e^{j\theta^-}$$

$$A^- e^{j\theta^-} = A^+ e^{j\theta^+} |\Gamma_L| e^{j\phi} e^{-2j\beta L}$$

$$A^- e^{j\theta^-} = A^+ |\Gamma_L| e^{j(\theta^+ + \phi - 2\beta L)}$$

When two complex numbers are equal, the angles must be equal so

$$\theta^- = \theta^+ + \phi - 2\beta L$$

$$\theta^+ - \theta^- = -\phi + 2\beta L$$

$$\theta^+ - \theta^- = -\phi + 2 \frac{2\pi}{\lambda} L$$

$$\theta^+ - \theta^- = -\phi + \frac{4\pi}{\lambda} L$$

The minima are located at

$$z_n = \frac{(\theta^+ - \theta^-)\lambda}{4\pi} - \frac{\lambda}{4} \mp n \frac{\lambda}{2}$$

$$z_n = \frac{(-\phi + \frac{4\pi}{\lambda} L)\lambda}{4\pi} - \frac{\lambda}{4} \mp n \frac{\lambda}{2}$$

$$z_n = \frac{-\phi\lambda}{4\pi} + L - \frac{\lambda}{4} \mp n \frac{\lambda}{2}$$

$$L - z_n = \frac{\phi\lambda}{4\pi} + \frac{\lambda}{4} \pm n \frac{\lambda}{2}$$

Choose the minimum closest to the load

$$L - z = \frac{\phi\lambda}{4\pi} + \frac{\lambda}{4}$$

Solve for ϕ

$$\phi = \frac{4\pi}{\lambda} (L - z) - \pi$$


Knowing the distance $L - z$ from a minimum to the load tells us the angle of the reflection coefficient.

It is convenient to rewrite this formula in degrees as:

$$\phi = \frac{4\pi}{\lambda} (L - z) - \pi$$
$$\phi = 720^\circ \frac{L - z}{\lambda} - 180^\circ$$

Find $\Gamma_L = |\Gamma_L|e^{j\phi}$ from a Measured Standing-Wave Pattern

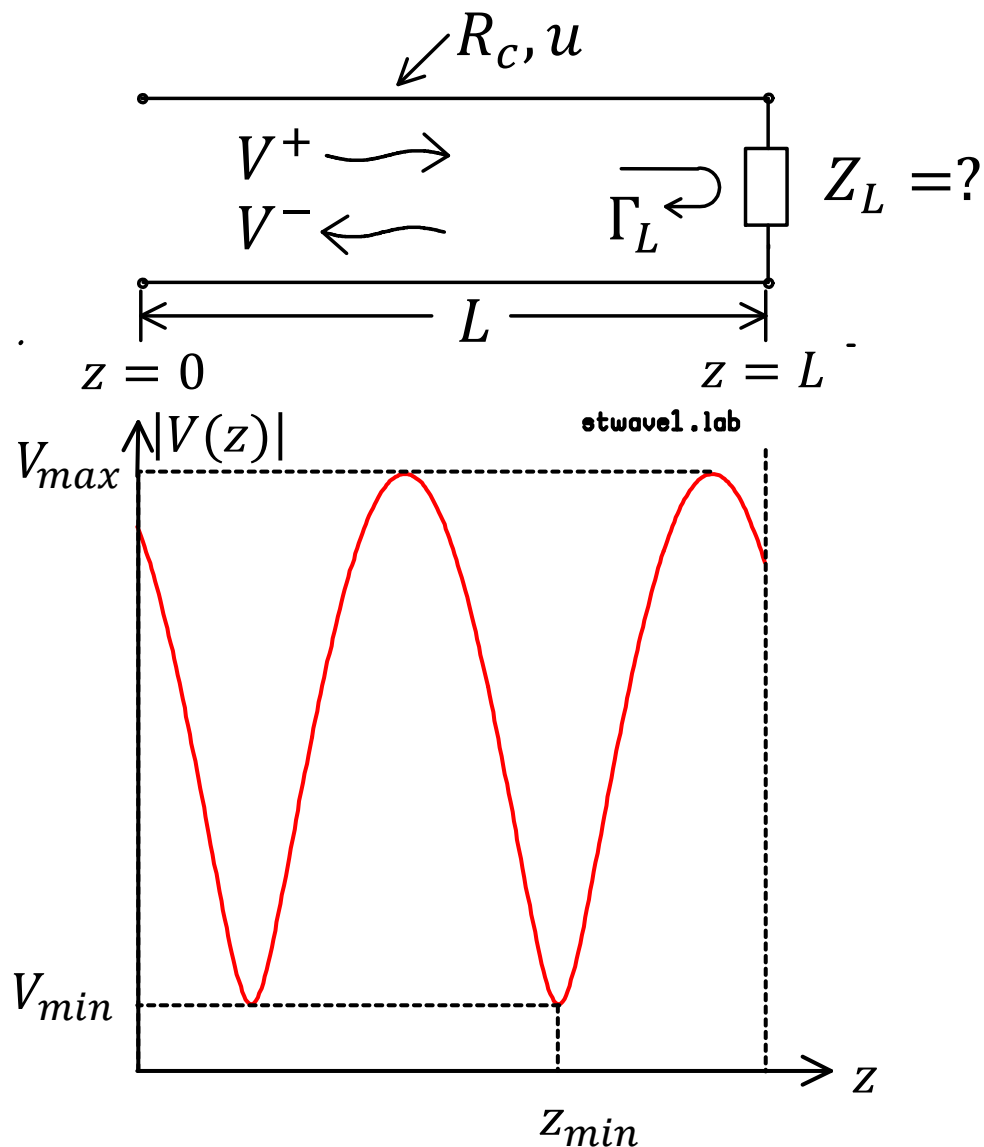Measure the SWR and the location of a minimum, z_{min} .



$$SWR = \frac{V_{max}}{V_{min}}$$

$$SWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$|\Gamma_L| = \frac{SWR - 1}{SWR + 1}$$

$$\phi = 720^\circ \frac{L - z}{\lambda} - 180^\circ$$

then

$$\Gamma_L = |\Gamma_L| \angle \phi$$


Since

$$\Gamma_L = \frac{Z_L - R_c}{Z_L + R_c}$$

then


$$Z_L = \frac{1 + \Gamma_L}{1 - \Gamma_L} R_c$$

Example:

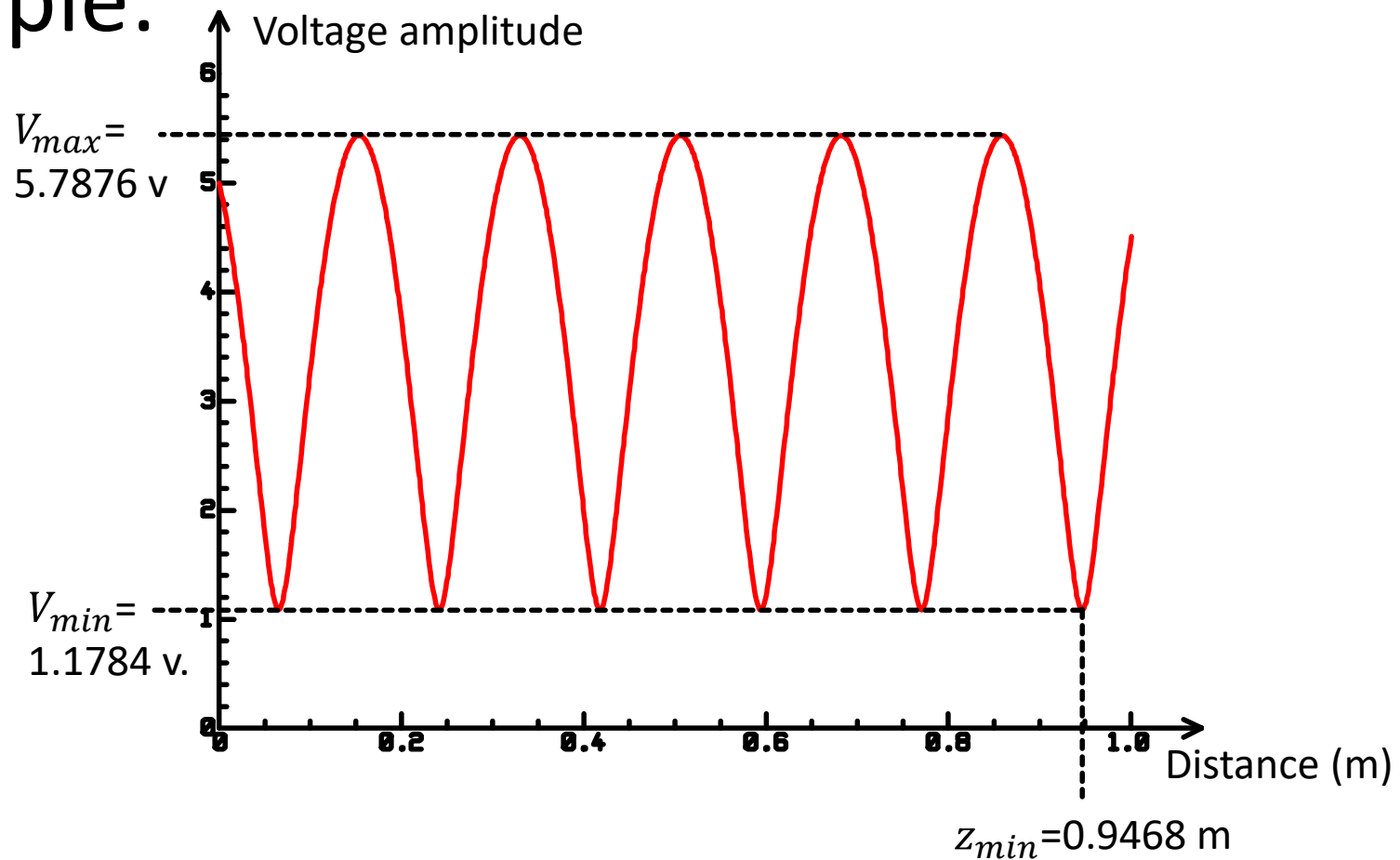

An engineer measures the standing-wave pattern for transmission line terminated with an unknown impedance Z_L . The transmission line has length $L = 1 \text{ m}$, characteristic impedance $Z_0 = 50 \text{ ohms}$ and speed-of-travel $u = 300 \text{ meters per microsecond}$. The frequency is 850 MHz . Find the value of the unknown impedance.

Solution:

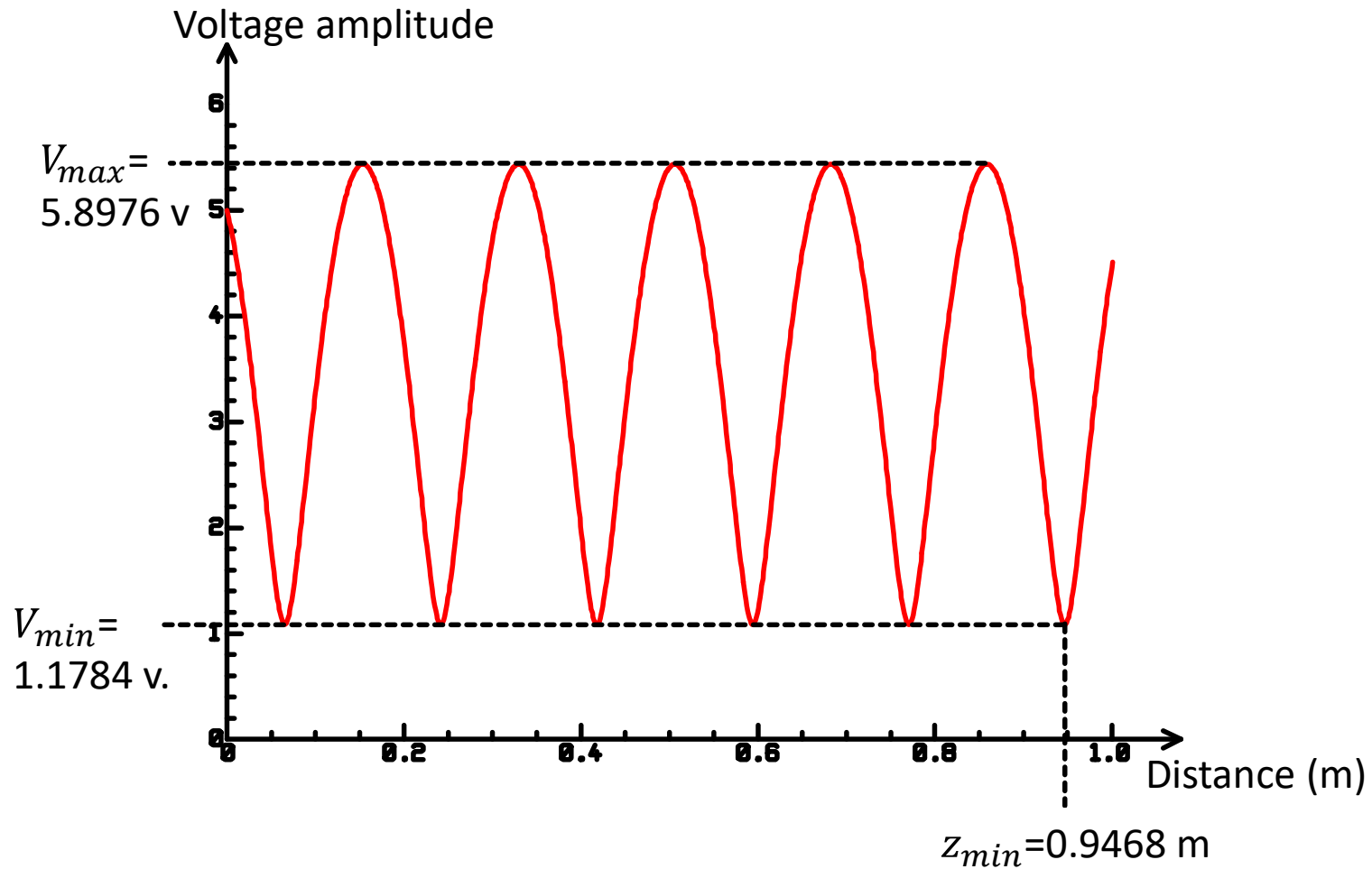

The maximum voltage is $V_{max} = 5.8976 \text{ v}$

The minimum voltage is $V_{min} = 1.1784 \text{ v}$

The location of the minimum is $z_{min} = 0.9468 \text{ m}$

The load is at $z = L = 1 \text{ m}$.

Calculate Γ_L and Z_L :

The maximum voltage is $V_{max} = 5.8976$ v

The minimum voltage is $V_{min} = 1.1784$ v

The location of the minimum is $z_{min} = 0.9468$ m

$$SWR = \frac{V_{max}}{V_{min}} = \frac{5.8974}{1.1784} = 5.005$$

$$|\Gamma_L| = \frac{SWR - 1}{SWR + 1} = \frac{5.005 - 1}{5.005 + 1} = 0.66694$$


$$\lambda = \frac{u}{f} = \frac{300}{850} = 0.35294$$

$$\phi = 720^\circ \frac{L - z}{\lambda} + 180^\circ = 720^\circ \frac{1 - 0.9468}{0.35294} - 180^\circ = -71.2^\circ$$

$$\Gamma_L = |\Gamma_L| e^{j\phi} = 0.66694 \angle -71.2^\circ$$



$$Z_L = \frac{1 + \Gamma_L}{1 - \Gamma_L} R_c = 50 \frac{1 + 0.66694 \angle -71.2^\circ}{1 - 0.66694 \angle -71.2^\circ} = 27.35 - j62.21 \Omega$$

Vector Network Analyzer (VNA)

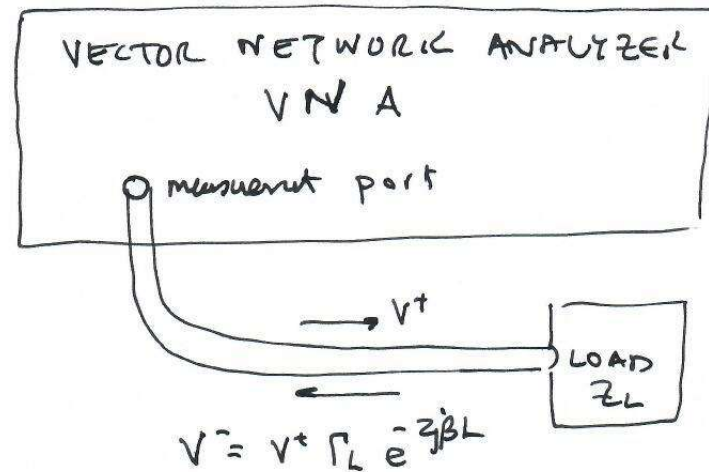

$$\begin{aligned} V^+ &= A^+ \angle \theta^+ \\ V^- &= V^+ \Gamma_L e^{-2j\beta L} \\ &= A^+ \angle \theta^+ |\Gamma_L| e^{j\phi} e^{-2j\beta L} \\ &= A^+ |\Gamma_L| \angle (\theta^+ + \phi - 2\beta L) \end{aligned}$$

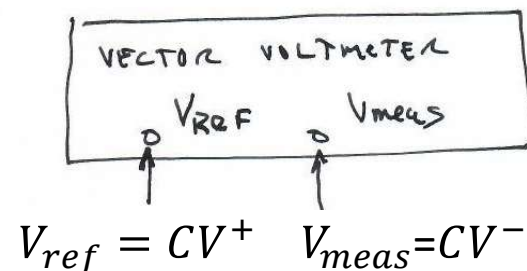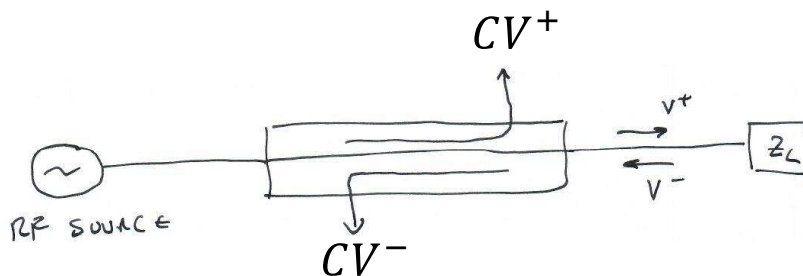What is in the VNA box? Answer: a directional coupler plus a vector voltmeter.



Directional Coupler

C = coupling factor of the directional coupler

CV^+ goes to V_{ref}

CV^- goes to V_{meas}

$$\begin{aligned} \left| \frac{V_{meas}}{V_{ref}} \right| &= \left| \frac{CV^-}{CV^+} \right| = \left| \frac{V^-}{V^+} \right| = |\Gamma_L| \\ \angle V_{meas} - \angle V_{ref} &= (\theta^+ + \phi - 2\beta L) - \theta^+ \\ &= \phi - 2\beta L \end{aligned}$$