

ELEC353 Lecture Notes Set 4

The homework assignments are posted on the course web site.

Homework #2: Do this assignment by January 25nd, 2019.

Homework #3: Do homework #3 by February 1, 2019.

Homework #4: Do homework #4 by February 8, 2019.

Mid-term test: Thursday February 14, 2019.

The course web site is:

www.ece.concordia.ca/~trueman/web_page_353.htm

The course outline

The lecture notes

The homework assignments and solutions


Practice problems

Past midterm tests.

Software: BOUNCE, TRLINE

Review: Analysis of Transmission Lines


Inan, Inan and Said Section 2.2.2

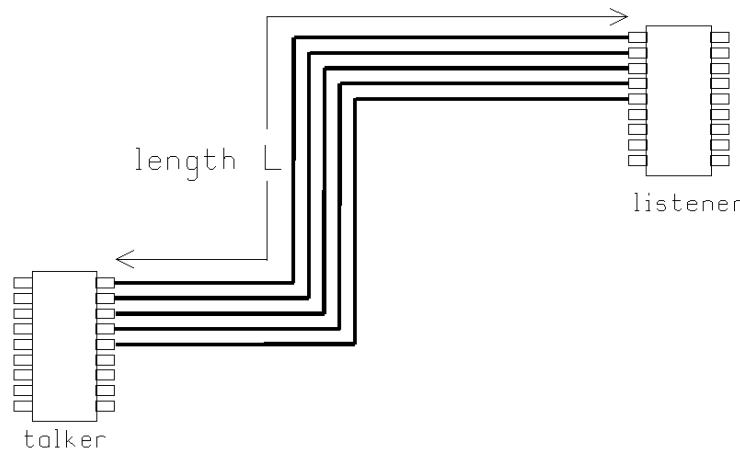

$$\frac{\partial V}{\partial z} = -\ell \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial z} = -c \frac{\partial V}{\partial t}$$
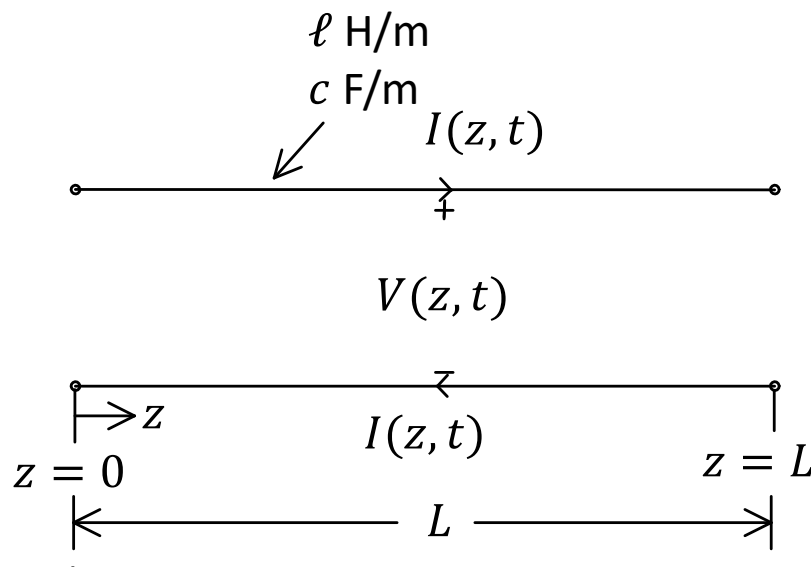
$$\frac{\partial^2 V}{\partial z^2} = \frac{1}{u^2} \frac{\partial^2 V}{\partial t^2}$$




$$V(z, t) = f^+\left(t - \frac{z}{u}\right) + f^-\left(t + \frac{z}{u}\right)$$

$$I(z, t) = \frac{1}{R_e} f^+\left(t - \frac{z}{u}\right) - \frac{1}{R_e} f^-\left(t + \frac{z}{u}\right)$$

$$u = \frac{1}{\sqrt{\ell c}} \text{ m/s}$$

$$R_e = \sqrt{\frac{\ell}{c}}$$

Transmission Line Driven by a Generator

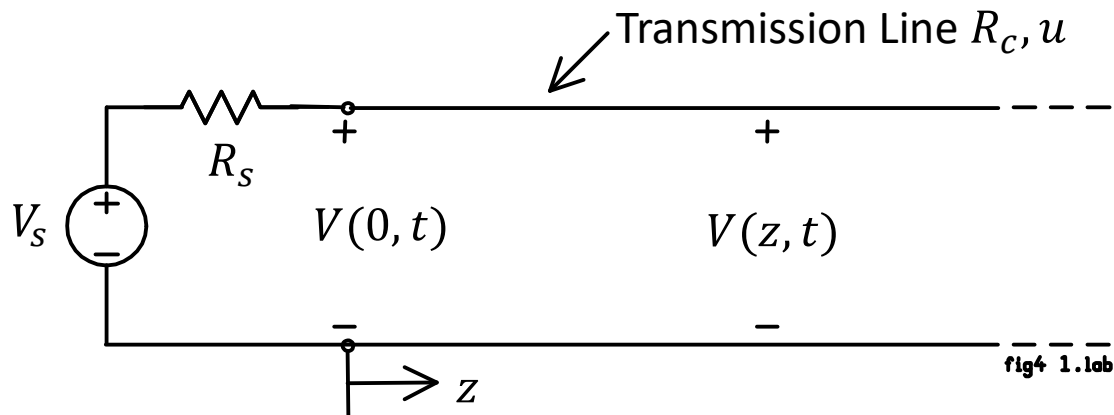

$$V(z, t) = f^+\left(t - \frac{z}{u}\right) + f^-\left(t + \frac{z}{u}\right)$$

$$I(z, t) = \frac{1}{R_c} f^+\left(t - \frac{z}{u}\right) - \frac{1}{R_c} f^-\left(t + \frac{z}{u}\right)$$

There is no reflected wave, so $f^- = 0$

$$V(z, t) = f^+\left(t - \frac{z}{u}\right)$$

$$I(z, t) = \frac{1}{R_c} f^+\left(t - \frac{z}{u}\right)$$

at the generator terminals at $z = 0$

$$\left. \begin{aligned} V(0, t) &= f^+(t) \\ I(0, t) &= \frac{1}{R_c} f^+(t) \end{aligned} \right\} R_{input} = \frac{V(0, t)}{I(0, t)} = R_c$$


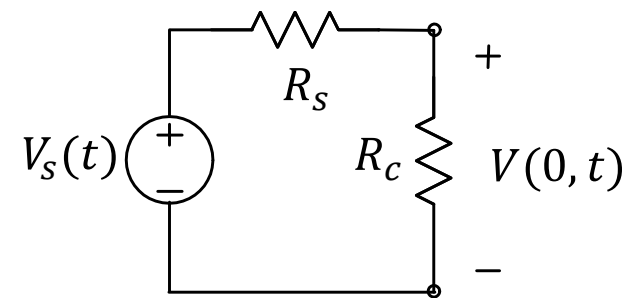



fig4 2.1ab

$$V(0, t) = \frac{R_c}{R_c + R_s} V_s(t)$$

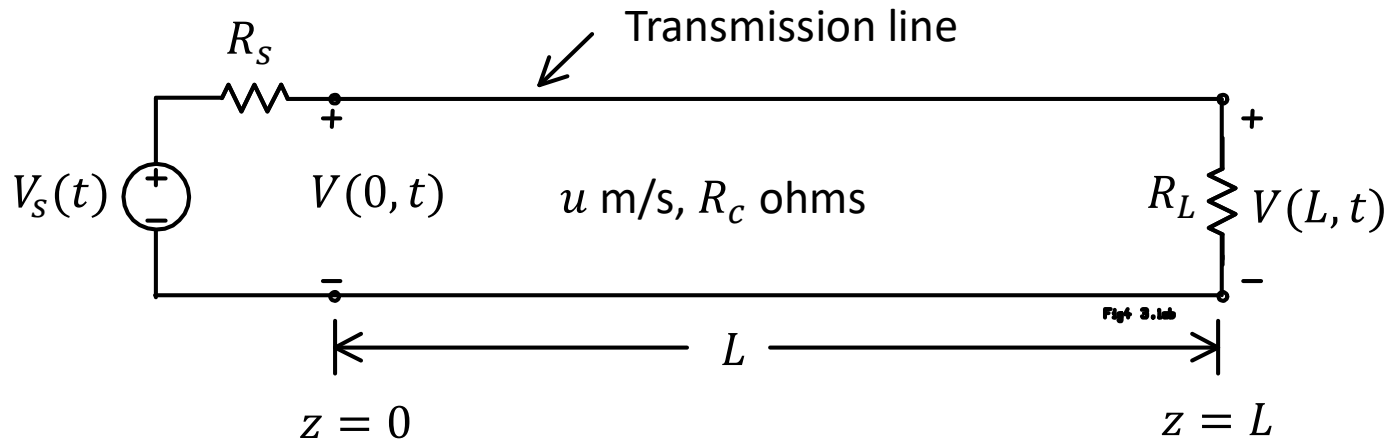Transmission Line Terminated with a Resistor



The Reflection Coefficient at the Load

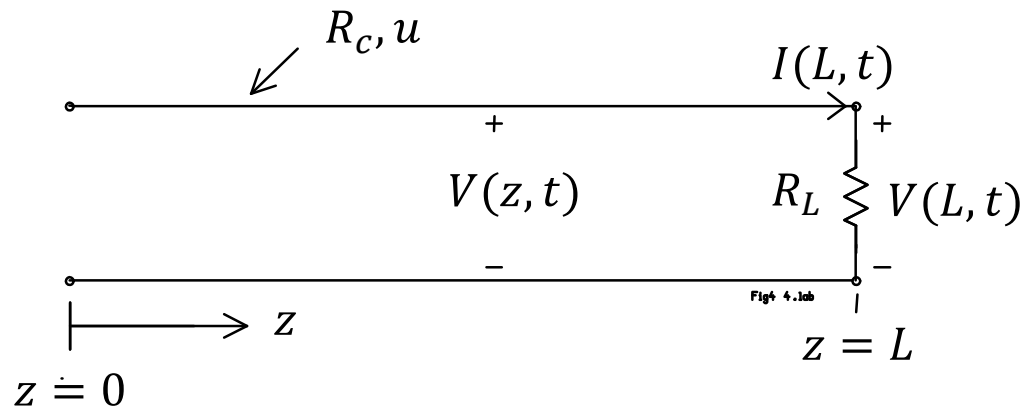

$$V^+(z,t) = f^+\left(t - \frac{z}{u}\right)$$

$$V^-(z,t) = f^-\left(t + \frac{z}{u}\right)$$

Simplify the notation

$$V(z,t) = f^+\left(t - \frac{z}{u}\right) + f^-\left(t + \frac{z}{u}\right)$$




$$V(z,t) = V^+(z,t) + V^-(z,t)$$


$$I(z,t) = \frac{1}{R_c} f^+\left(t - \frac{z}{u}\right) - \frac{1}{R_c} f^-\left(t + \frac{z}{u}\right)$$


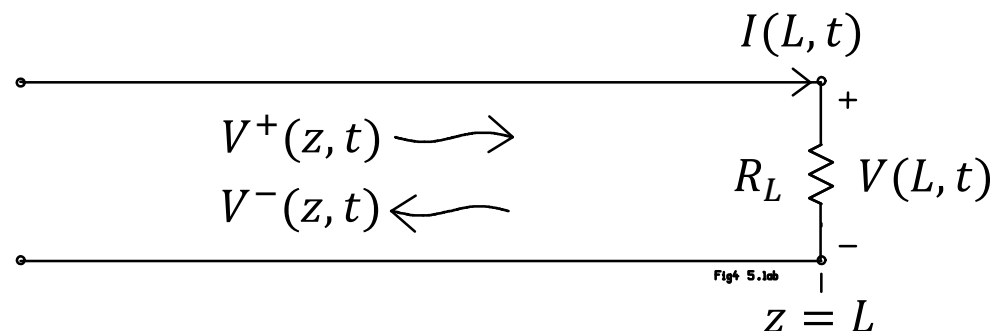
$$I(z,t) = \frac{1}{R_c} V^+(z,t) - \frac{1}{R_c} V^-(z,t)$$



Reflection from the Load

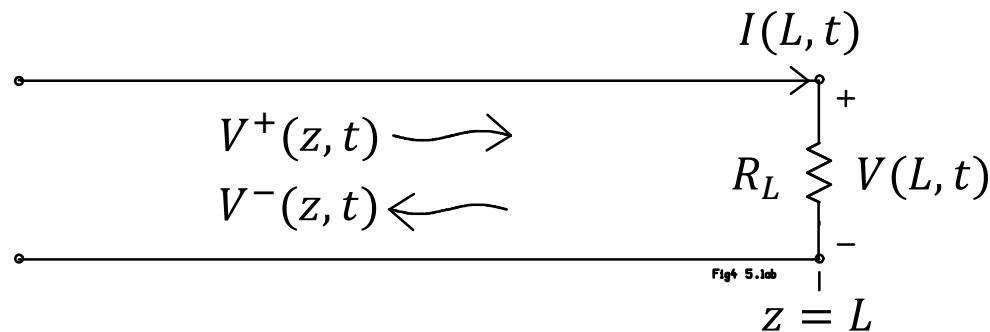

$$V(z, t) = V^+(z, t) + V^-(z, t)$$

$$I(z, t) = \frac{1}{R_c} V^+(z, t) - \frac{1}{R_c} V^-(z, t)$$

At the load, $z = L$, we must obey Ohm's Law:

$$V(L, t) = R_L I(L, t)$$

$$V^+(L, t) + V^-(L, t) = R_L \left(\frac{V^+(L, t)}{R_c} - \frac{V^-(L, t)}{R_c} \right)$$

Solve for V^- :

$$V^- = \frac{R_L - R_c}{R_L + R_c} V^+$$


Define

"reflection coefficient" Γ :

$$\Gamma = \frac{V^-}{V^+} \quad \Gamma = \frac{R_L - R_c}{R_L + R_c}$$

$$V^- = \Gamma V^+$$

Important Special Cases

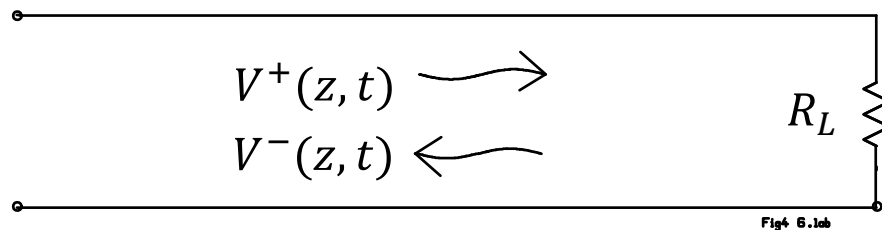

$$\Gamma = \frac{R_L - R_c}{R_L + R_c}$$

$$V^- = \Gamma V^+$$

Matched Load: $R_L = R_c$ so $\Gamma = 0$.

- The “incident” wave is completely absorbed by the load.

$$R_L > R_c, \Gamma = \frac{R_L - R_c}{R_L + R_c} > 0$$

Extreme case:


- If $R_L \rightarrow \infty$, then $\Gamma \rightarrow +1$, so the reflected voltage has the same amplitude as the incident voltage.
- $R_L \rightarrow \infty$ is an open-circuit load, for which $\Gamma \rightarrow +1$.

$$R_L < R_c, \Gamma = \frac{R_L - R_c}{R_L + R_c} < 0$$

Extreme case:


- If $R_L \rightarrow 0$, then $\Gamma \rightarrow -1$, so the reflected voltage is the negative of the incident voltage.
- $R_L \rightarrow 0$ is a short-circuit load, for which $\Gamma \rightarrow -1$.

Solving Transmission-Line Circuits

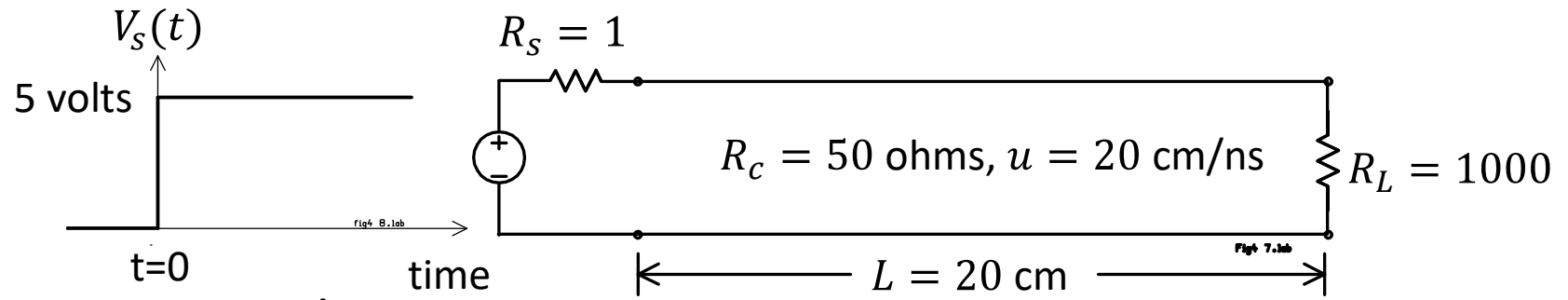

Find the voltage across the load resistor as a function of time.


Values of the coefficients:

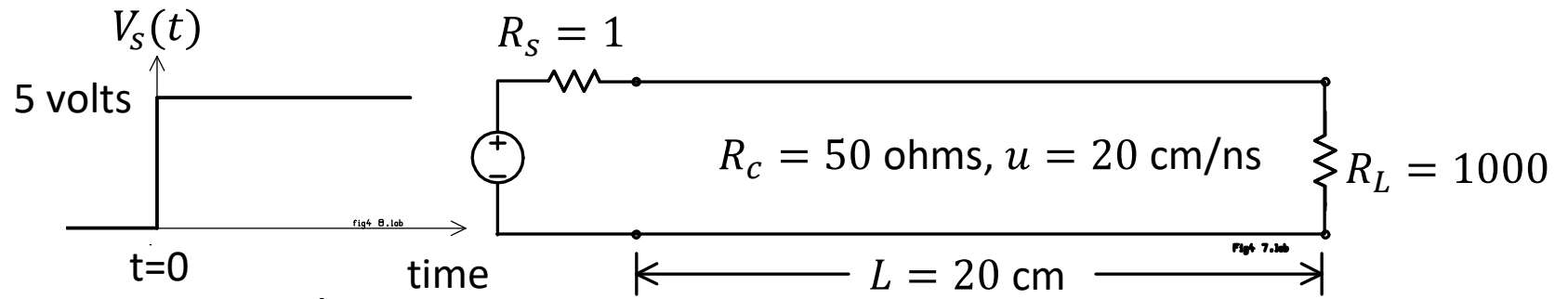

○ Transit time: $T_d = \frac{L}{u} = \frac{20}{20} = 1$ ns.

○ Load reflection coefficient: $\Gamma_L = \frac{R_L - R_c}{R_L + R_c} = \frac{1000 - 50}{1000 + 50} = 0.9047$

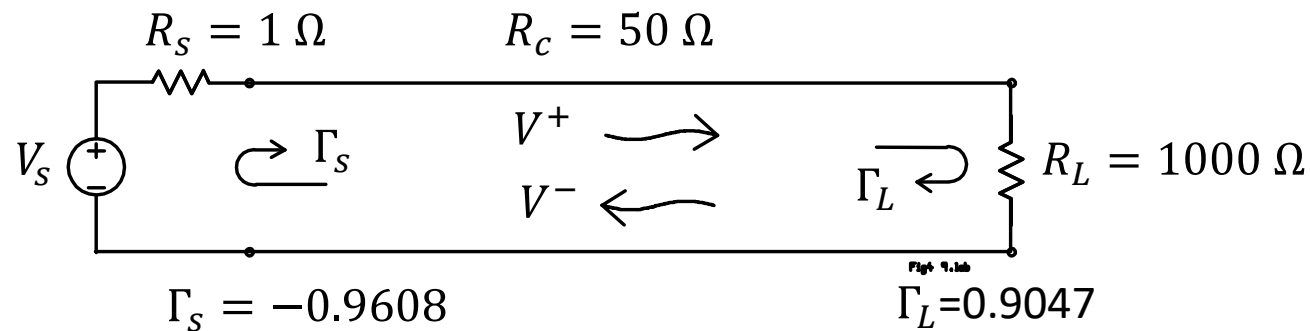○ Source reflection coefficient: $\Gamma_s = \frac{R_s - R_c}{R_s + R_c} = \frac{1 - 50}{1 + 50} = -0.9608$



Initial Step Launched onto the Transmission Line

In general $V(z, t) = V^+(z, t) + V^-(z, t)$

At the generator terminals $V(0, t) = V^+(0, t) + V^-(0, t)$


Before $t = 2T$ when the reflection from the load arrives, $V^-(0, t) = 0$ so

$$V(0, t) = V^+(0, t)$$

So we can find V^+ using


$$V^+(0, t) = V(0, t)$$

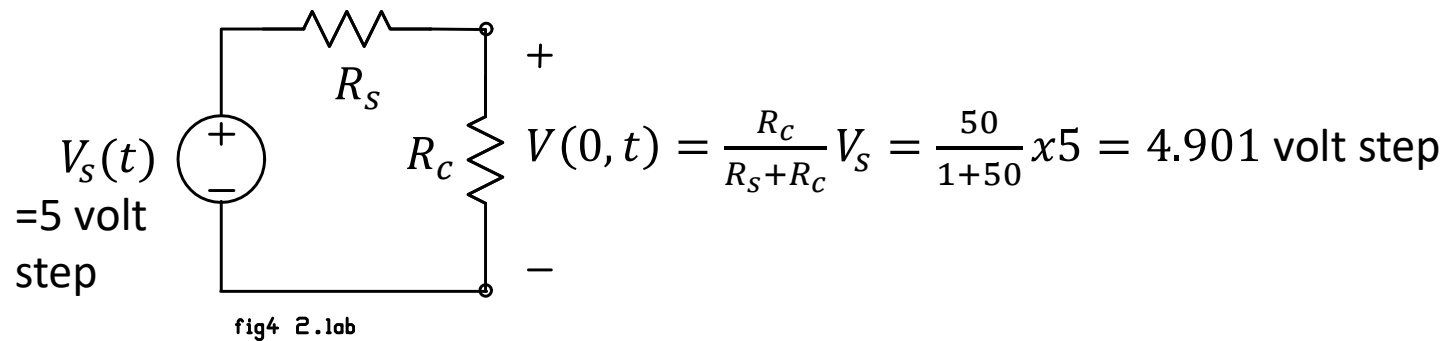The input resistance of the transmission line is R_c .



$$V^+ = V(0, t) = 4.901 \text{ volt step}$$

After one transit time:

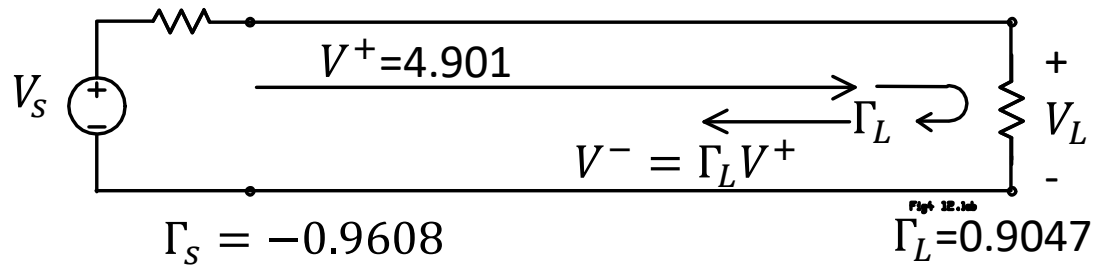


$$V^- = \Gamma_L V^+ = 0.9047 \times 4.901 = 4.434 \text{ volts}$$


The voltage at the load after one transit time is the incident plus the reflected voltage:

$$V(L, t) = V^+(L, t) + V^-(L, t) = 4.901 + 4.434 = 9.335 \text{ volts}$$

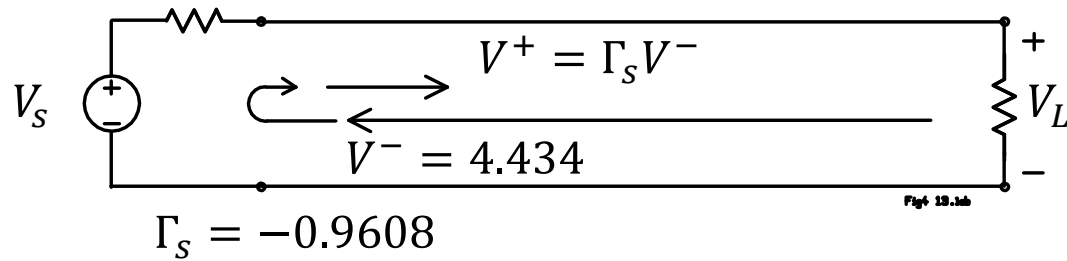At $t = T_d$ the voltage is $4.901 + 4.434 = 9.335$ volts.



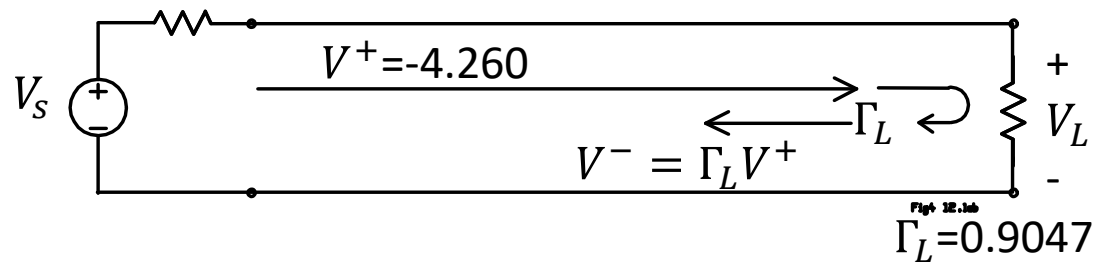After two transit times: $V^+ = \Gamma_S V^- = -0.9608 \times 4.434 = -4.260$ volts



After three transit times: $V^- = \Gamma_L V^+ = 0.9047 \times -4.260 = -3.854$

The voltage at the load after one transit time is the incident plus the reflected voltage:

$$V(L, t) = V^+(L, t) + V^-(L, t)$$


At $t = T_d$ the voltage is $4.901 + 4.434 = 9.335$ volts.

After three transit times, a new incident wave arrives and generates a new reflected wave.



The voltage is the previous value plus the new incident voltage plus the new reflected voltage.

At $t = 3T_d$ the voltage is $9.335 - 4.260 - 3.854 = 1.221$ volts.

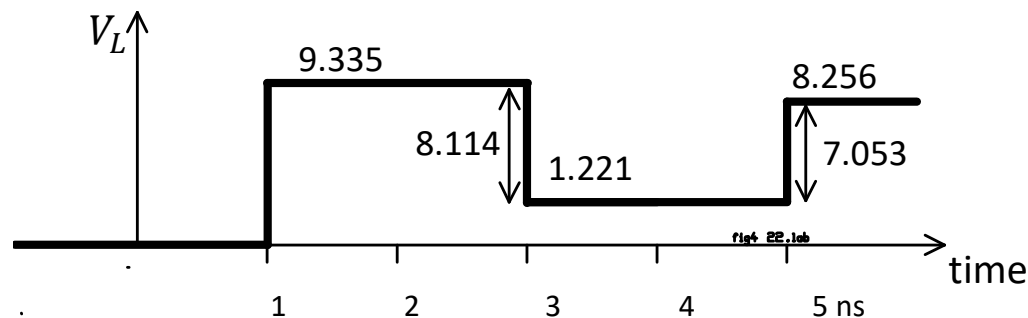Homework: show that at $t = 5T_d$ the voltage is $1.221 + 7.035 = 8.256$ volts




Removing the Reflections:

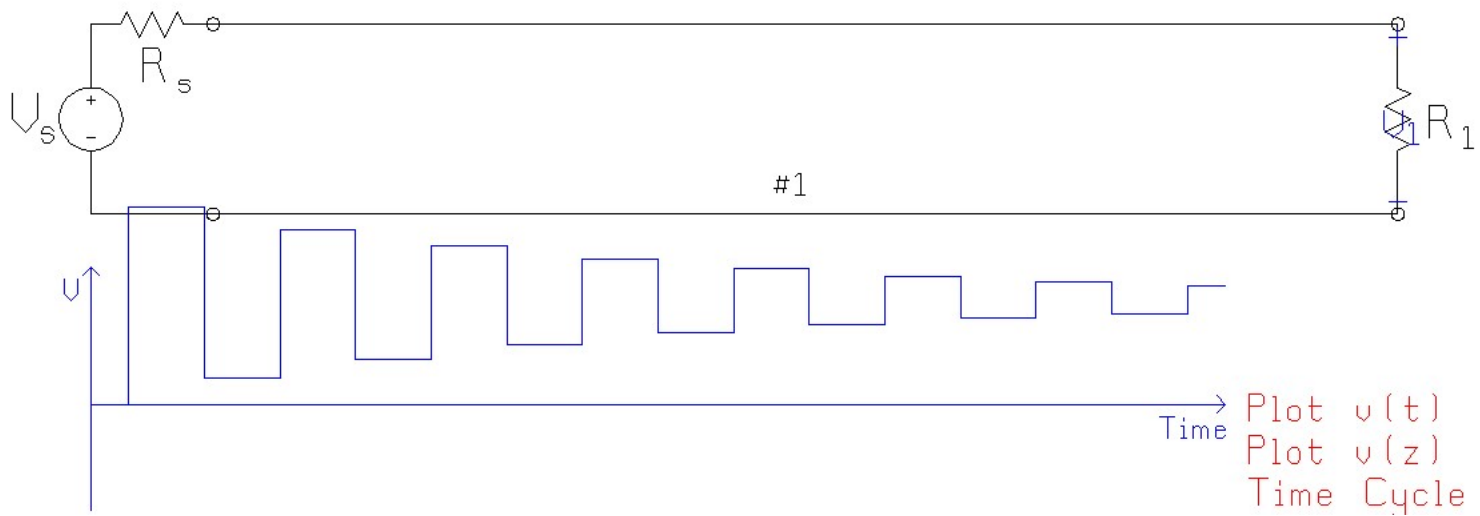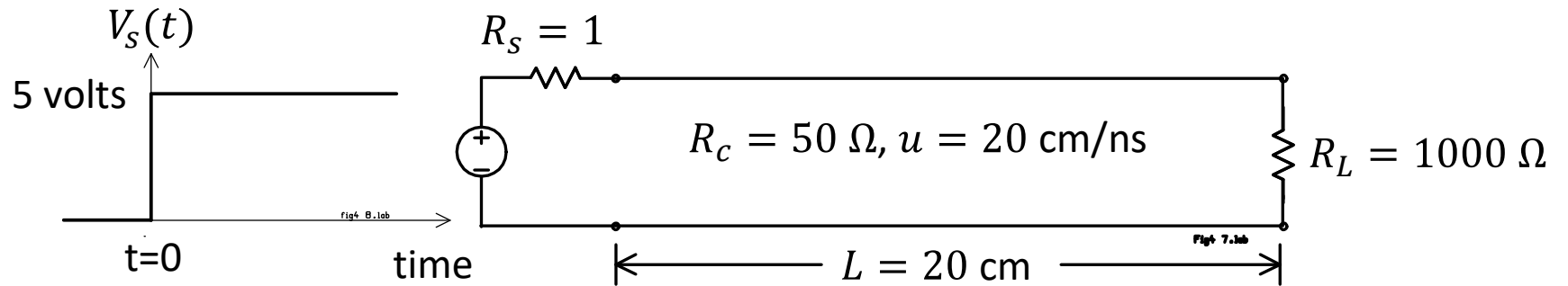


Better match at the source:

$$R_s = 10\Omega$$

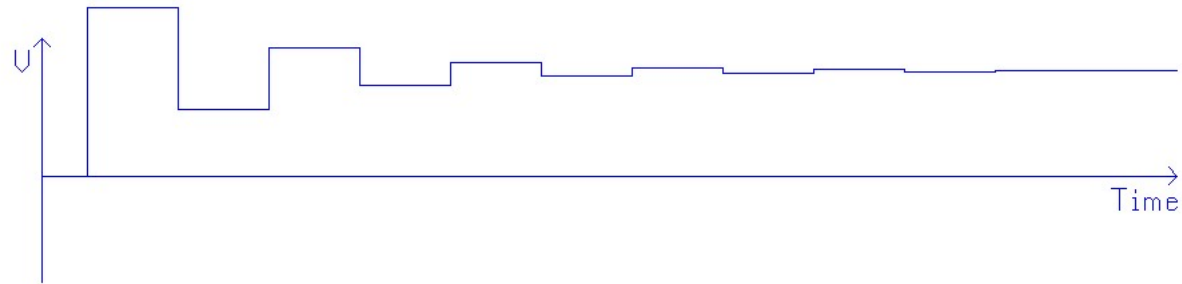

$$R_s = 25\Omega$$

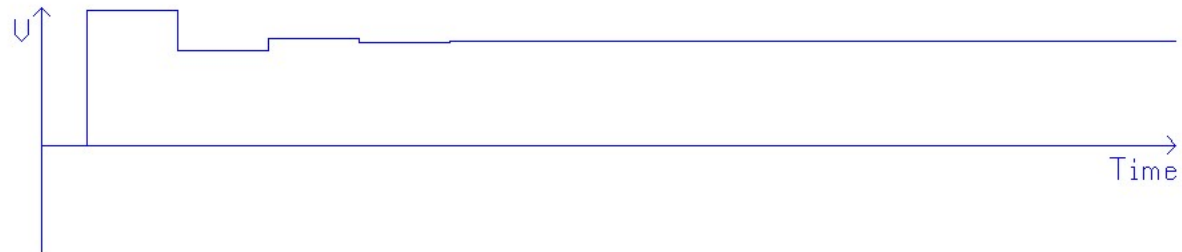


$$R_s = 50\Omega$$




Perfect match!

Better match at the load:

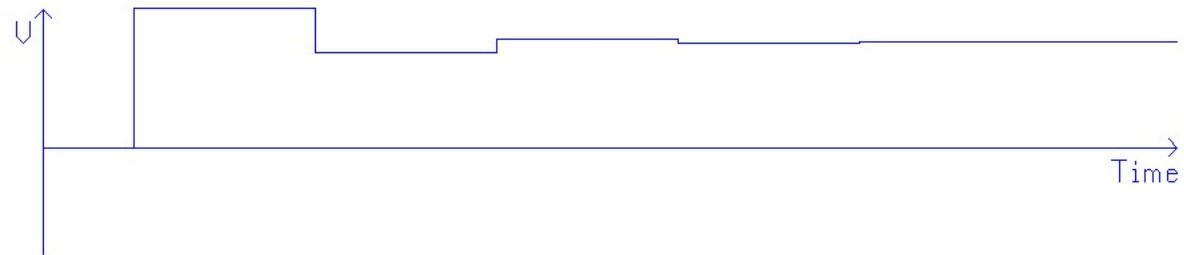


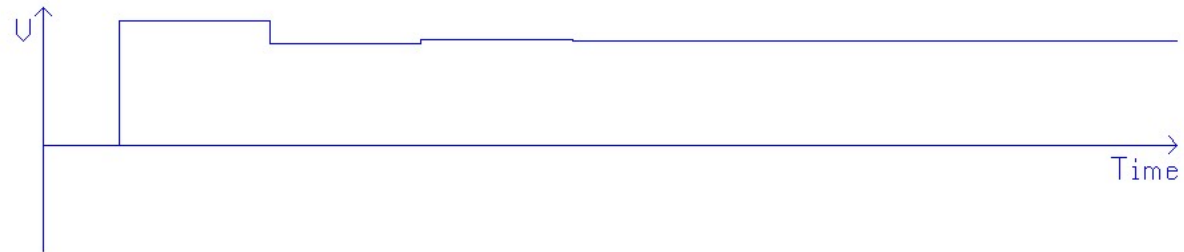$R_s = 1 \text{ ohm}$ and $R_L = 100 \text{ ohms}$



$R_L = 75 \text{ ohms}$


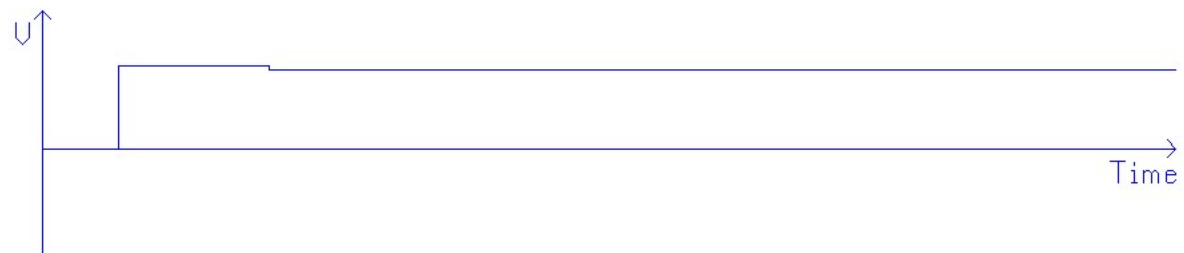
Better match at the generator and at the load:



$R_s = 35 \text{ ohms}$ and $R_L = 100 \text{ ohms}$


There is a small reflection at $3T_d$.

Removing DC Power Dissipation

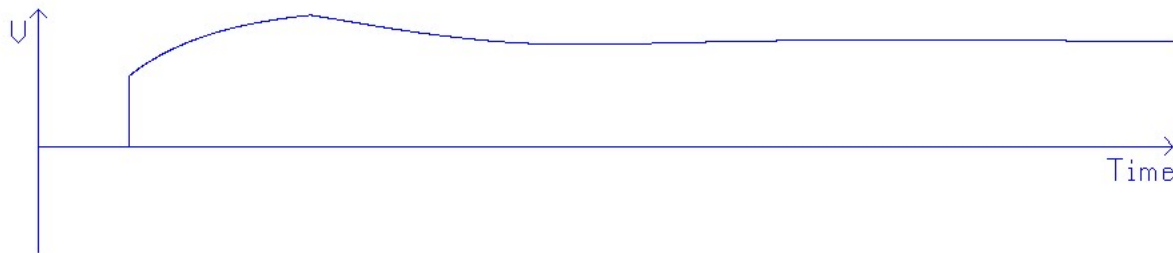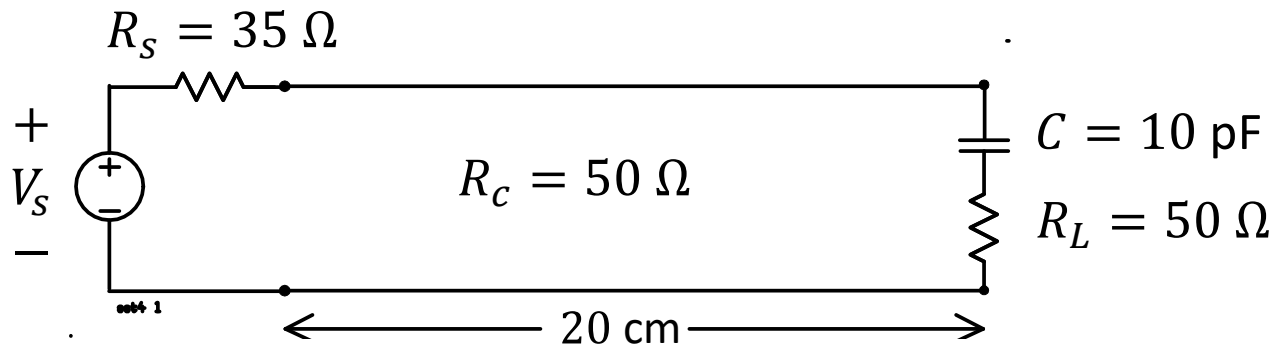


The Bounce Diagram

(Inan and Inan Section 2.3.1)

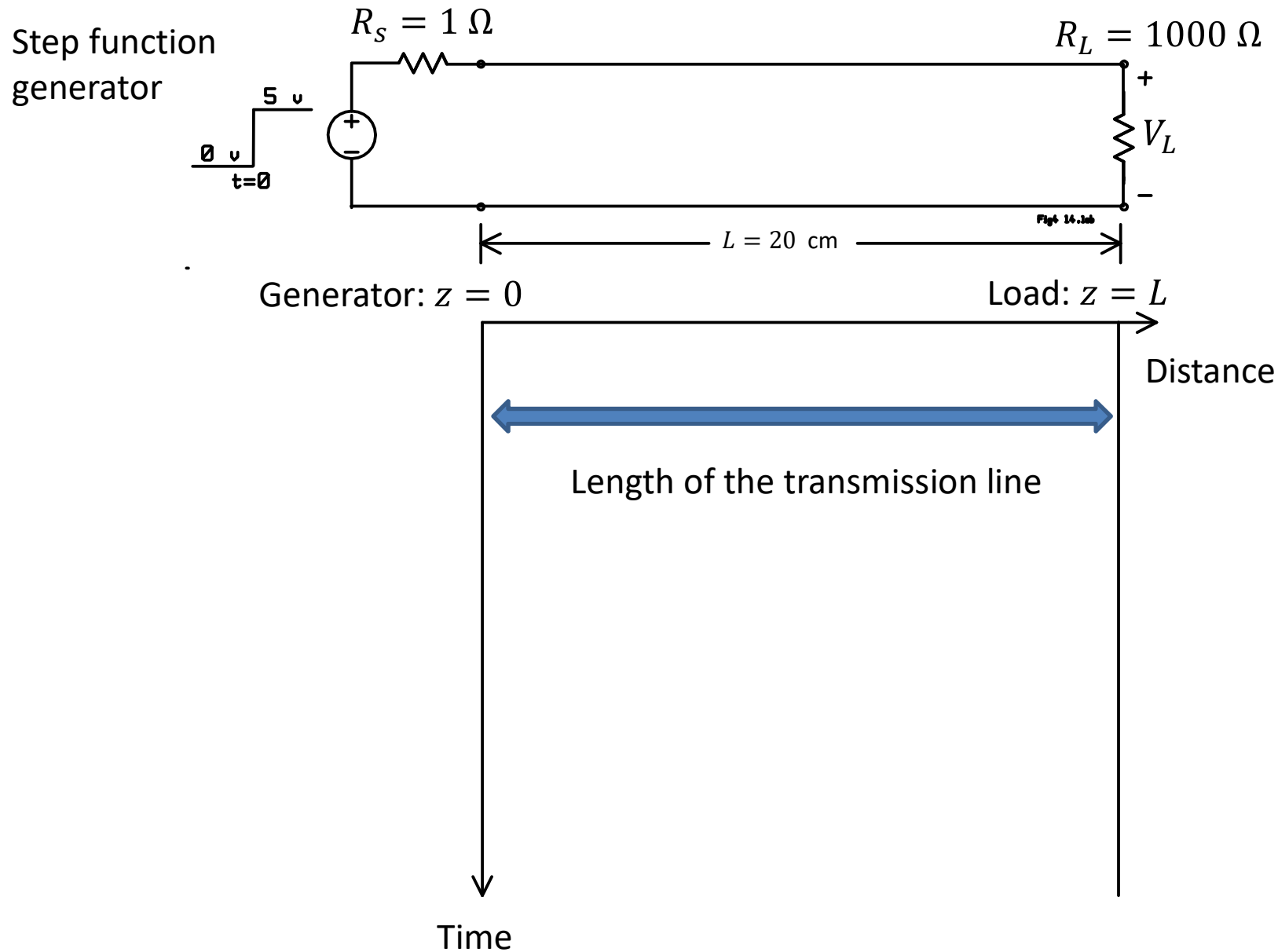

Problem setup:

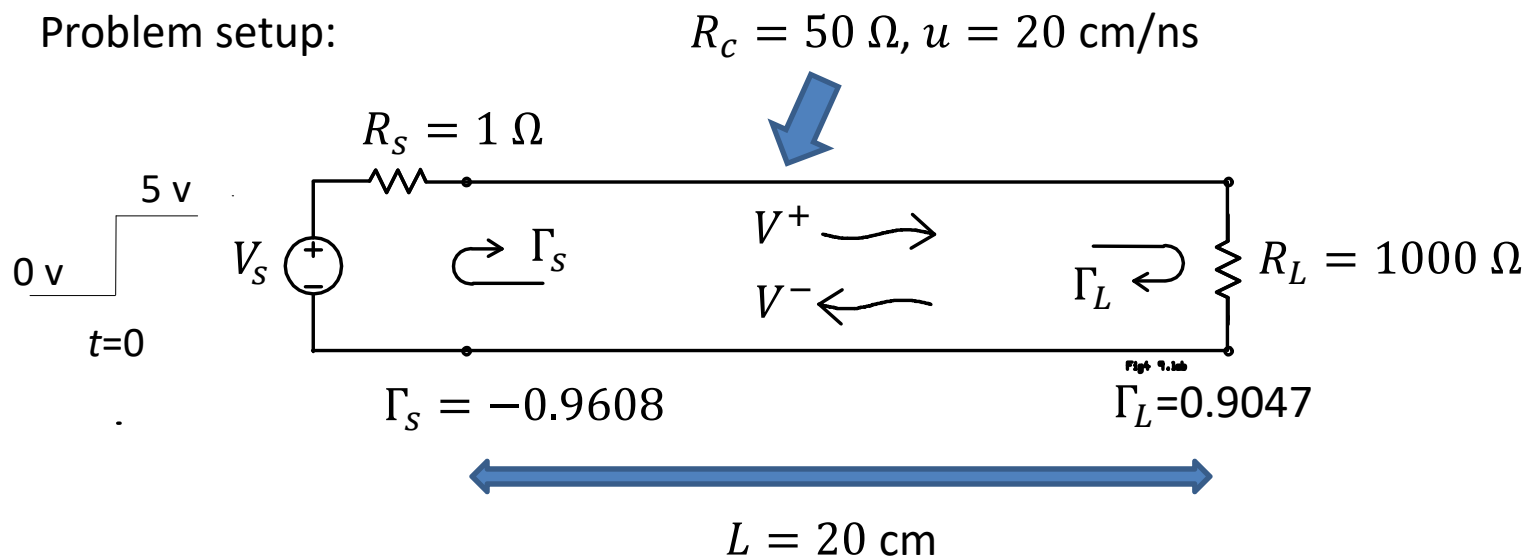




$$T_d = \frac{L}{u} = \frac{20}{20} = 1 \text{ ns}$$

$$V^+ = \frac{R_c}{R_s + R_c} V_s = \frac{50}{50 + 1} \times 5 = 4.901 \text{ volts}$$

$$\text{Load reflection coefficient: } \Gamma_L = \frac{R_L - R_c}{R_L + R_c} = \frac{1000 - 50}{1000 + 50} = 0.9047$$
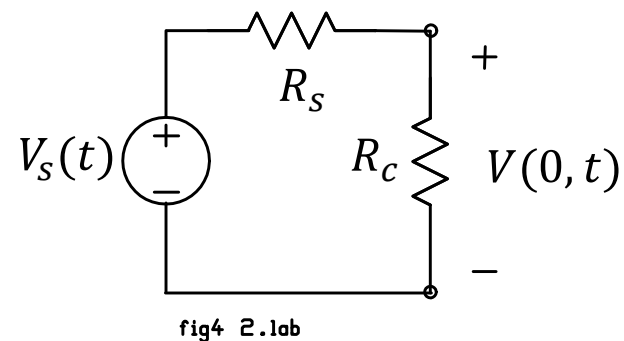
$$\text{Source reflection coefficient: } \Gamma_s = \frac{R_s - R_c}{R_s + R_c} = \frac{1 - 50}{1 + 50} = -0.9608$$



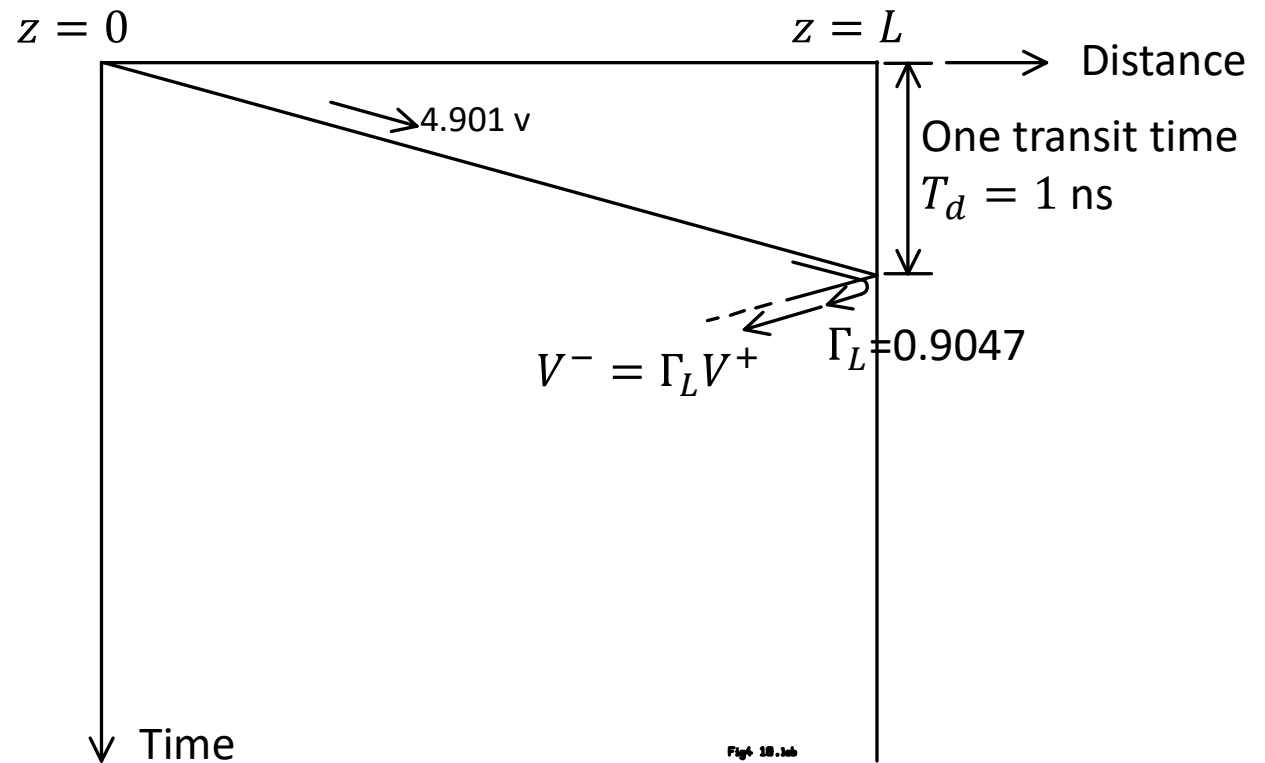
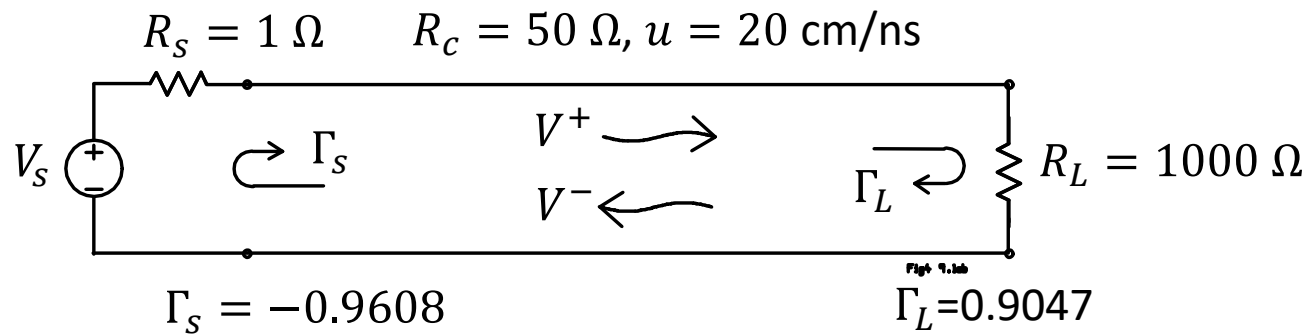


$$V^- = \Gamma_L V^+ = 0.9047 \times 4.901 = 4.434 \text{ v}$$



at the load

$$V(z=L) = V^+(z=L) + V^-(z=L)$$

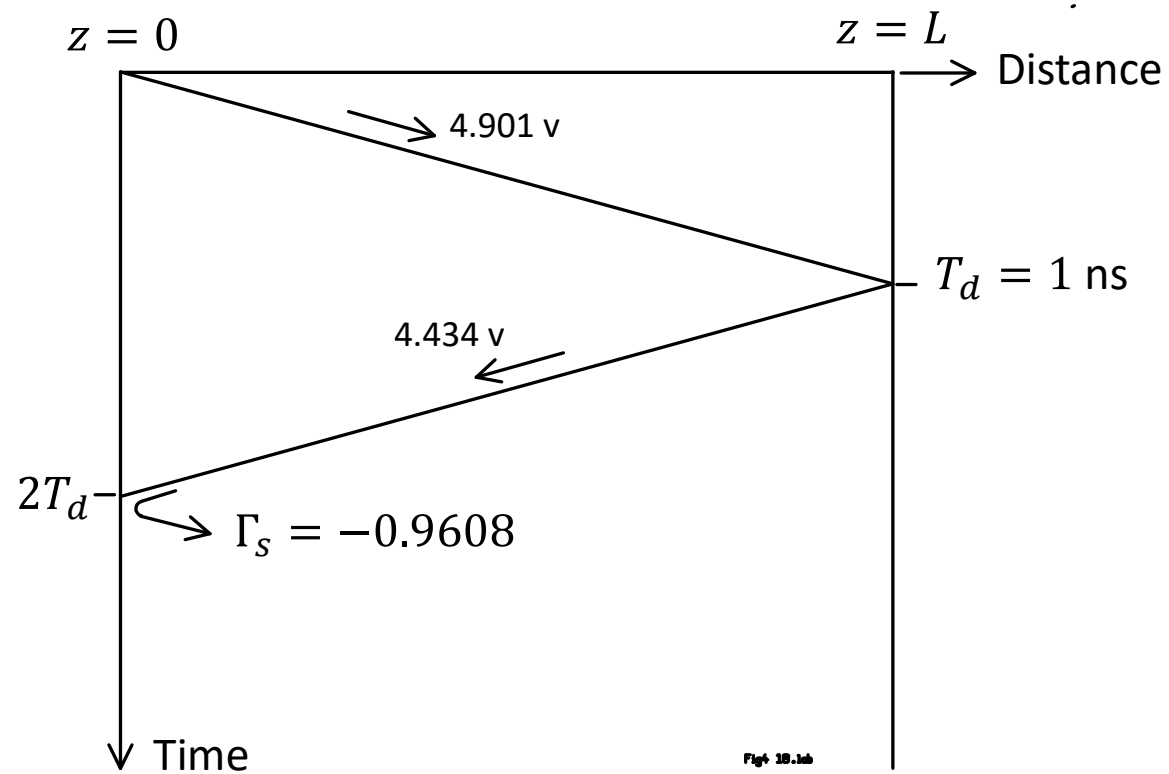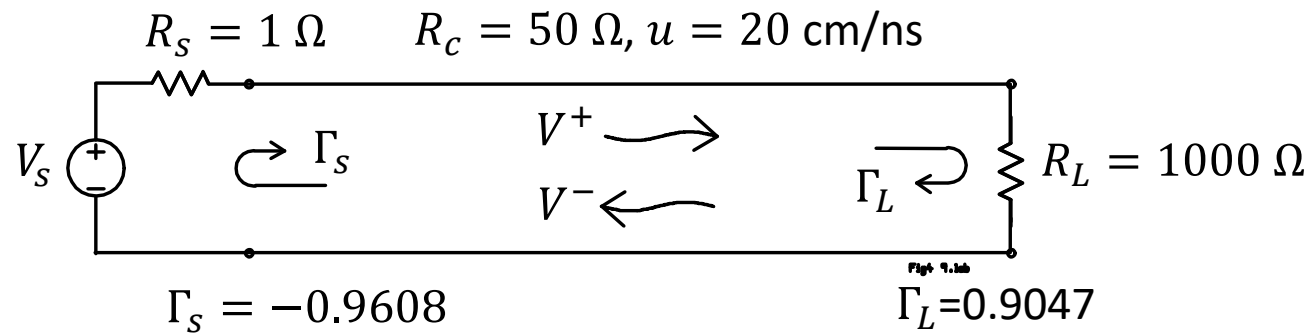
$$V(z=L) = 4.901 + 4.434 = 9.335 \text{ volts}$$


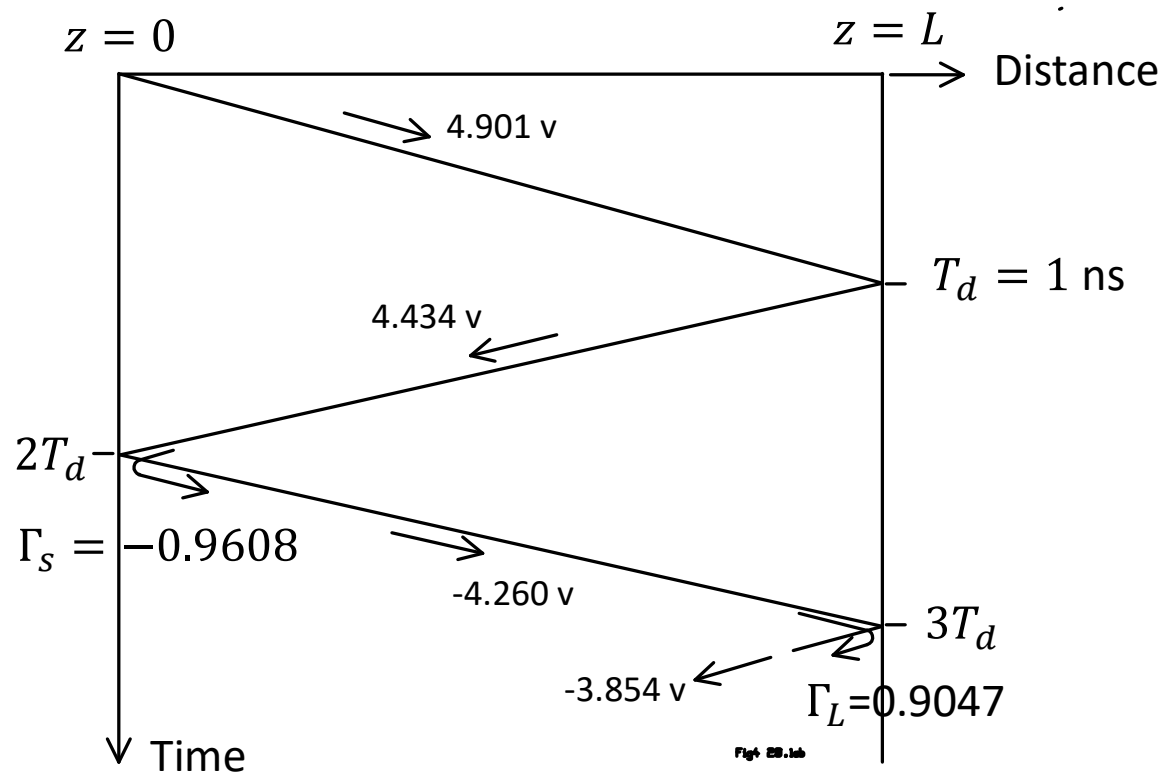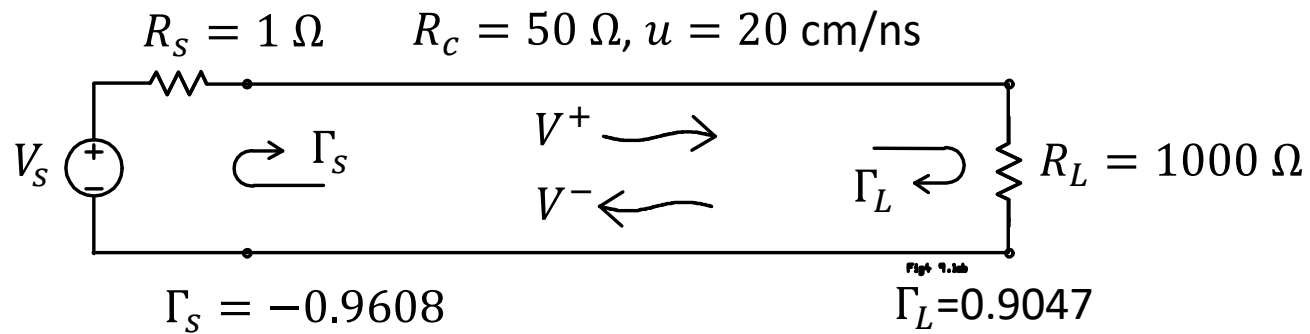
$$V^+ = \Gamma_s V^- = -0.9608 \times 4.434 = -4.260 \, \text{v}$$


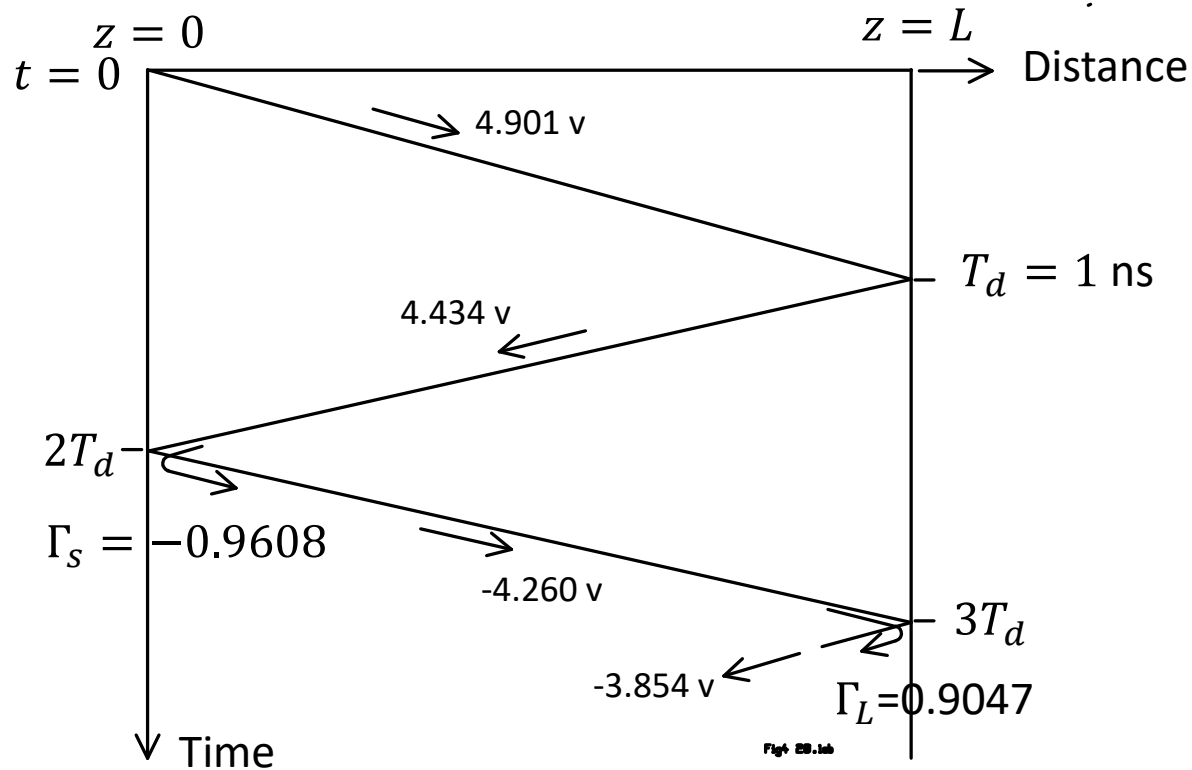
$$V^- = \Gamma_L V^+ = 0.9047x - 4.260 = -3.854 \text{ v}$$



Find the load voltage:

Read the $z = L$ axis downward from $t = 0$ at the top.


From $t=0$ to T_d the voltage at the load is zero.

At $t = T_d$, voltage step $V^+ = 4.901$ arrives, and generates voltage $V^- = 4.434$ volts, so the load voltage steps up to $4.901 + 4.434 = 9.335$ volts.

From $t = T_d$ to $t = 3T_d$ the voltage at the load is constant at 9.335 volts.

At $t = 3T_d$, voltage step $V^+ = -4.260$ volts arrives, and generates voltage step $V^- = -3.854$ volts, and the net CHANGE is $V^+ + V^- = (-4.260) + (-3.854) = -8.114$ volts.

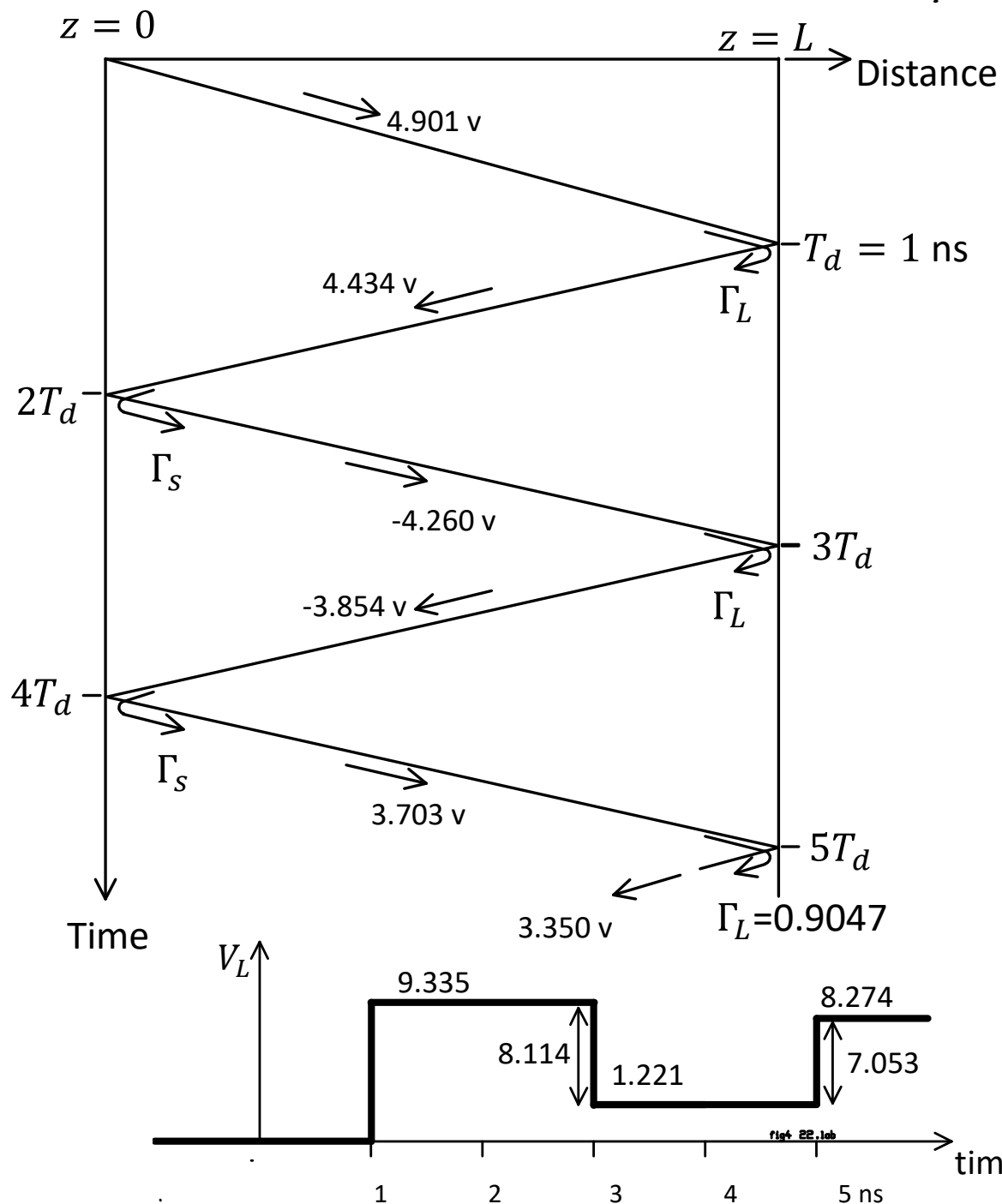So the load voltage changes to $9.335 - 8.114 = 1.221$ volts.



At $T_d = 1 \text{ ns}$

$$V(z = L) = 4.901 + 4.434 = 9.335$$

At $3T_d$:

The change is

$$-4.260 - 3.854 = -8.114 \text{ volts}$$

The load voltage is

$$9.335 - 8.114 = 1.221 \text{ volts}$$

At $5T_d$:


The change is

$$3.703 + 3.350 = 7.053 \text{ volts}$$


The load voltage is

$$1.221 + 7.053 = 8.274 \text{ volts}$$


Response to a Pulse Function

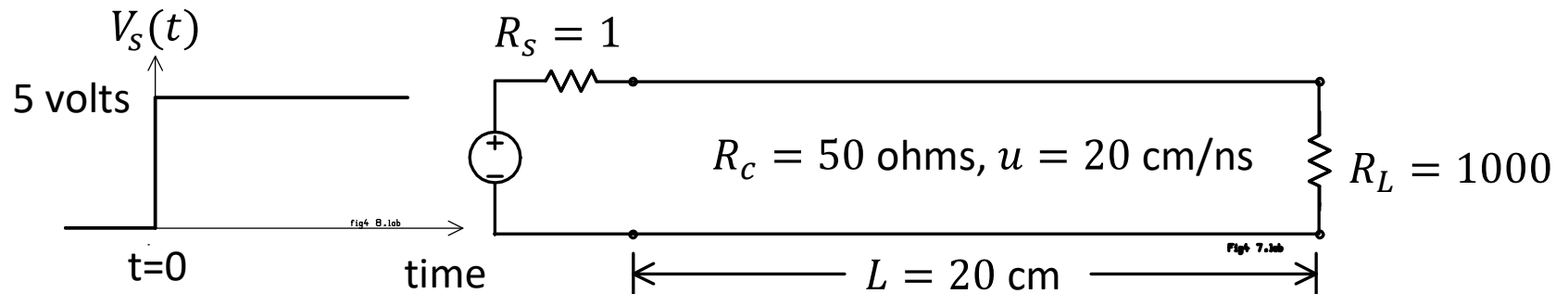

We calculated the step response:

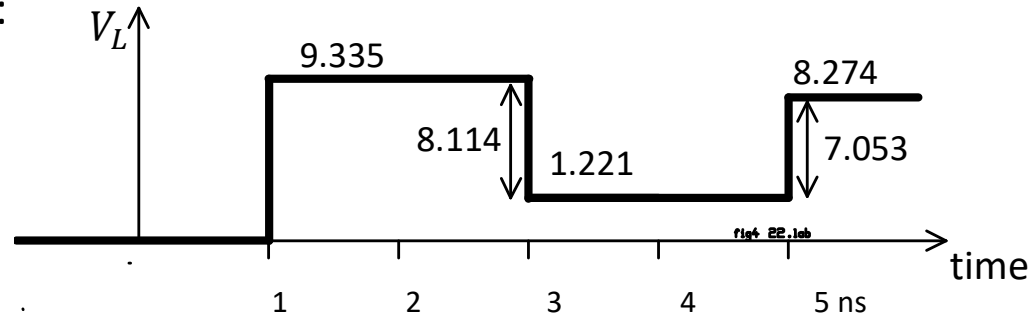


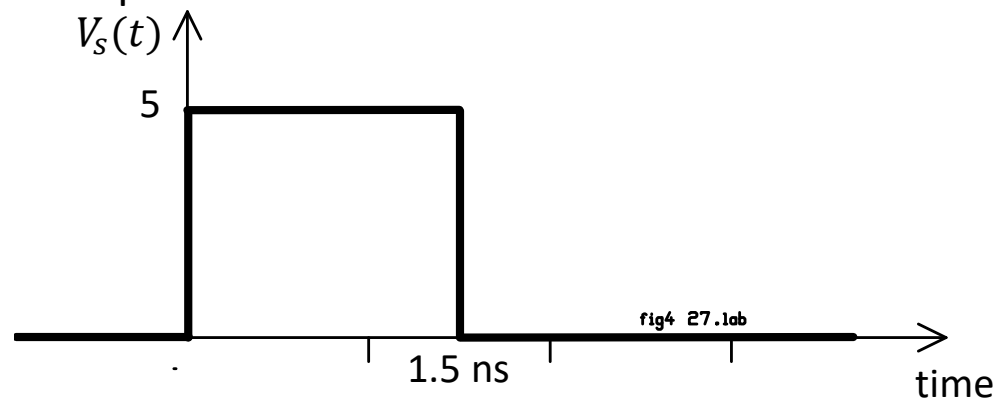How do we calculate response to a pulse excitation?



$$V_s(t) = 5u(t) - 5u(t - 1.5)$$

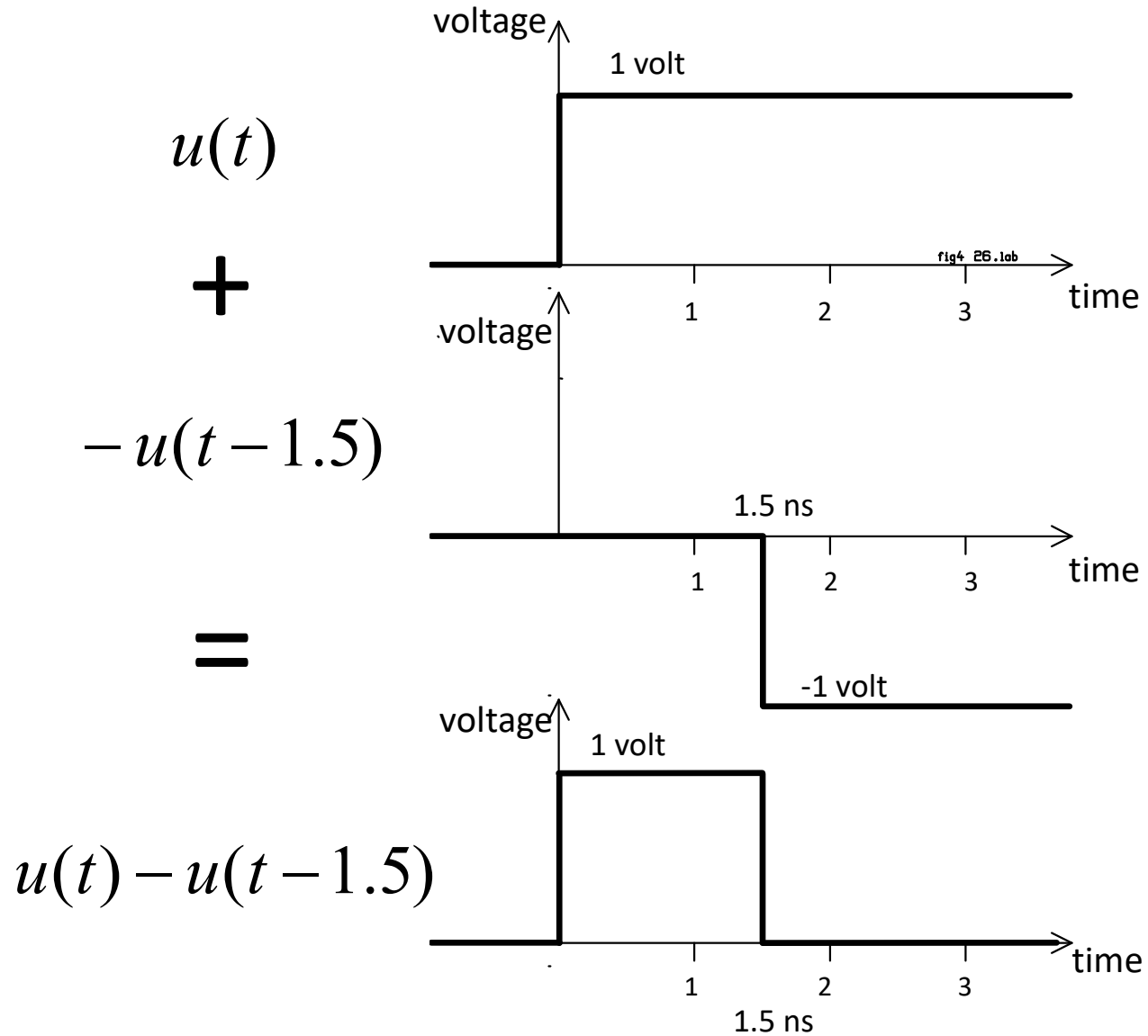Construct a unit pulse excitation from two step functions:



Construct the Pulse Response from the Step Response

The response to a unit step function $u(t)$ is $V_{step}(t)$

The response to $u(t-1.5)$ is $V_{step}(t-1.5)$

The response to a unit pulse function $(u(t) - u(t-1.5))$ is $(V_{step}(t) - V_{step}(t-1.5))$




The response to $5u(t) - 5u(t-1.5)$ is $5V_{step}(t) - 5V_{step}(t-1.5)$

So the response to the pulse $5(u(t) - u(t-1.5))$ is

$$V_{pulse}(t) = 5[V_{step}(t) - V_{step}(t-1.5)]$$

We can use this formula as a recipe for constructing the pulse response.

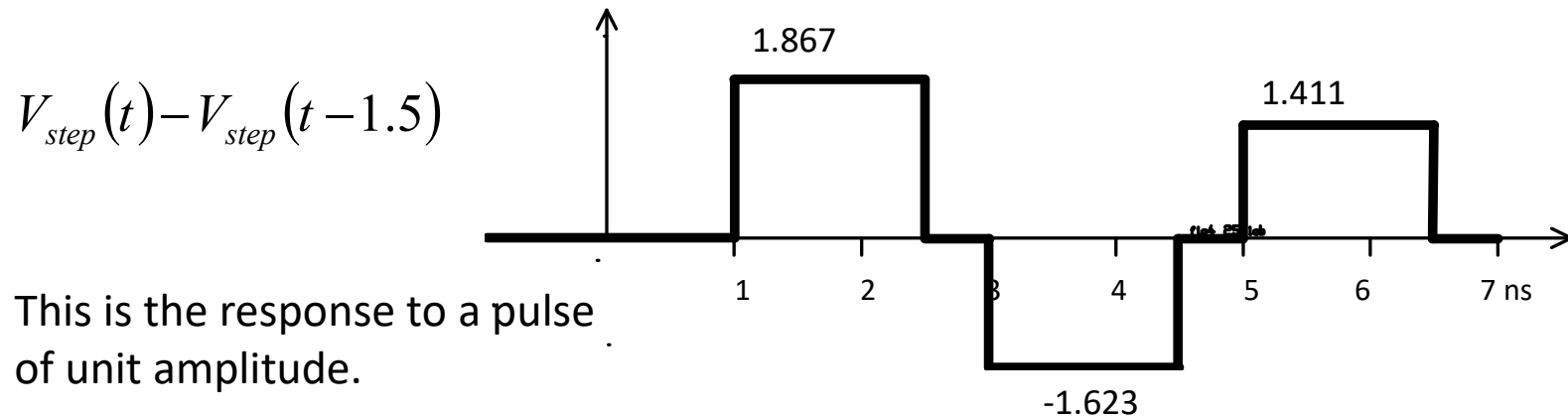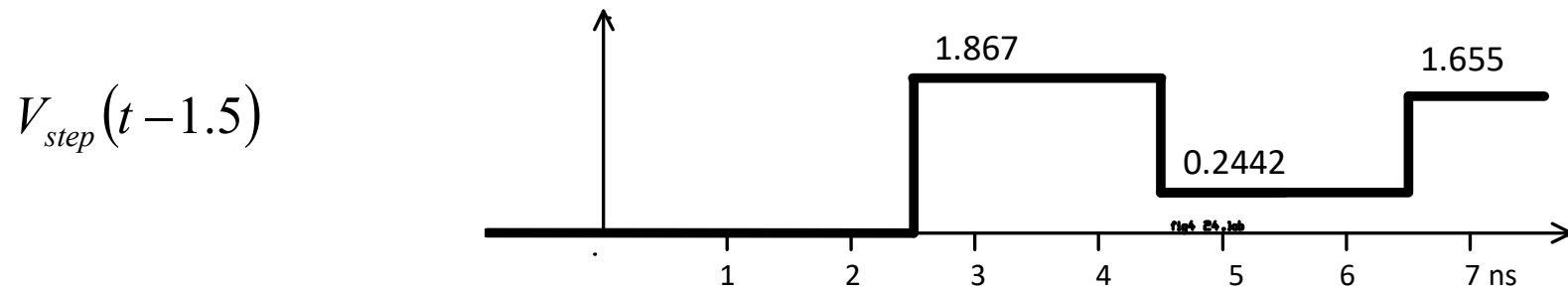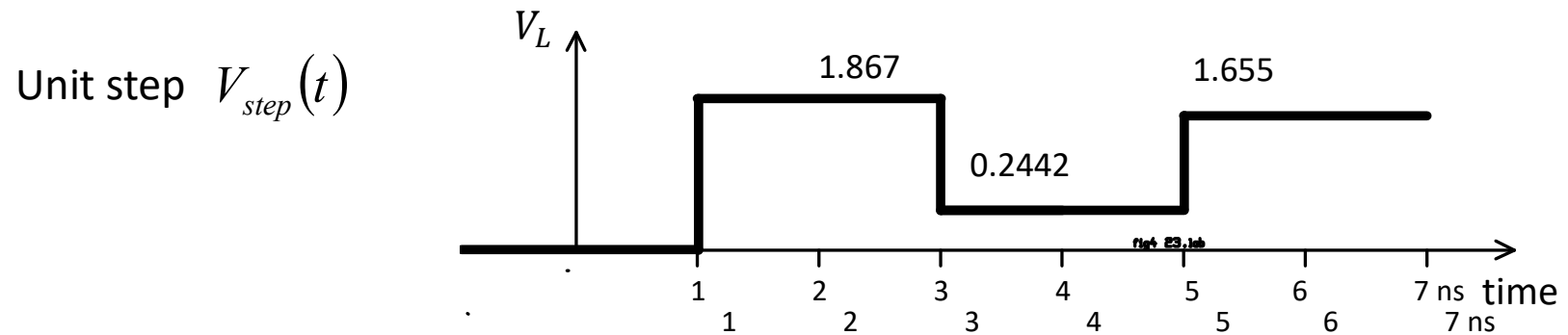
Construct the pulse response: $V_{pulse}(t) = 5[V_{step}(t) - V_{step}(t - 1.5)]$



Multiply the unit pulse response by five: $V_{pulse}(t) = 5[V_{step}(t) - V_{step}(t - 1.5)]$


Unit pulse response:

$$V_{step}(t) - V_{step}(t - 1.5)$$

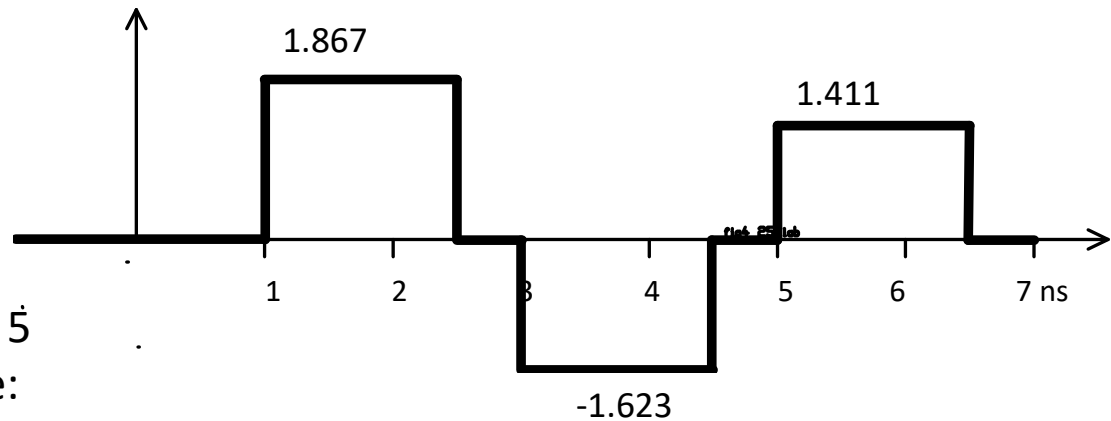



Multiply the unit pulse response by 5 to get the response to a 5 volt pulse:

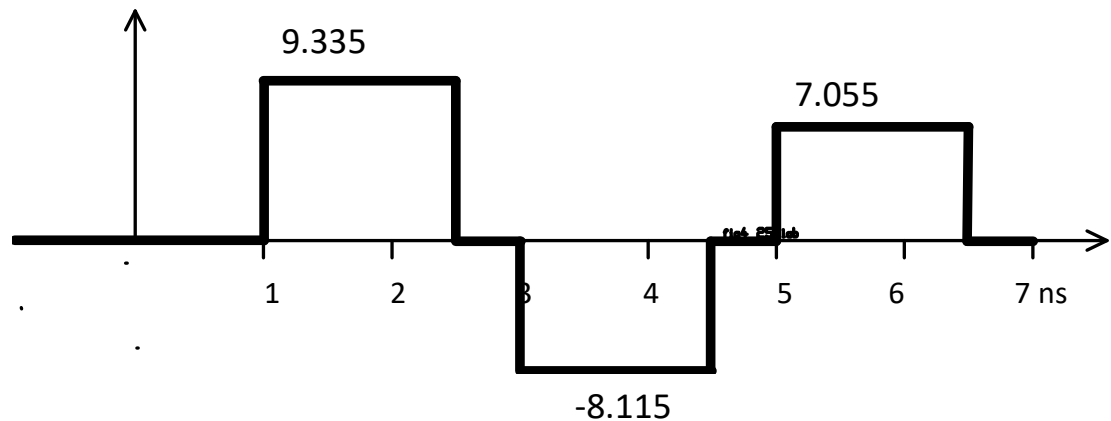
$$V_{pulse}(t) = 5[V_{step}(t) - V_{step}(t - 1.5)]$$



Tracking the Leading Edge and the Trailing Edge

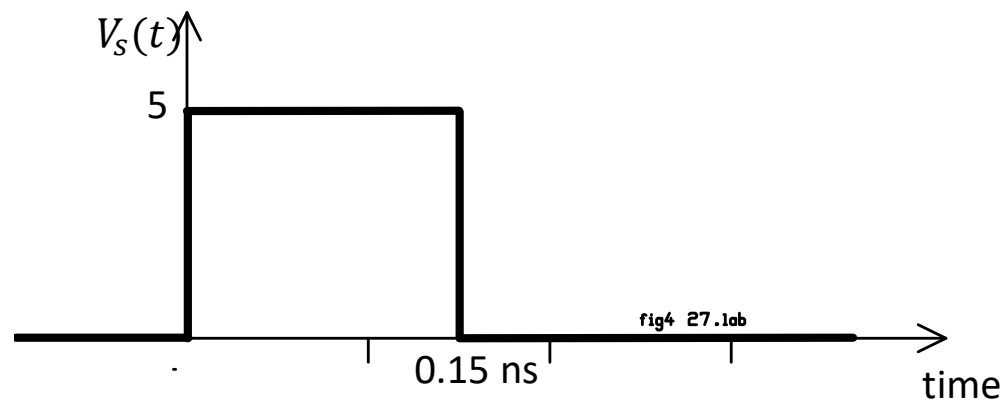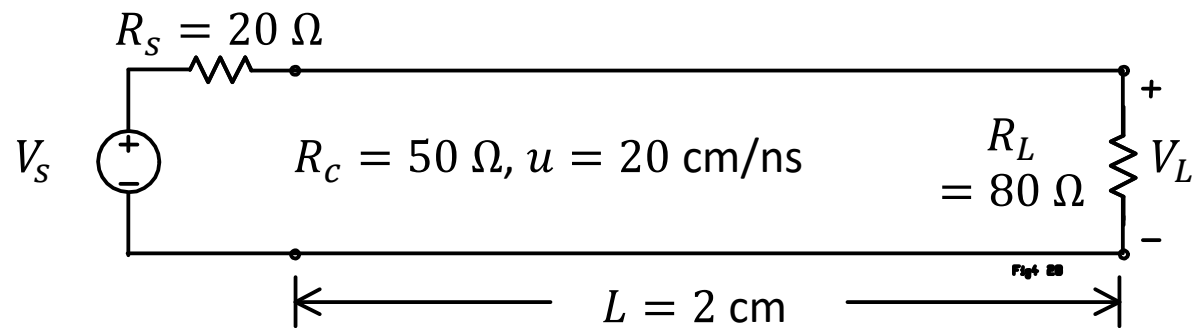Another way to find the pulse response is to draw a bounce diagram that keeps track of the leading edge of the pulse and of the trailing edge of the pulse.



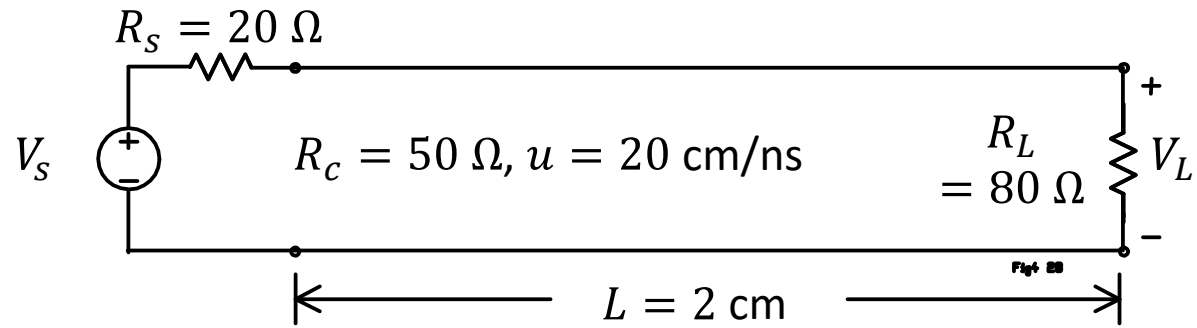


$$T_d = \frac{L}{u} = \frac{2}{20} = 0.1\text{ ns.}$$

$$\Gamma_s = \frac{R_s - R_c}{R_s + R_c} = \frac{20 - 50}{20 + 50} = -0.4286$$


$$\Gamma_L = \frac{R_L - R_c}{R_L + R_c} = \frac{80 - 50}{80 + 50} = 0.2307$$

$$V(0, t) = \frac{R_c V_x}{R_c + R_s} = \frac{50 \times 5}{50 + 20} = 3.57\text{ volts.}$$

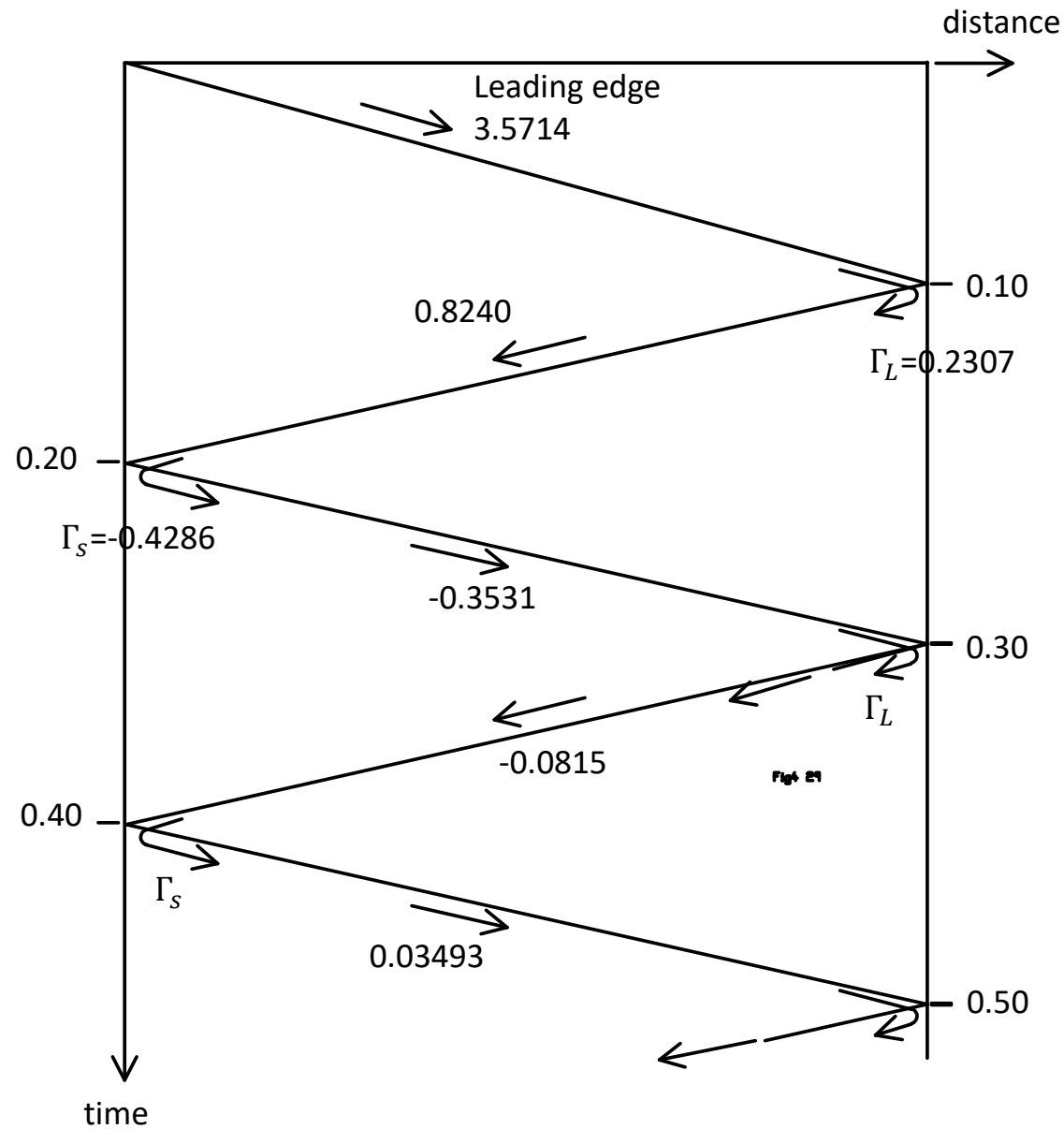
Track the leading edge of the pulse to find the step response:




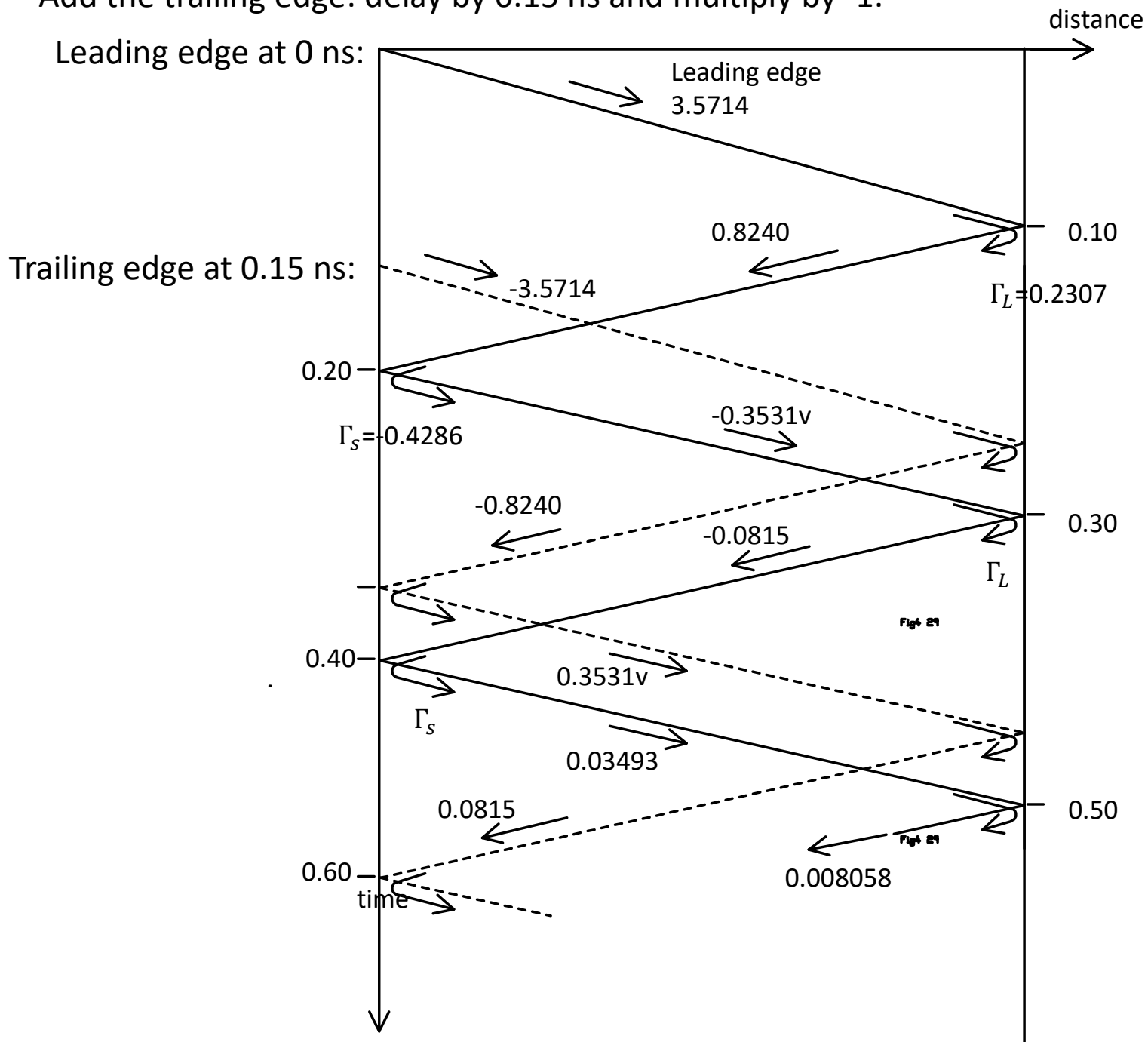
Add the trailing edge: delay by 0.15 ns and multiply by -1.



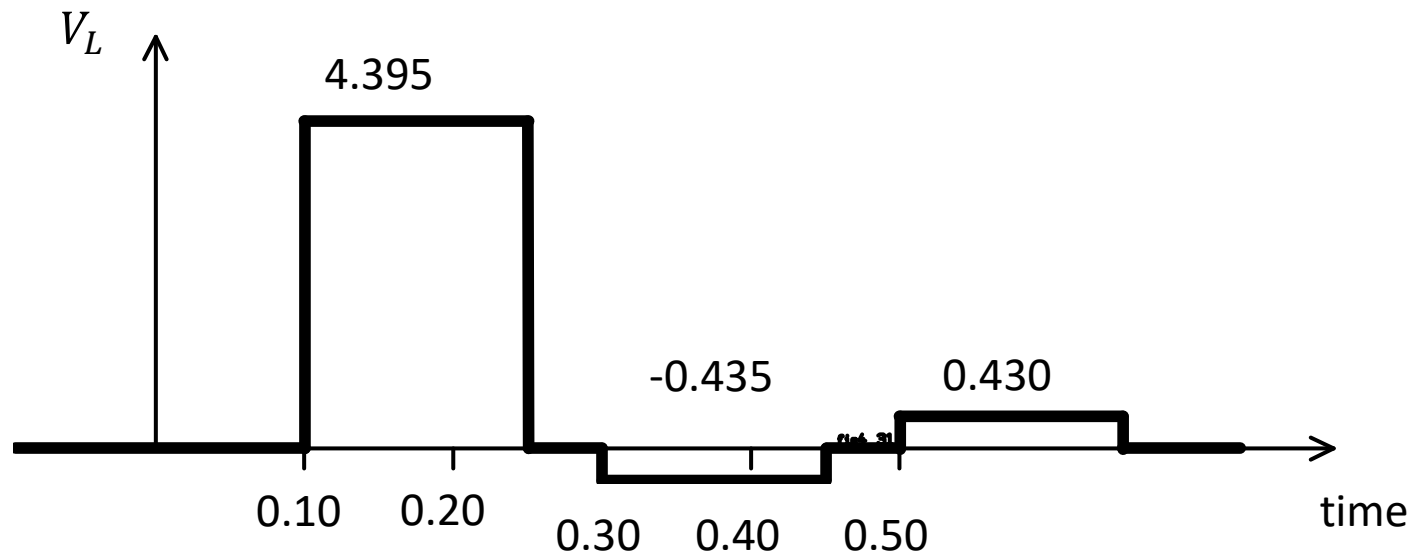
To find the voltage at the load, go down the time axis starting at the top at $t=0$:



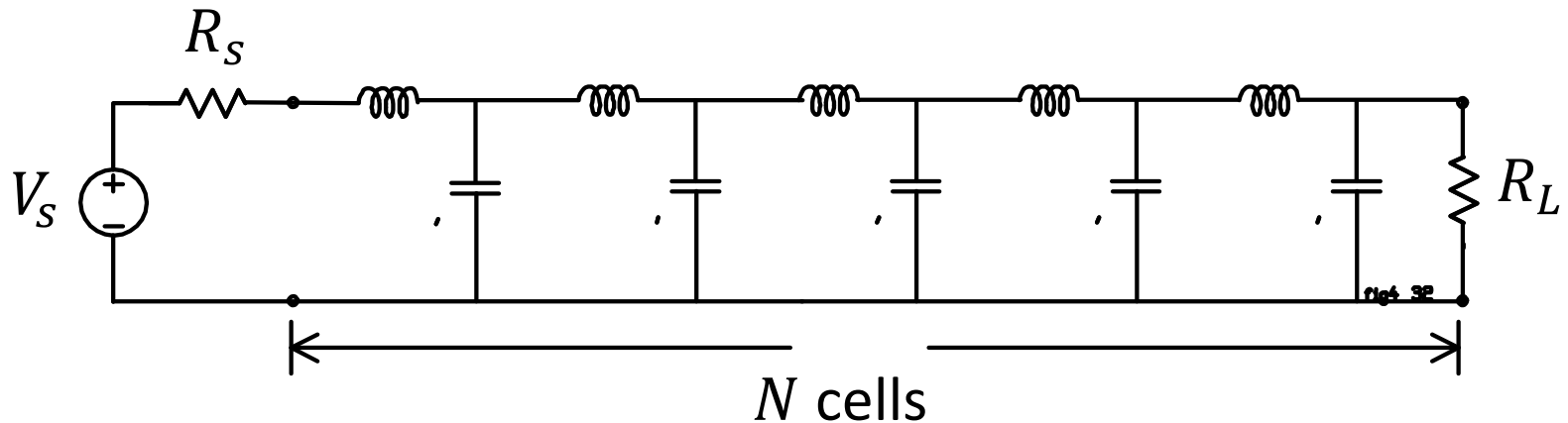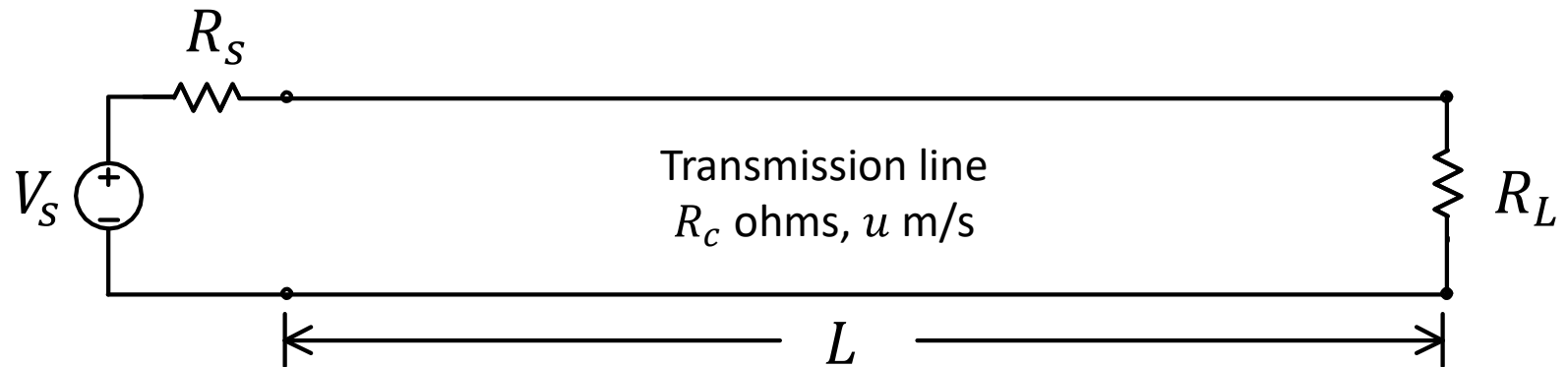Final Values in Transmission-Line Circuits




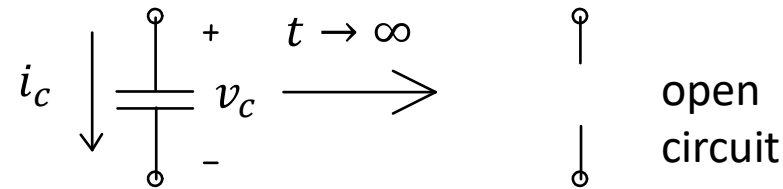Final Values for Capacitors and Inductors






$$i_c = C \frac{dv_c}{dt}$$

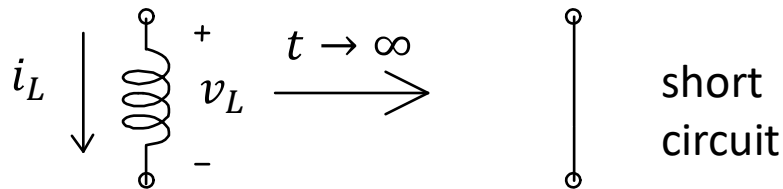As $t \rightarrow \infty$, $\frac{dv_c}{dt} \rightarrow 0$ and $i_c = C \frac{dv_c}{dt} \rightarrow 0$ and the capacitor becomes an open circuit.




$$v_L = L \frac{di_L}{dt}$$

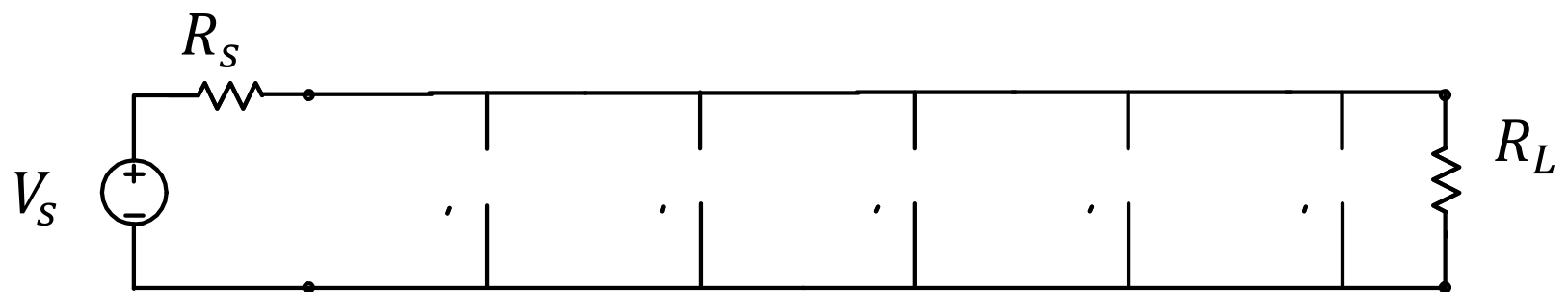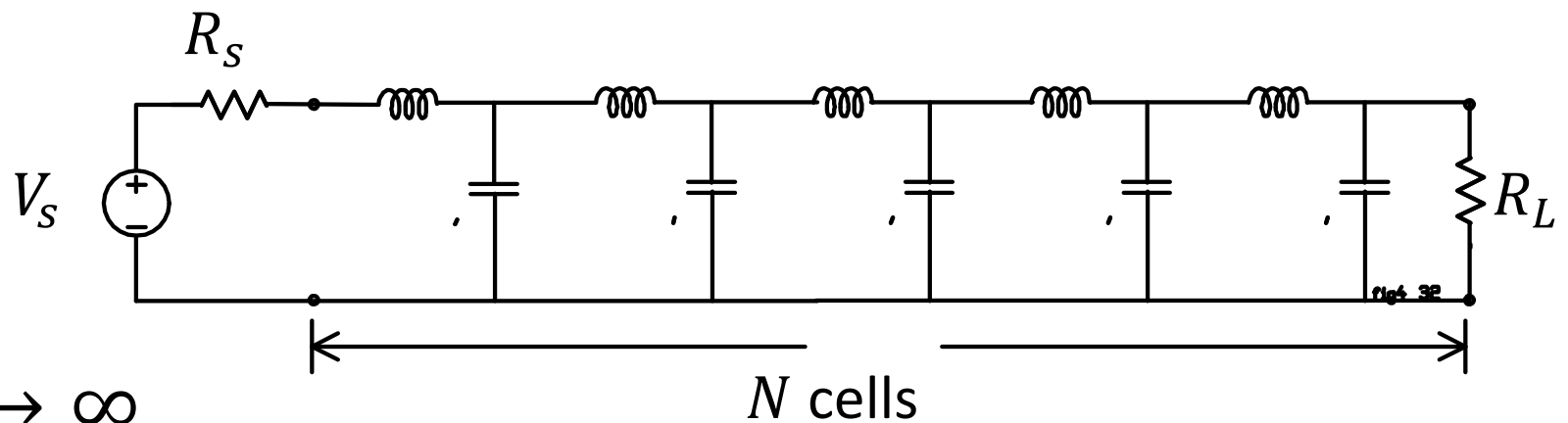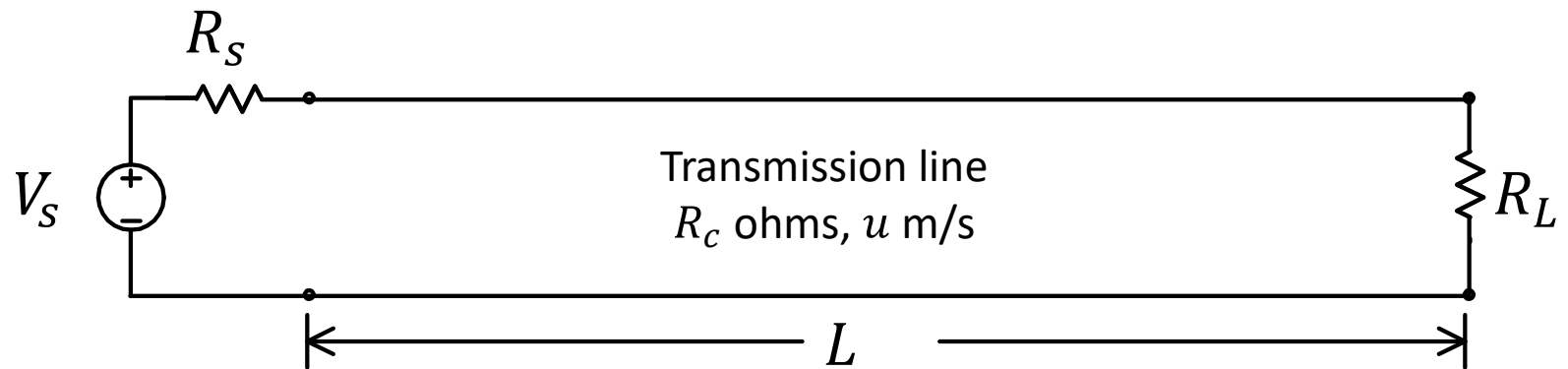As $t \rightarrow \infty$, $\frac{di_L}{dt} \rightarrow 0$ and $v_L = L \frac{di_L}{dt} \rightarrow 0$ and the inductor becomes a short circuit.




To calculate the final value of the voltages and currents, make C 's open circuits and L 's short circuits.

Final Values Circuit

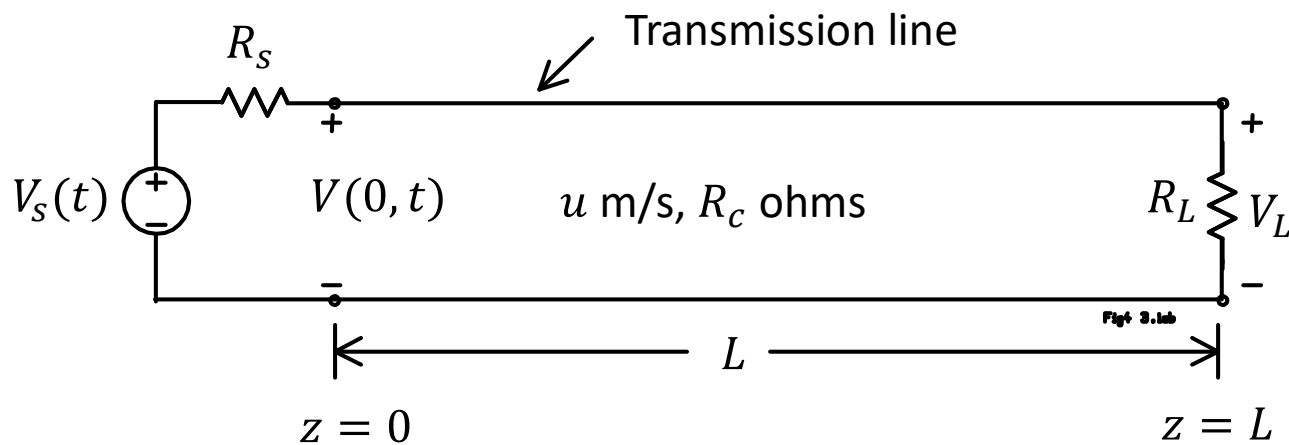


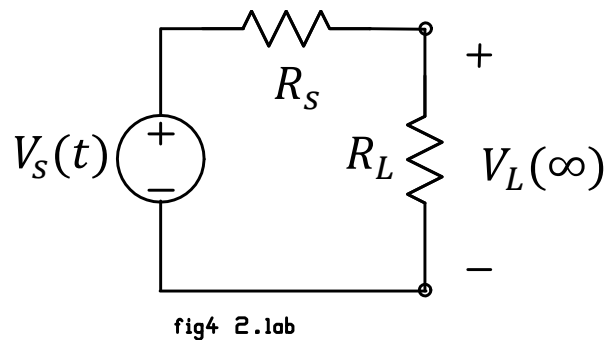- Replace L by a short circuit
- Replace C by an open circuit
- Hence, the transmission line becomes an ideal short circuit.




$$V_L(\infty) = \frac{R_L}{R_s + R_L} V_s(\infty)$$

Example

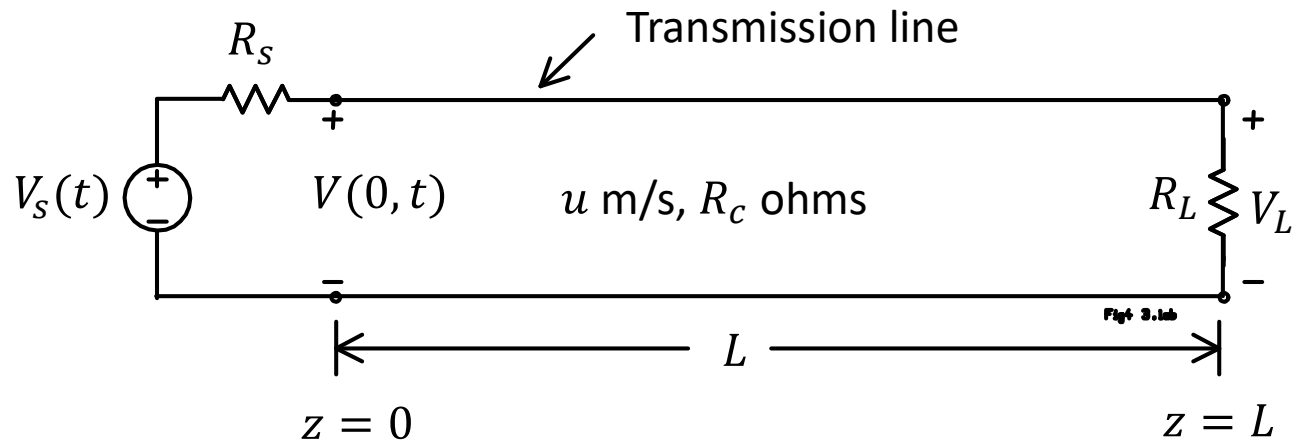

The generator $V_S(t)$ is a step function of height 5 volts starting at $t = 0$. The internal resistance is $R_S = 10$ ohms and the load resistor is $R_L = 100$ ohms. Find the final value of the voltage across the load V_L .

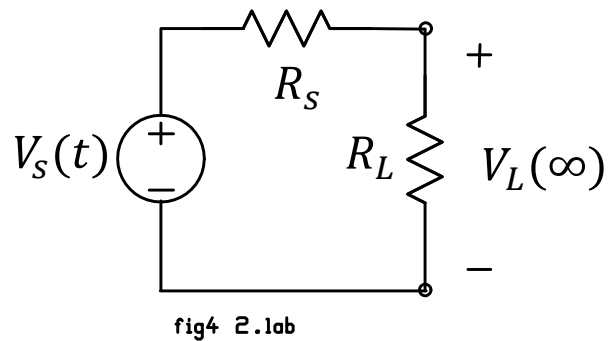Final Values Circuit: the transmission line behaves like an ideal short circuit.



$$V_L(\infty) = \frac{R_L}{R_S + R_L} V_S(\infty) = \frac{100}{10 + 100} \times 5 = \frac{100}{110} \times 5 = 4.55 \text{ volts}$$